

3

~~2M~~

(219)

-: HAND WRITTEN NOTES:-

OF

ELECTRICAL ENGINEERING

(1)

-: SUBJECT:-

POWER ELECTRONICS

3

To

TOPICS

1. Power semiconductor devices - 25%
2. Phase controlled rectifiers - 35%
 - Application → DC drives
 - Charging batteries
 - Solar batteries
3. Inverters - 12%
4. Choppers - 12 - 15%
5. AC Voltage controllers & cycloconverters - 3 to 4%
6. Other applications - 7 - 10%.
 - AC drives
 - HVDC
 - SMPS

POWER SEMICONDUCTOR DEVICES

(4)

Power Electronics - deals with control of conversion of high power applications.

Power Semiconductor devices - should be capable to handle large magnitudes of power.

e.g. Power diode, SCR(PN), LASCR, GTO, ASCR, RCT, TRIAC, DIAC, Power transistors (BJT, MOSFET, IGBT) (f[↑])

Signal Electronics - deals with control of low power applications.

Signal Devices - handle low power & very high switching frequencies.

e.g. Signal diodes → Zener diode
→ LEDs
→ Varactor diode

Signal transistors → BJT
→ MOSFET
→ UJT etc.

* In the fabrication of semiconductor devices we must sacrifice one quality in order to improve the other quality.

e.g. If the device operates at very high switching frequency the power rating is reduced.


* A switch can be utilized in 4 different modes but all the devices need not operate in all the 4 modes.

* FOUR MODES OF A SWITCH (Ideal)

1. Forward Blocking Mode


(5)

$$S(\text{off}) \quad (-V_F, 0)$$

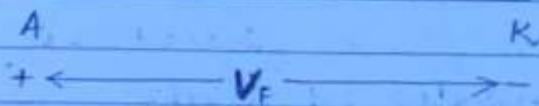


2. Forward Conduction Mode

$$(0, I_F)$$

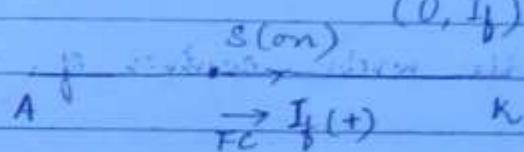

3. Reverse Blocking Mode

$$S(\text{off}) \quad (V_R, 0)$$

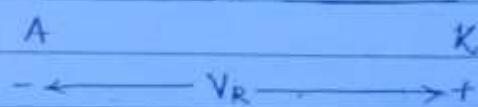

4. Reverse Conduction Mode

$$S(\text{on}) \quad (0, I_R)$$



$$(0, I_B) \quad FC$$

$$\begin{matrix} R_B \\ \times \\ (V_R, 0) \end{matrix}$$


$$(0, J_R) \times RC$$

$$\begin{matrix} I \\ \times \\ FO \\ (V_F, 0) \end{matrix}$$



$$V_{AK}$$

- * TRIAC will support all four modes of operation.
∴ It's treated as an AC switch. ($AC \rightarrow AC$)
- Applications \rightarrow AC voltage controllers (6)
- * SCR is a DC switch because it will not support reverse conduction.


POWER DIODE -

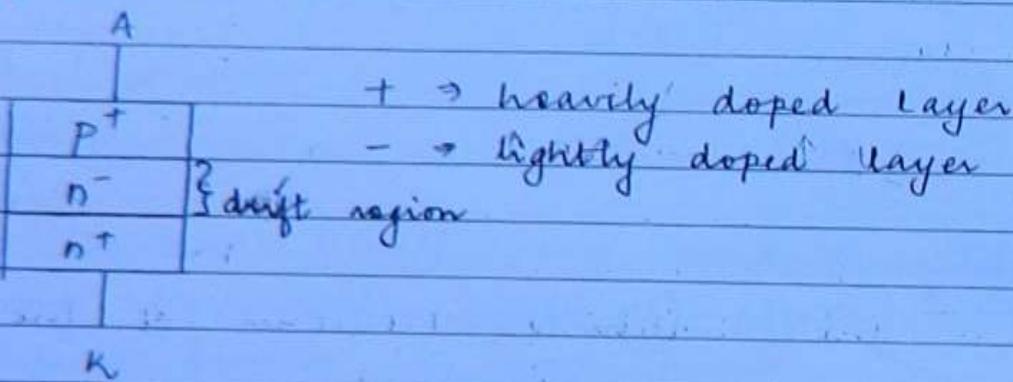

Signal Diode -

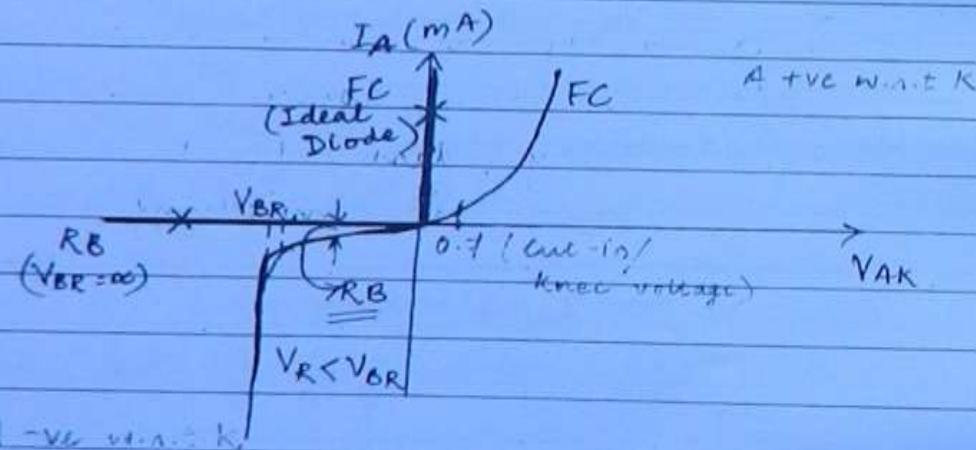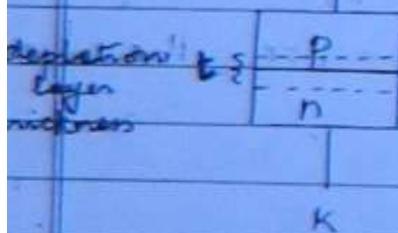

Power Diode -

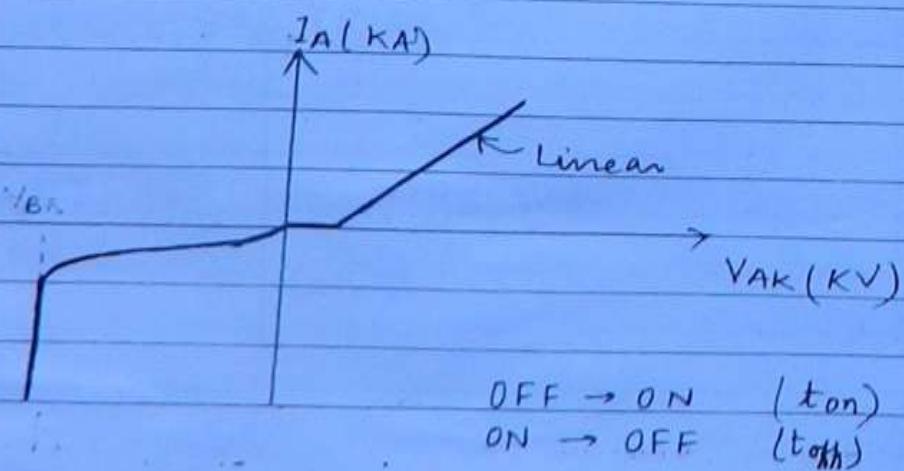

Significance of drift region -

(7)


- * The thickness of the depletion layer decides the reverse blocking voltage capability.
- * The thickness of the depletion layer \uparrow , due to the n-region (depletion layer penetrates more deeper into the lightly doped layer to equilise the charge) this \uparrow the reverse blocking capability of the diode.

Input Diode \rightarrow NRI \uparrow

REVERSE RECOVERY CHARACTERISTICS -

- * Explains the switching behaviour of the diode from ON time to OFF time.
- * When diode is conducting some excess is stored in the device. These excess charge carriers are mainly due to the minority carriers. When diode is switching from ON \rightarrow OFF, the excess charge carriers are still present in the device after anode current becomes 0.
- * In order to remove these excess charge carriers and acquire equilibrium state, recombination process takes place & hence reverse current flows in the device until all the excess charge carriers are removed from the device.
- * This process is known as Reverse Recovery Process & the transition time during this process is known as Reverse Recovery Time (t_{rr}).

8

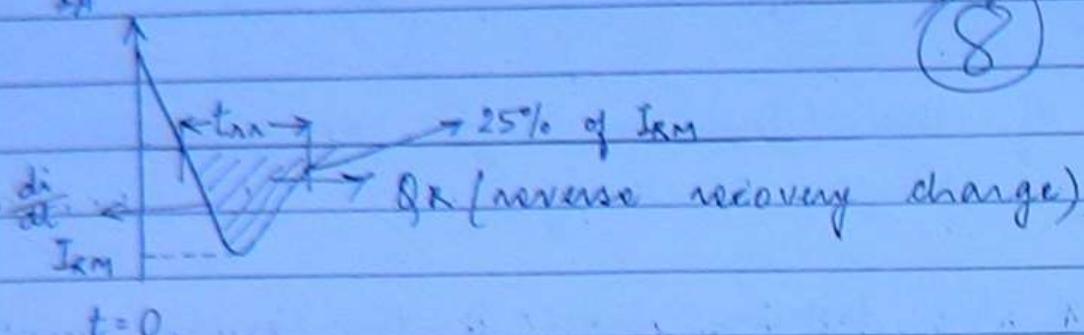 $ON \rightarrow OFF$

$$t_{RR} \Rightarrow (I_A = 0) - t_0 : (\downarrow I_A = 25\% \text{ of } I_{RM})$$

$$I_{RM} = \left[\frac{eQ_R}{dt} \right]^{\frac{1}{2}}$$

$$t_{RR} = \left[\frac{eQ_R}{di/dt} \right]^{\frac{1}{2}}$$

< Q_R depends on I_A .

$$\begin{aligned} I_A \uparrow &\Rightarrow Q_R \uparrow \\ \therefore I_{RM} \uparrow &\text{ f. thm } t_{RR} \uparrow \end{aligned}$$

* The t_{RR} decides the switching frequency of the diode.
 $t_{RR} \uparrow \Rightarrow f_s \downarrow$

Classification of Power Diodes based on Reverse Recovery Time (t_{RR}):

1. General Purpose Diode
2. Fast Recovery Diode
3. Schottky Diode

(Slow)

- (high speed) -

General Purpose
Diodes

Fast Recovery
Diode

Schottky Diode

Q

1. $t_{RN} \rightarrow 25 \mu s$

$t_{RN} \rightarrow 5 \mu s$ (en)

$t_{RN} \rightarrow$ nano secs

2. $I_{Rating} \rightarrow 1A$ to several
1000's of A.

$I_{Rating} \rightarrow 1A$ to
several 100's of A.

$I_{Rating} \rightarrow$ limited
to 300 A.

$V_{Rating} \rightarrow 50V$ to 5kV

$V_{Rating} \rightarrow 50V$ to 3kV.


$V_{Rating} = 100V$.

- * In fast recovery diodes, the layers are doped with gold / platinum.
- * Gold / platinum doping \Rightarrow reduces the lifetime of charge carriers & increases the speed of recombination. This reduces the reverse recovery time.
- * Used in choppers & inverters
- * Schottky diode is a metal to semiconductor junction diode. Here the conduction is only due to majority carriers.
- * Since there is no minority charge carriers the t_{on} delay is very much reduced \therefore it operates at very high switching frequency.
- * Due to the absence of drift region, the thickness of depletion layer is reduced \therefore it can block a small reverse voltage limited to 100V.
- * Can be used in low power high switching frequency applications.
e.g. Switch Mode Power Supply (SMPS)
- * Used in uncontrolled rectifiers, free wheeling diodes for rectifiers.

Diode is an uncontrolled device because there is no control terminal to decide its on/off state.

(10)

SCR -

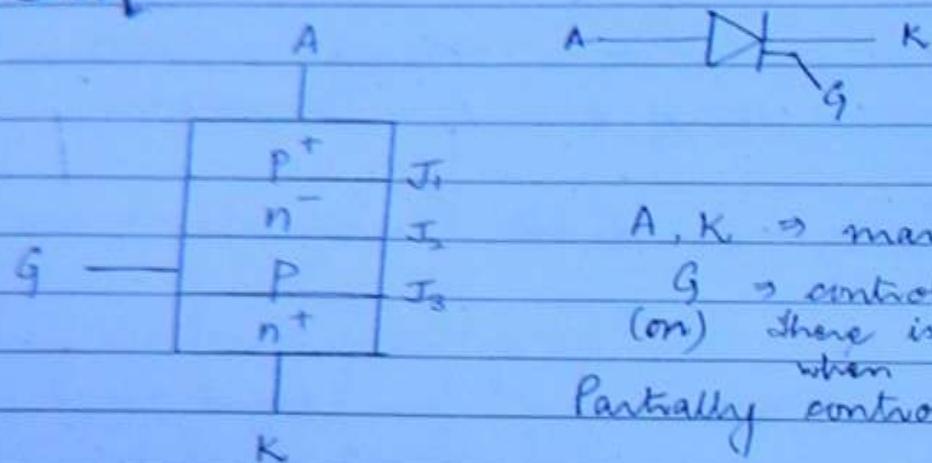


A, K \Rightarrow main terminals

G \Rightarrow control terminals

(on) There is no control of gate when SCR is ON.

Partially controlled device

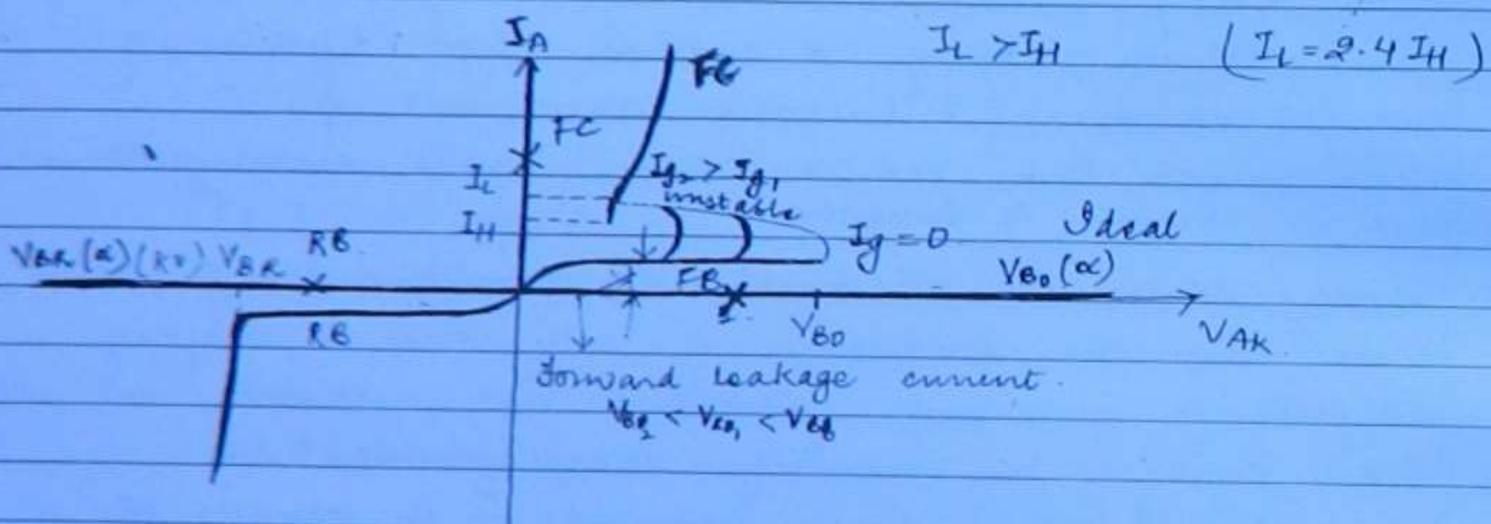

Forward Blocking Mode - A +ve w.r.t K

$J_1, J_3 \Rightarrow FB$

$J_2 \Rightarrow KB$.


\therefore SCR \rightarrow OFF.

Forward Conduction Mode

V_{AK}^+ (forward breakdown voltage)
 $V_{AK} \uparrow \Rightarrow V_{BD}$ then breakdown occurs
 at J_2 \therefore SCR \rightarrow ON

(11)

Significance of gate signal -

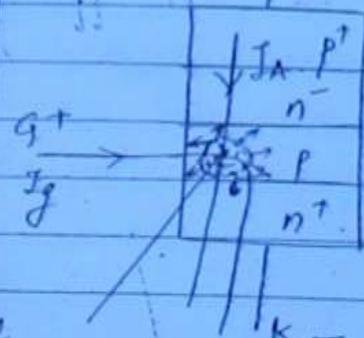

When gate signal is applied, charge gets accumulated in depletion region p, $I_A \uparrow$ and \uparrow the "charge" accumulation as it gets a conduction path. This leads to \uparrow of charge & thus breakdown of depletion region turning on the SCR.

If $I_g \uparrow$ or $\frac{dI_g}{dt} \uparrow$ Initial conduction Area \uparrow

$\Rightarrow \frac{dI_A}{dt} \uparrow$ and lesser V_{tg} is need for breakdown i.e less V_{ao} .

Reverse Blocking Mode -

A ~~needs~~ -ve w.r.t K.

$J_2 \Rightarrow FB$

$J_1, J_3 \Rightarrow RB$

SCR \rightarrow OFF


Significance of Latching Current -

- Latching current is related to turn on process
- When SCR is in the ON state, gate signal is removed to avoid the continuous gate power loss
- If we remove the gate signal when $I_A < I_L$ then SCR fails to turn off. We must maintain the gate pulse width until I_A reaches just above certain minimum value (Latching current)
- When we remove gate signal, when $I_A > I_L$ then

After minimum SCR continues to be the ON state.

Q What is the minimum gate pulse width required to turn on the SCR in the following circuit.

$$I_L = 100 \text{ mA}$$

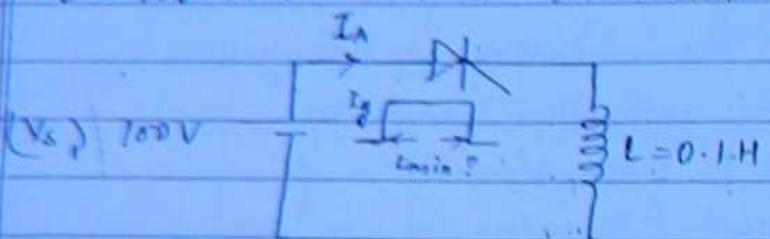

(12)

$$V_S = L \frac{dI_A}{dt}$$

$$\int dI_A = \int V_S dt$$

$$I_A = \frac{V_S}{L} \cdot t \Rightarrow t_{\min} = \frac{I_A \times L}{V_S}$$

$$t_{\min} = \frac{I_L \times L}{V_S} = \frac{100 \times 10^{-3} \times 0.1}{100}$$

$$t_{\min} = 100 \mu\text{sec.}$$

* The minimum gate pulse width requirement to turn on the SCR depends on the load parameters.

e.g. $L \uparrow \rightarrow t_{\min} \uparrow$

if Load is $R = 20 \Omega$ $L = 0.1 \text{ H}$ in prev ques.

$$V_S = L \frac{dI_A}{dt} + R I_A$$

$$I_A = \frac{V_S (1 - e^{-RT})}{R}$$

$$T = \frac{L}{R} = \frac{0.1}{20} = \frac{1}{200}$$

$$I_A = 5 (1 - e^{-200t})$$


$$I_L = 5 (1 - e^{-200t_{\min}})$$

$$t_{\min} = 101 \mu\text{s}$$

Significance of Holding current -

(T3)

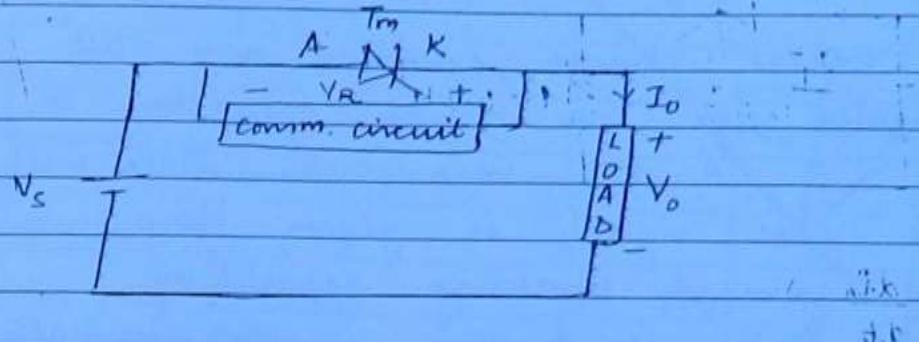Holding current is related to turn OFF process.
Gate has no control to turn OFF SCR. In some cases we require commutation circuit to turn OFF SCR.



Comm SCR forces anode current to reduce below I_H . After that it applies reverse voltage to remove all charge carriers ⁱⁿ the device.

* Procedure to turn OFF SCR using a commutation ckt -

Commutation circuit forces anode current to reduce below a certain minimum value & then applies a reverse voltage across the SCR atleast for a period of device turn off time or greater than that.

Circuit turn-off time (t_c)

It is the time for which the comm circuit applies a reverse voltage across after the anode current becomes 0. W

Device turn off time (t_d)

It is the time taken to remove charge carriers present in the device provides the t_d .

will turn on before applying gate (behaves as diode) Page

In successful commutation $t_c > t_q$ always

If $t_c < t_q$ commutation fails

(14)


Q what do you mean by commutation failure?

If $t_c < t_q$ some excess charge carriers are still present in the device. For the next operation to turn on the SCR if A +ve w.r.t K, SCR will turn on before the gate signal is given. Here the SCR is losing forward blocking capability behaving as a diode. This is known as commutation failure.


To avoid this problem, the commutation circuit should apply reverse voltage across the SCR atleast for a period of t_q or greater than that.

Holding current is the minimum I_A below which the SCR becomes off and regains the forward blocking capability if a reverse voltage is applied across SCR atleast for a period of t_q or more than that.

Switching Characteristics of SCR -

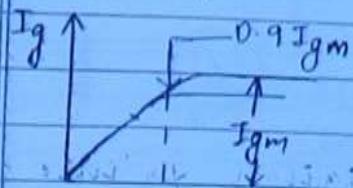

(IS)

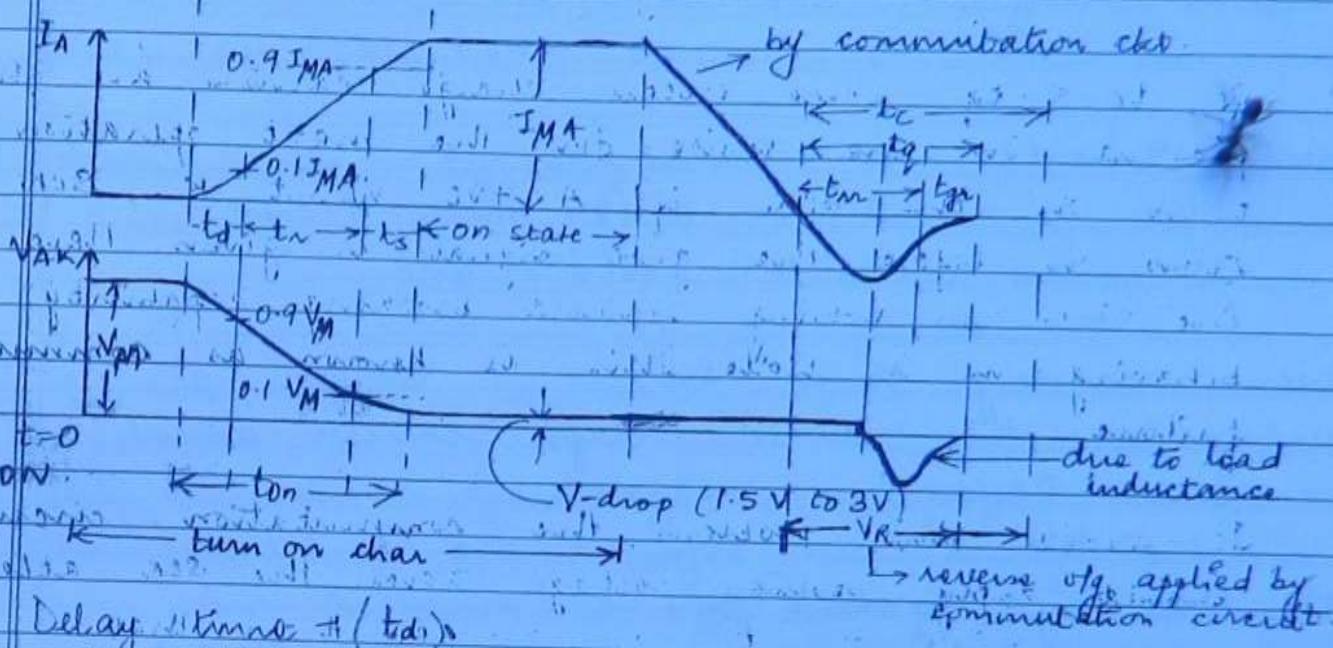

Delay time: t_d (t_{di})

depends on gate signal magnitude & d/dt of gate signal magnitude.

Delay time $\Rightarrow 0.9 I_{gm}$ to $0.1 I_{MA}$
 $0.9 I_{gm}$ to $0.9 V_m$

Delay time depends on $\Rightarrow I_g \uparrow$ & $\frac{dI_g}{dt} \uparrow \Rightarrow t_d \rightarrow 0$
 $\therefore t_{on} \downarrow$

\Rightarrow (initial conduction area) \uparrow
 $\frac{dI_A}{dt} \uparrow$ initial state
 $t_d \downarrow$

Rise time (t_r) 0.1 IMA to 0.9 IMA
 0.1 V_M to 0.9 V_M

(16)

Rise time depends on Load parameters
eg. $L \propto \frac{dI}{dt} \downarrow \therefore t_r \uparrow, t_{on} \uparrow$

Spread time (t_s) 0.9 IMA to I_{MA}
 0.1 V_M to (ON state V-drop)
 (1.5 to 3 V)

Reverse recovery time (t_{rr})

During t_{rr} the excess charge carriers present in the outer layers is reduced.

Gate Recovery time (t_{gr})

During t_{gr} the excess charge carriers present in the inner layers near the gate junction is removed.

Device turn off time (t_d)

$$t_d = t_{rr} + t_{gr}$$

The device turn off time is generally very much greater than turn on time. Therefore the device turn off time decides the switching characteristics of the SCR.

$t_d \rightarrow$ slow thyristors (converter grade thyristors)
 $t_d \rightarrow 50\mu\text{s}$ to $100\mu\text{s}$

\rightarrow fast thyristors (inverter grade thyristors)

$$t_d \rightarrow 3\mu\text{s}$$
 to $50\mu\text{s}$

For successful commutation $t_c > t_q$

Page


(17)

$$t_c = SF \cdot t_q$$

SF > 1 for successful comm.
(safety factor)


TURN - ON / TRIGGERING METHODS OF SCR -

1. Forward voltage triggering -

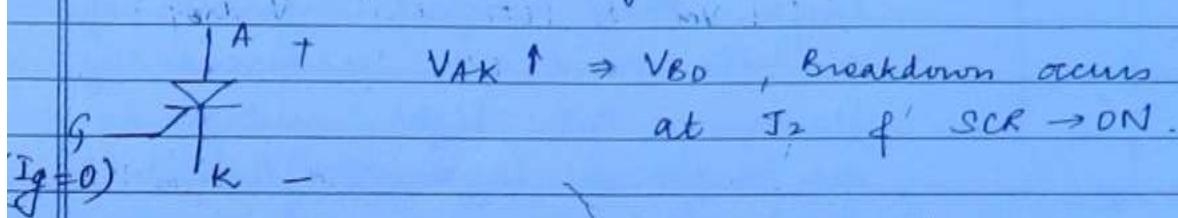

This method is generally not preferred because the SCR may get destroyed due to high power loss when triggered at high voltage.

2. dv/dt triggering -

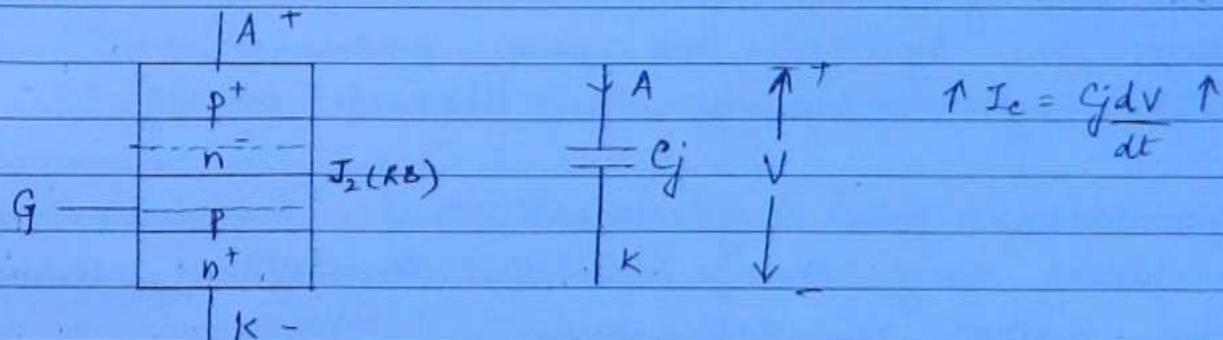


At high dv/dt the charging current increases. If the increase in charging current is more than the latching current then SCR is turned on.

Critical dv/dt → It's the dv/dt at which SCR will turn on. At critical dv/dt charging current is equal to latching current i.e. $I_c = I_L$.

(18)

3 Light triggering -

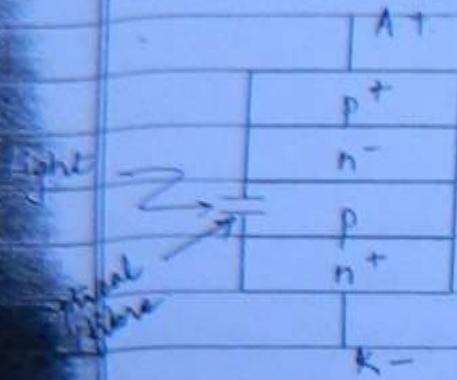

When light radiation is incident near the depletion layer then more number of e⁻-hole pairs are produced by absorbing the light energy in the depletion layer, if this initiates the turn on process.

Application → Used in LASCRs for HVDC applications.

Thermal triggering -

When temperature is increased near the reverse biased gate junction, then the device is initiated to turn on by e⁻-hole pairs produced in depletion layer absorbing the thermal energy.


Semiconductors are very sensitive of the characters of the device may change as the temperature changes, so this method is not used.

Gate triggering -

(a) Continuous Gate Triggering -

Continuous gate signal is applied until the SCR is expected to be in the ON state. This is not efficient triggering due to continuous gate power loss.

(b) Pulse gate signal -

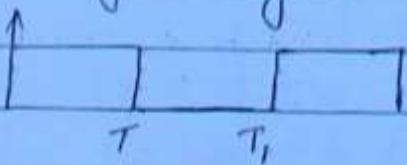

79


T = gate pulse width

$T > t_{min}$

$T_1 \rightarrow$ time period

$$d = \frac{T_1}{T} = \text{duty cycle.}$$

(c) High frequency gate signal


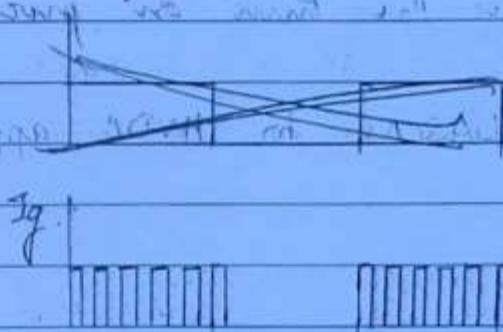


Adv.

→ reduces the size of pulse transformer

↓
provides electrical isolation b/w high power main circuit & low power gate firing circuit.

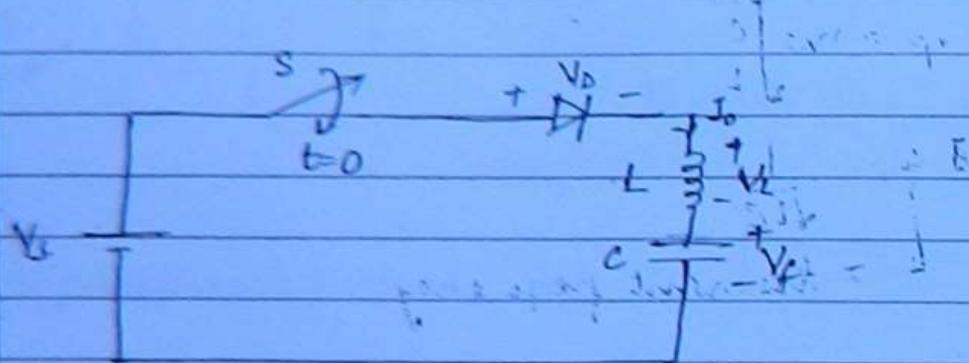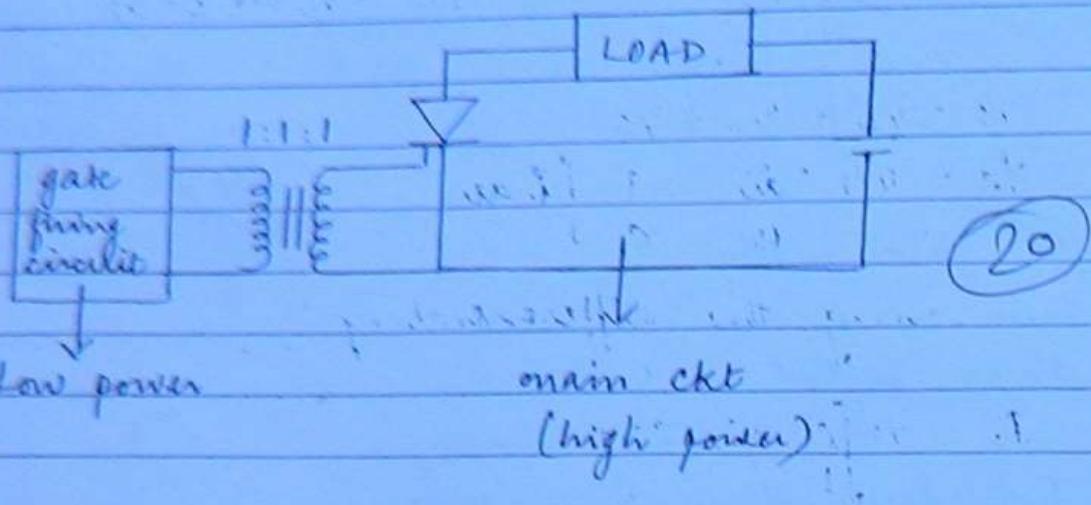→ we can trigger more than one SCR using a pulse transformer.



$$V_C(t=0) = 0 \text{ V}$$

- i) When switch is closed at $t=0$ then diode conducts if
- $\pi\sqrt{LC}$
 - $\pi\sqrt{LC}$
 - $\pi\sqrt{3LC}$
 - $\pi\sqrt{LC}$

ii) $V_C = ?$ when diode stops conducting

- V_s
- αV_s
- $-V_s$
- $-\alpha V_s$

Qd. i) $S \rightarrow DN$ ($t=0$) $R_D = D = FB$ (on at $t=0$)

$$V_S = V_D + V_L + V_C$$

$$V_S = 0 + \frac{L di}{dt} + \frac{1}{C} \int i dt$$

(21)

on solving the differential eq.





$$I_o = V_S \sqrt{\frac{C}{L}} \sin \omega_0 t$$

$$I_o = I_p \sin \omega_0 t$$

$$\text{where } I_p = V_S \sqrt{\frac{C}{L}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Resonant frequency

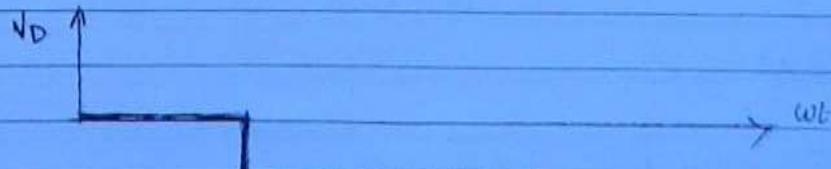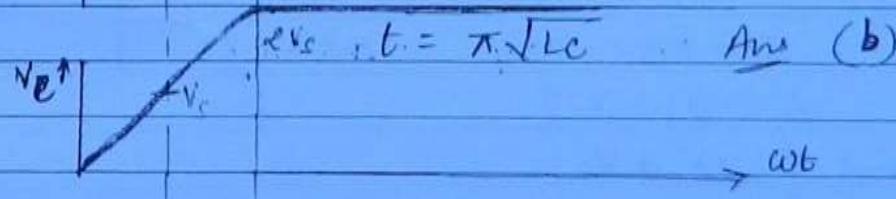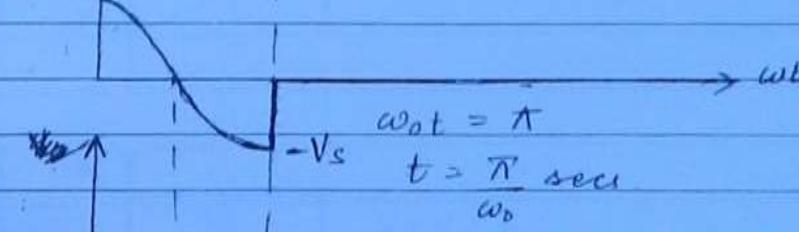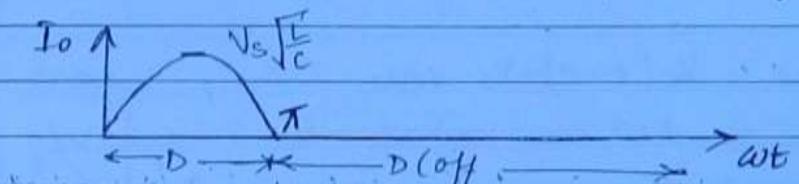

PIV of diode = V_S

$$V_L = L \frac{dI}{dt}$$

$$= L \frac{d}{dt} (I_p \sin \omega_0 t)$$

$$V_L = V_s \cos \omega_0 t$$

$$V_C = V_s - V_L$$

$$= V_s + L V_s \cos \omega_0 t$$

$$V_C = V_s (1 + \cos \omega_0 t)$$

$$-V_s + V_D + 0 + 2V_s = 0$$

$$V_D = -V_s$$

(22)

From 0 to 90°

$$\text{Source} \rightarrow \frac{1}{2} L I^2 + \frac{1}{2} C V^2$$

From 90° to 180°

$$\frac{1}{2} L I^2 \rightarrow \frac{1}{2} C V^2$$

In prev ques assume $V_C(t=0) = V_0$ volts where $V_0 < V_s$.

i) When switch is closed at $t=0$ secs what's the cap. v/g (V_C) after the diode stops conducting.

- a) $\alpha(V_s + V_0)$
- b) $\alpha(V_s - V_0)$
- c) $\alpha V_s + V_0$
- d) $\alpha V_s - V_0$

$\rightarrow ON$ ($t=0$)

$$D = FB$$

$$V_s = 0 + L \frac{di}{dt} + \frac{1}{C} \int i dt + V_0$$

$$V_s - V_0 = L \frac{di}{dt} + \frac{1}{C} \int i dt$$

$$I_o = (V_s - V_0) \sqrt{\frac{C}{L}} \sin \omega_0 t \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$I_o = I_p \sqrt{\frac{C}{T}} \sin \omega_0 t$$

$$V_L = L \frac{di}{dt} (\text{I} \sin \omega t)$$




$$V_L = (V_s - V_o) \cos \omega t$$

$$V_C = V_s - V_L$$

$$= V_s - (V_s - V_o) \cos \omega t$$

$$V_C = V_s(1 - \cos \omega t) + V_o \cos \omega t$$


(23)

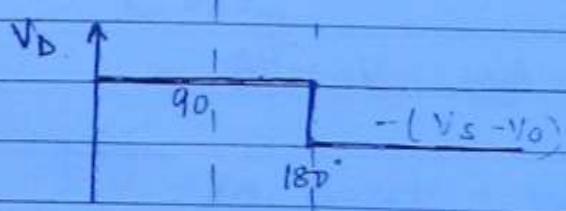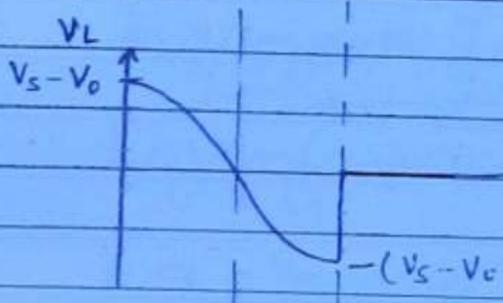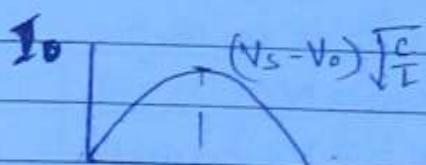

$$PIV = V_s - V_o$$

Ans $V_C = \vartheta V_s - V_o$

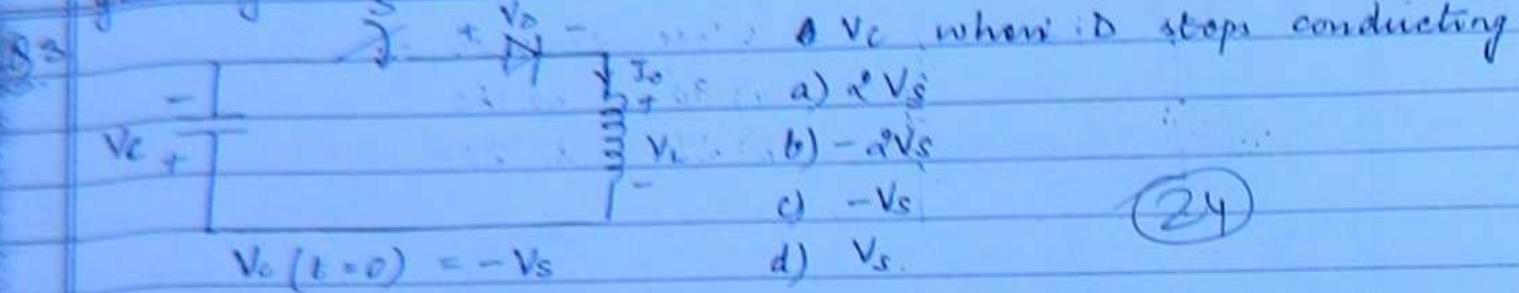When charging current of cap behaves as an ^{improper} function of time given by $V_c = V_s \cos \omega t$.



$$V_o + V_D + V_L = 0$$




$$V_L + (V_c - V_s) = 0$$

$$\therefore V_s = V_L + V_c$$

$$V_s = L \frac{di}{dt} + \int i dt$$

$$I_o = V_s \sqrt{\frac{C}{L}} \sin \omega t$$

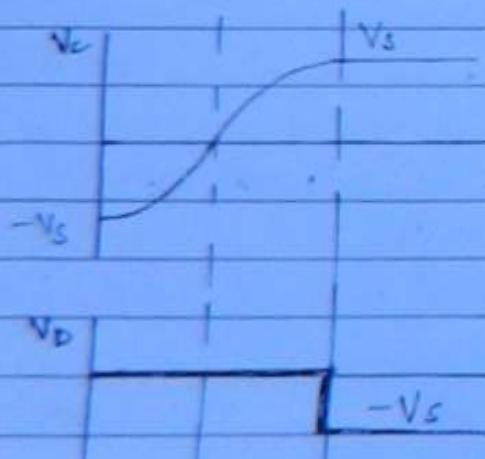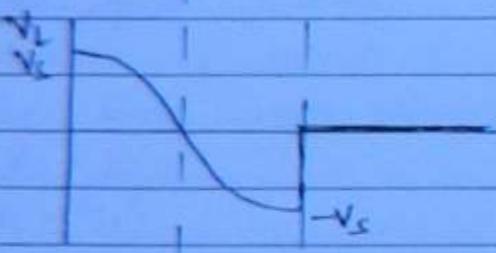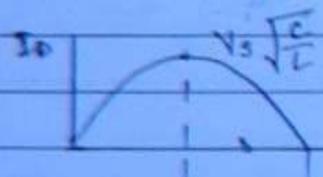Ans same as $I_o = V_s \sqrt{\frac{C}{L}} \sin \omega t$ (a)



$$V_L = L \frac{di}{dt} (I_p \sin \omega t)$$

$$V_L = V_s \cos \omega t$$

$$\therefore V_c = V_s + V_L$$

$$V_c = -V_s \cos \omega t$$

$$(1) \text{ W.A. is } 1$$


Ans $V_c = V_s$

$$P1 V = V_s$$

Q4. If $V_c(t=0) = V_s$ then cap vlg reverses of $V_c = -V_s$

ATE

Q4

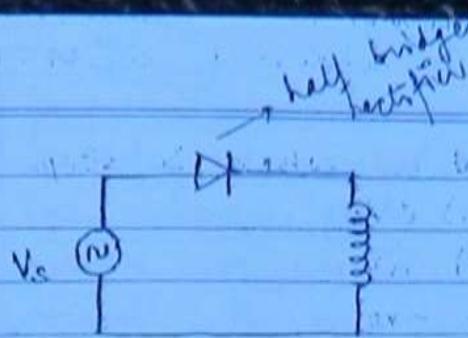

- Diode conducts for
 a) 90° b) 180°
 c) 270° d) 360°

(D)

sol.

$$V_s = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$\int di = \int V_m \sin \omega t dt$$

$$V_s = V_m \cos \omega t + C$$

$$V_s = V_m (\cos \omega t - 1)$$


$$I = -\frac{V_m}{\omega L} \cos \omega t + K$$

$$\text{At } \omega t = 0 \quad I = 0$$


$$0 = -\frac{V_m}{\omega L} \cos 0 + K$$

$$K = \frac{V_m}{\omega L}$$
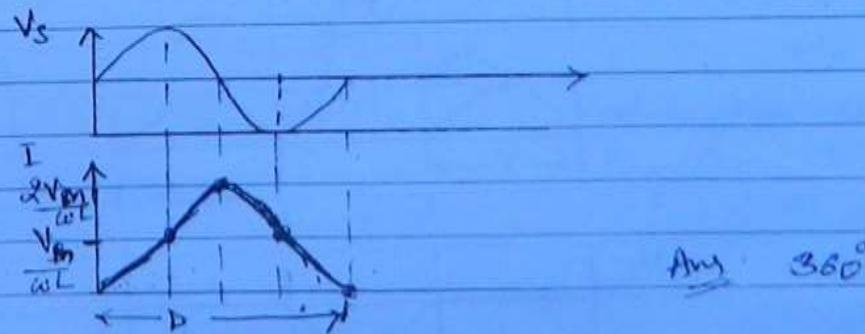
$$I = -\frac{V_m}{\omega L} \cos \omega t + \frac{V_m}{\omega L} = \frac{V_m}{\omega L} (1 - \cos \omega t)$$



85

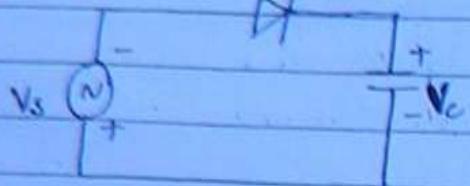

Diode conducts for

- a) 90° b) 180°
 c) 270° d) 360°

sol

$$V_C + V_S = 0$$

$$V_S = -V_C$$

$$V_{m \sin \omega t} = -\frac{1}{C} \int i \, dt$$

$$I = -V_m C \times \omega \times \sin \omega t$$

$$I = -V_m C \omega \cos \omega t$$

(26)

COMMUTATION TECHNIQUES


1. Natural / Line Commutation -

If nature of supply supports commutation process
 it's called natural commutation.

e.g. Rectifiers

AC voltage controllers



Step down cyclo converters

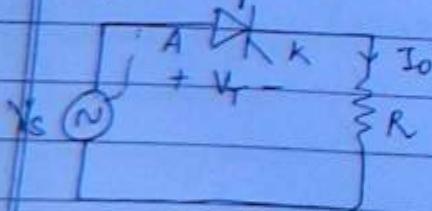

$T \rightarrow \text{ON}$

$$I_0 = \frac{V_S}{R}$$

$$I_0 = \frac{V_{m \sin \omega t}}{R}$$

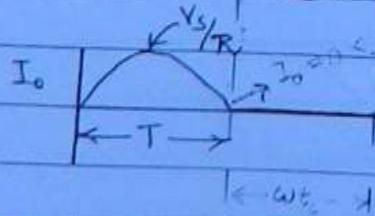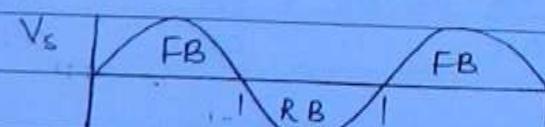

$$\omega t_c = \pi$$

$$t_c = \frac{\pi}{\omega} \text{ secs}$$

2

Forced commutation -

DC supply will not support the commutation process. We need a separate forced commutation circuit to turn off the SCR.

eg choppers
inverters



step up cycloconverter

(27)

a) Class A commutation circuits -

RLC should satisfy underdamped condition

$$R^2 L^2 < 4L/C$$

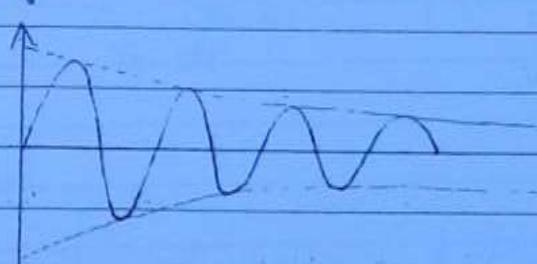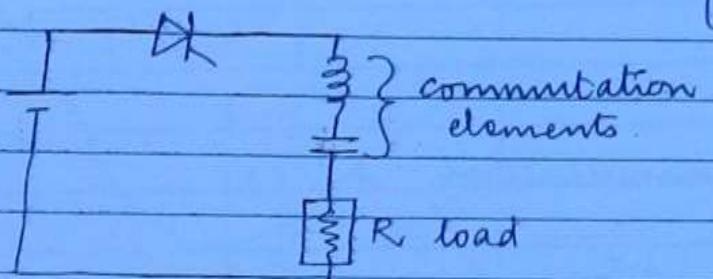


$$I = \frac{V_0}{\omega_n L} e^{-\delta t} \sin \omega_n t$$

$$\delta = \frac{R}{2L}$$

$$\omega_n = \sqrt{\frac{1 - R^2}{LC}} \frac{1}{4L^2}$$

↓ ringing frequency

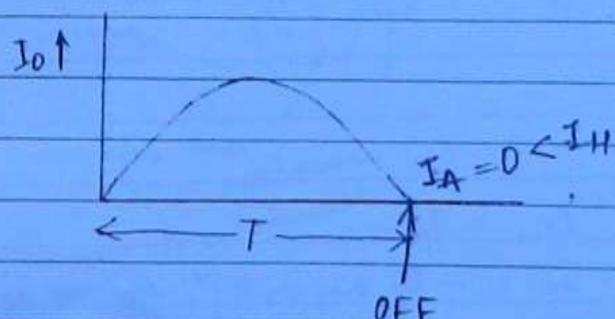

$$\omega_n t = \pi$$

$$t = \frac{\pi}{\omega_n}$$


conduction time of
thyristor = $\frac{\pi}{\omega_n}$ sec.

(28)


Load commutation -

If the load elements support the commutation process then it is known as load commutation.

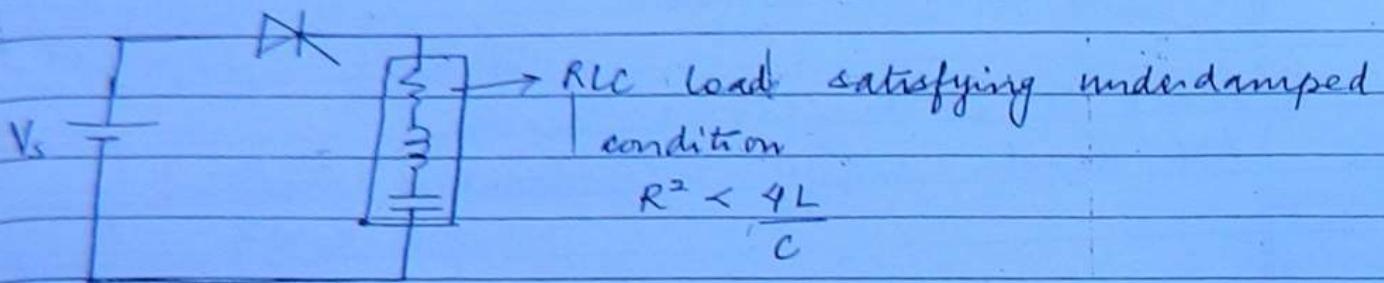eg if load is RLC load satisfying underdamped condition as shown in figure.



Class B - Current Commutation -

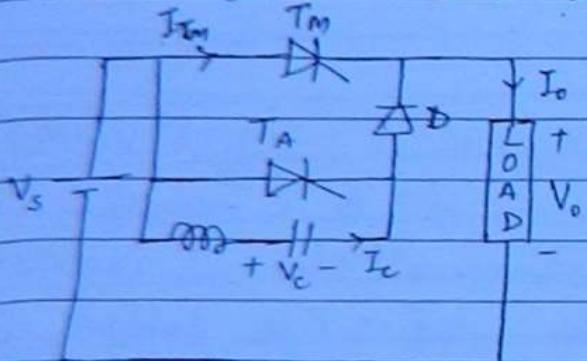

$$\text{Assume} \rightarrow V_o(t=0) = V_s$$

$\rightarrow I_o = \text{constant}$

(highly inductive load)


$\rightarrow T_M \rightarrow \text{ON } (t < 0)$

① Mode

$T_A \rightarrow \text{ON } (t=0)$

$$I_{T_M} = I_o$$
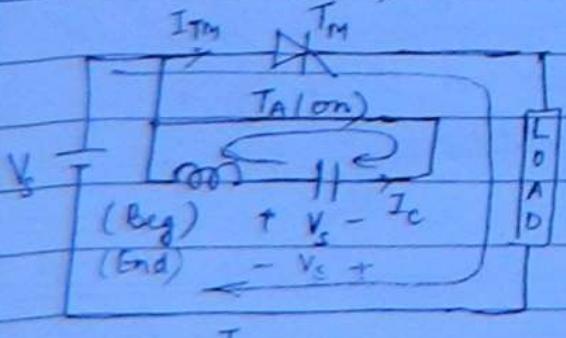
$$I_c = -I_p \sin \omega t \quad \left[\begin{array}{l} \text{"di" is opp to} \\ \text{reference } I_c \end{array} \right]$$





$$V_c = V_s \cos \omega t$$

$$\text{End} \rightarrow V_c = -V_s$$


$$I_o = 0$$

I_o

29

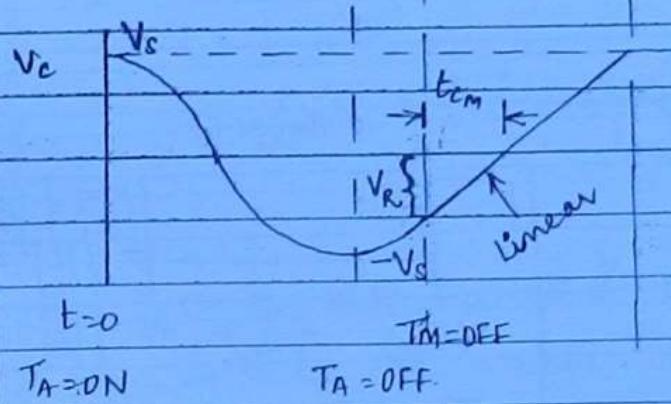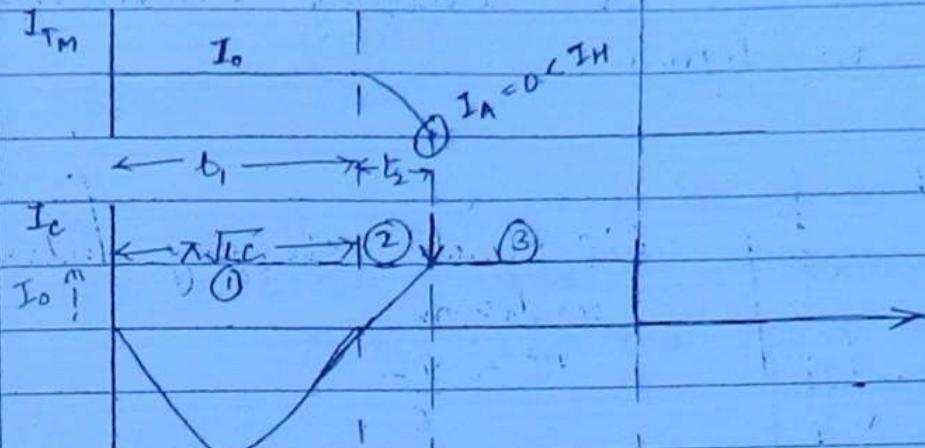

② MODE

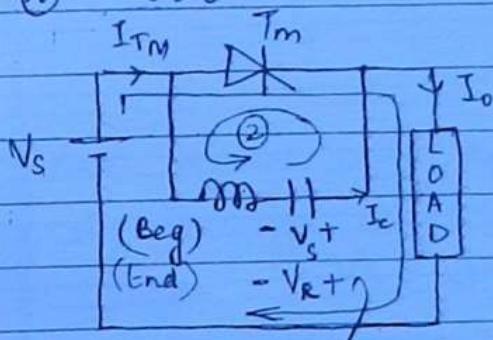

$$\downarrow I_{TM} = I_o - I_c \uparrow$$

GND \rightarrow when $I_c = I_o \quad I_{TM} = 0$
 $\therefore T_m \rightarrow OFF$

for this
also reference
is the initial
voltage V_c

$$I_p \sin \omega t_2 = I_o$$

$$\omega t_2 = \sin^{-1} \frac{I_o}{I_p}$$

$$t_2 = \sqrt{LC} \sin^{-1} \frac{I_o}{I_p}$$

V_C at the end of mode ②

$$V_C = V_S \cos(\pi + \omega_{L2} t)$$

$$V_C = -V_S \cos(\omega_{L2} t)$$

$$V_C = -V_S \cos\left[\sin^2 \frac{\theta_0}{I_p}\right]$$



(30)

At the end of mode ②

V_R is the reverse voltage of cap.

$$V_R = V_S \cos\left[\sin^2 \frac{\theta_0}{I_p}\right]$$

③ MODE

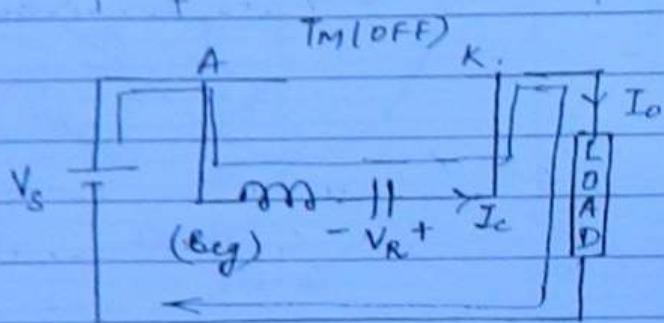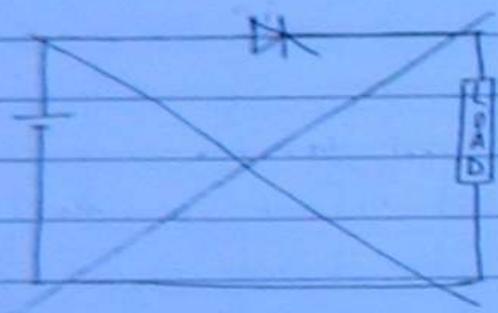

$$I_C = I_o$$

$$V_C = \frac{1}{C} \int i \, dt$$

$$V_C = \frac{I_o}{C} t$$

$$V_R = \frac{I_o}{C} t_{OFF}$$

$t_{OFF} = \frac{V_R C}{I_o}$

circuit turn off time
for main thyristor

$$(I_{Tm})_{peak} = I_0$$

$$(I_{Tn})_{peak} = V_s \int_L^C dt (I_p)$$

(31)

$$\text{conduction time of } T_n = \pi \sqrt{L C}$$

Min^m time required to turn OFF the main Thyristor after auxiliary Thyristor is switched ON.

$$t = \pi \sqrt{L C} \quad (\text{for low values of load current } I_0)$$

Max^m time required to turn OFF T_m

$$t = t_r + t_d$$

$$= \pi \sqrt{L C} + \sqrt{L C} \sin^{-1} \left(\frac{I_0}{I_p} \right)$$

from

If $I_0 > I_p$, commutation is not possible.

∴ $I_0 \leq I_p$ to make commutation possible.

$$t_{cm} = C V_R \\ I_0$$


Max reverse voltage applied across the T_m when it's in off state is V_R .

$$V_R = V_s \cos \left[\sin^{-1} \frac{I_0}{I_p} \right]$$

If diode is not present, there is no control on commutation.

in comm.
if diode
is not present

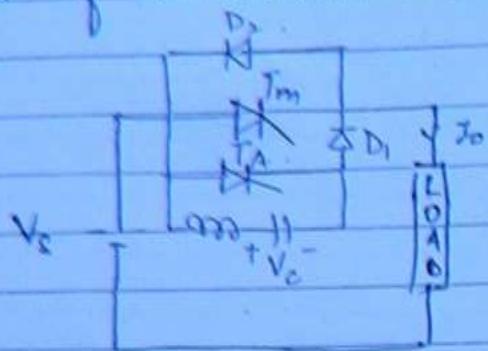Q. Check if commutation is possible. If possible, calculate the circuit turn-off time of T_M




At end of mode 1, reverses polarity of $+V_C -$ to $-V_C +$
 In mode 2, T_M is ON, D_1 reverses & biases D_2
 D_1 is JFB and D_2 is RB. so commutation is possible
 provided I_{D2} is $\leq I_{RB}$. The switch off becomes a normal class B.p.

so for snub resistances R_s we will take $R_s = \frac{V_c}{I_o}$

1st two modes pair same as previous case. i.e.,


Mode (3)

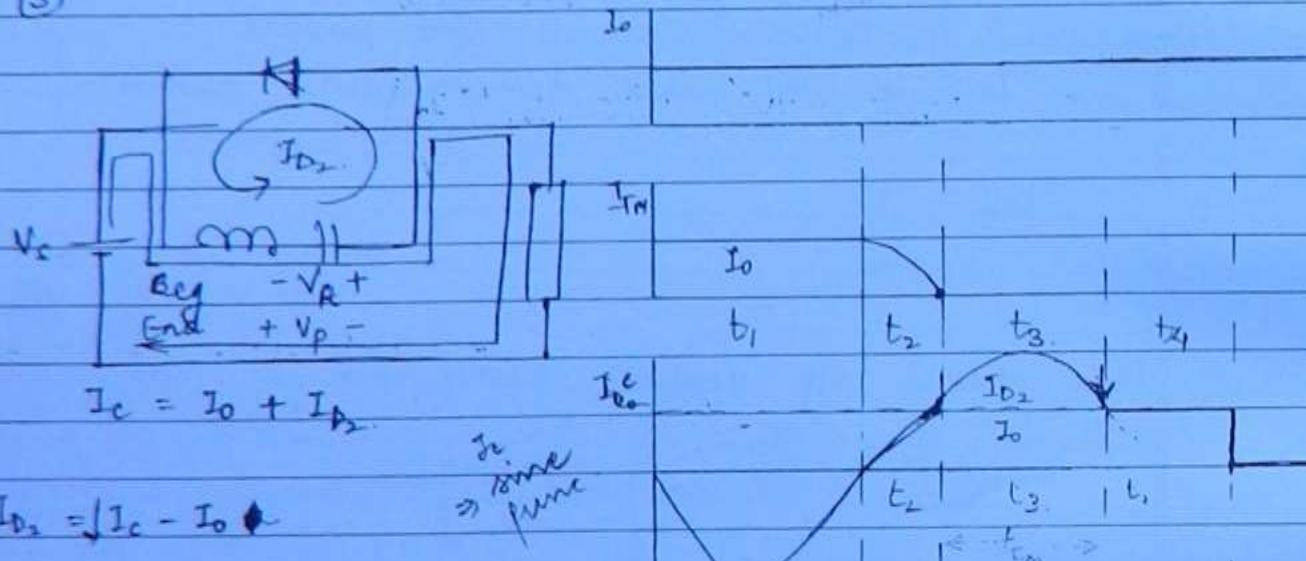


END \rightarrow when $I_c = I_o$

$$I_{D2} = 0$$

$D_2 = \text{OFF}$

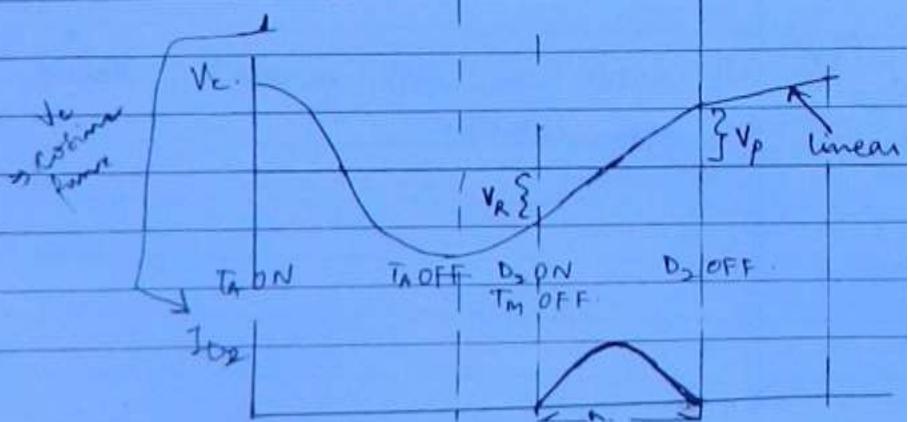

Mode (4)

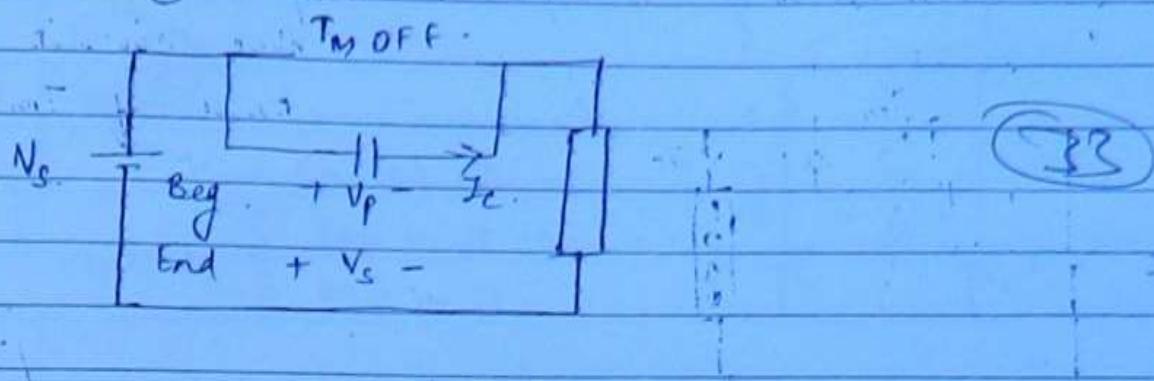

In mode (3): when D_2 is in the ON state
voltage drop of D_2 applies. But reverse voltage action.
The main thyristor's conduction time of D_2
is equal to switch turn-off time of T_M .


$$t_{cm} = t_3 = \pi\sqrt{LC} - 2t_s$$

$$t_{cm} = \pi\sqrt{LC} - 2\sqrt{LC} \sin^{-1}\left(\frac{I_o}{I_p}\right)$$

Applications -


This type of commutation technique is used in step down choppers. ∴ it's also known as current commutation chopper.

(c) Class C - Complementary Commutators

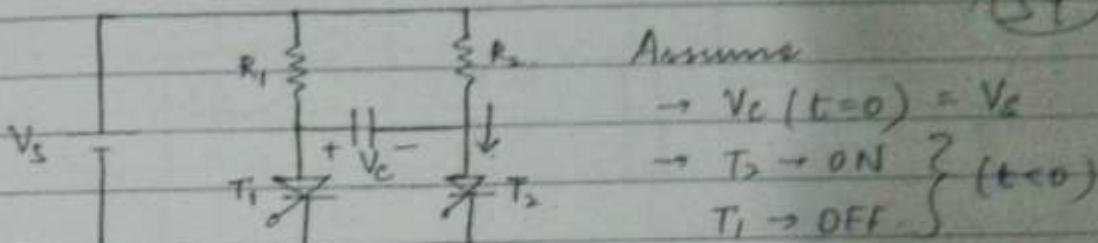

Mode ①

At $t=0$, $T_1 \rightarrow ON$

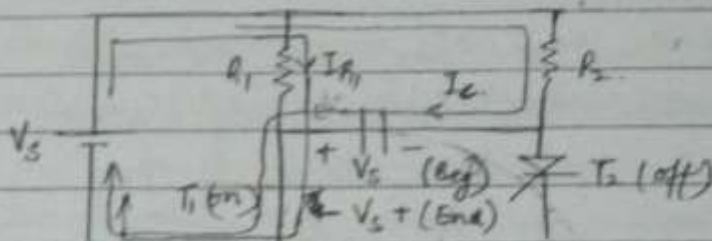

$$I_{T_1} = I_{R_1} + I_c \\ = \frac{V_s}{R_1} + K e^{-t/R_{ac}}$$

initial current

$$I_{T_1} = \frac{V_s}{R_1} + \frac{2V_c}{R_2} e^{-t/R_{ac}}$$

steady state current

transient current

$$V_c = \frac{1}{C} \int i_{ac} dt = \frac{1}{C} \int R_2 I_c e^{-t/R_{ac}} dt \\ = \frac{2}{C} V_s e^{-t/R_{ac}} - V_s \quad \text{by trial f. from form}$$

V_c graph

$$V_c = V_s (e^{-t/R_{ac}} - 1)$$




t_{c_0} = start time off time of T_2

$$V_c (e^{-t_{c_0}/R_{ac}} - 1) = 0$$

At $t=t_{c_0}$, $V_c = 0$

$$V_s [e^{-t_{c_0}/R_{ac}} - 1] = 0$$

$$t_{c_0} = R_{ac} \ln 2$$

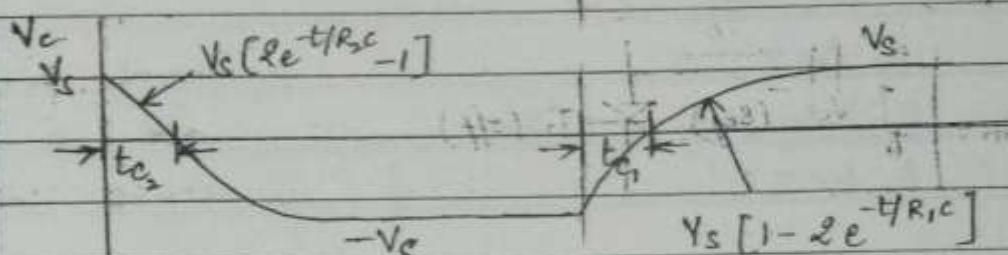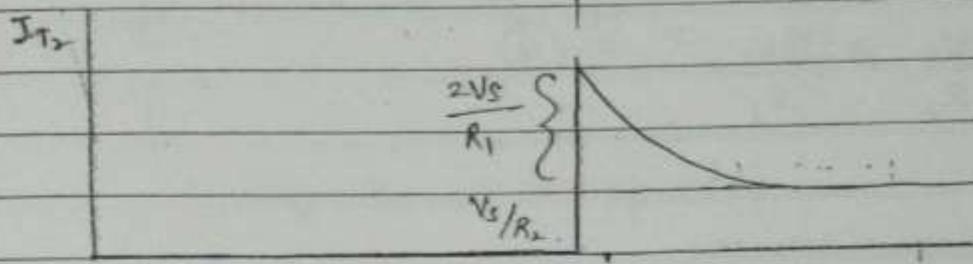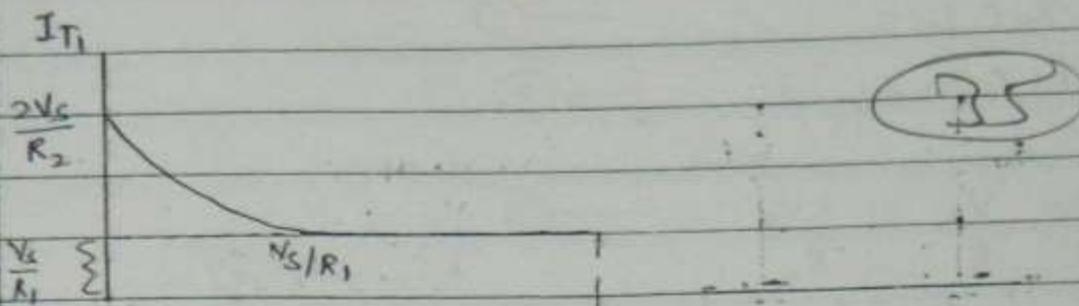


$t=0 \quad T_1 \rightarrow \text{ON}$ (t₁) $t=t_1 \quad T_2 \rightarrow \text{ON}$

$T_2 \rightarrow \text{OFF}$ (t₂) $t=t_2 \quad T_2 \rightarrow \text{ON}$

Mode ②

At $t=t_2$, $T_2 \rightarrow \text{ON}$

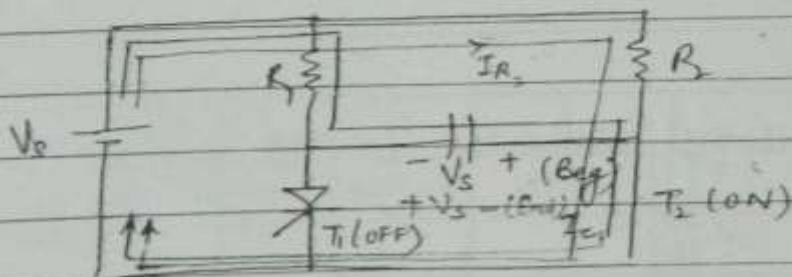

$$I_{T_2} = I_{R_2} + I_c$$

$$I_{T_2} = V_s + 2V_s e^{-t/R_{1,C}}$$

R_2 R_1
Steady state current transient current

$$t_{c_1} = R_1 C \ln 2$$

$$t_{C_2} = R_2 C \ln 2 \quad (1)$$

$$t_{C_1} = R_1 C \ln 2 \quad (2)$$

$$(I_{T_1})_{peak} = \frac{V_s}{R_1} + \frac{2V_s}{R_2} \quad (3)$$

$$(I_{T_2})_{peak} = \frac{V_s}{R_2} + \frac{2V_s}{R_1} \quad (4)$$

* Desired value of capacitance

from (1) $C = \frac{t_{C_2}}{R_2 \ln 2}$

$$C = \frac{(SF) t_{C_2}}{R_2 \ln 2} \quad (5)$$

from (2), $C = \frac{(SF) t_{C_1}}{R_1 \ln 2} \quad (6)$


From eq (5) & (6) we get 2 different values for capacitance We must consider the highest value of capacitance to make commutation possible.

Applications -

- Current source invert. inverter (CSI)
- Parallel Inverter

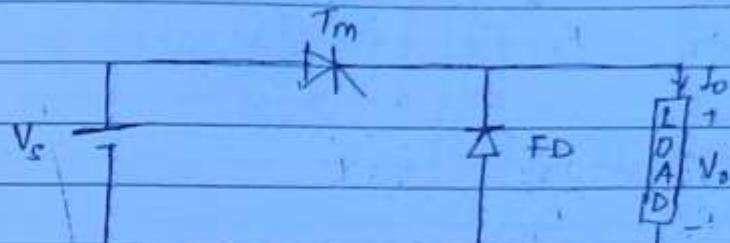(d) Class D - Voltage Commutation


It's used in step down choppers. \therefore it's also known as voltage commutation chopper.



37

Step down choppers


without commutation circuit

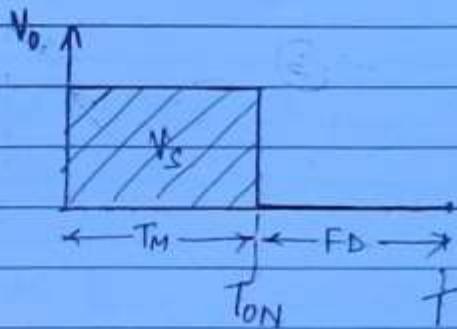

~~duty cycle~~ $\alpha = \frac{T_m}{T}$

$$V_o = \frac{\text{Area}}{\text{Time period}} = \frac{V_s T_m}{T} =$$



$$V_o = \alpha V_s$$

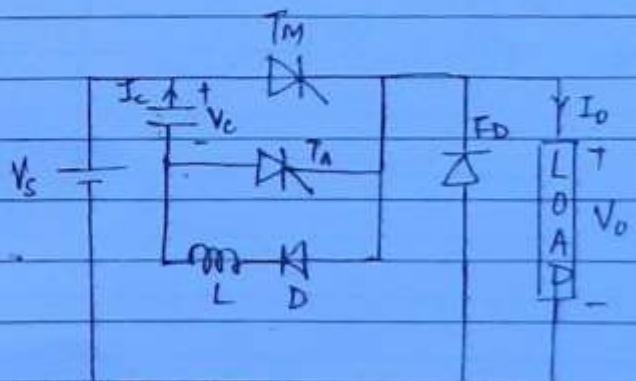

Assume

$\rightarrow V_c(t=0) = V_s$

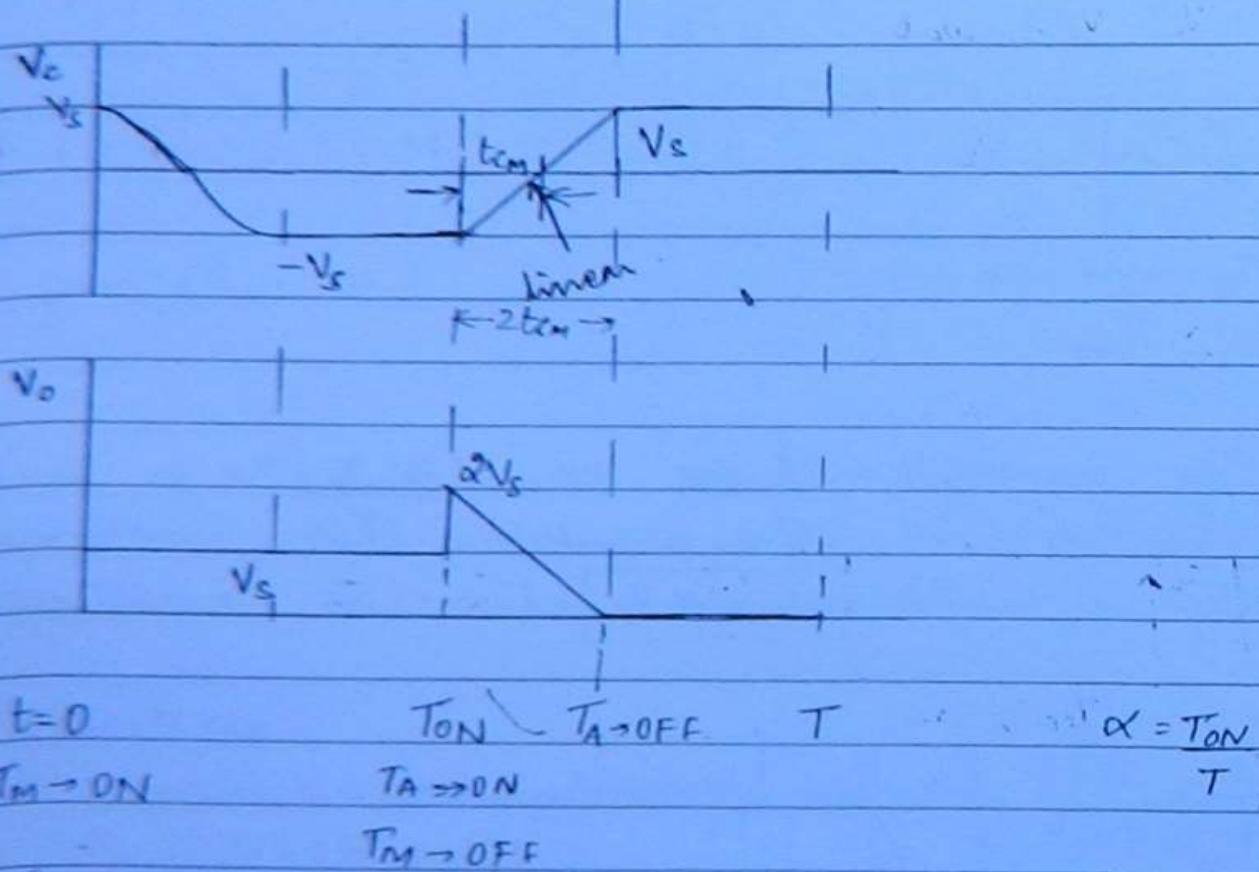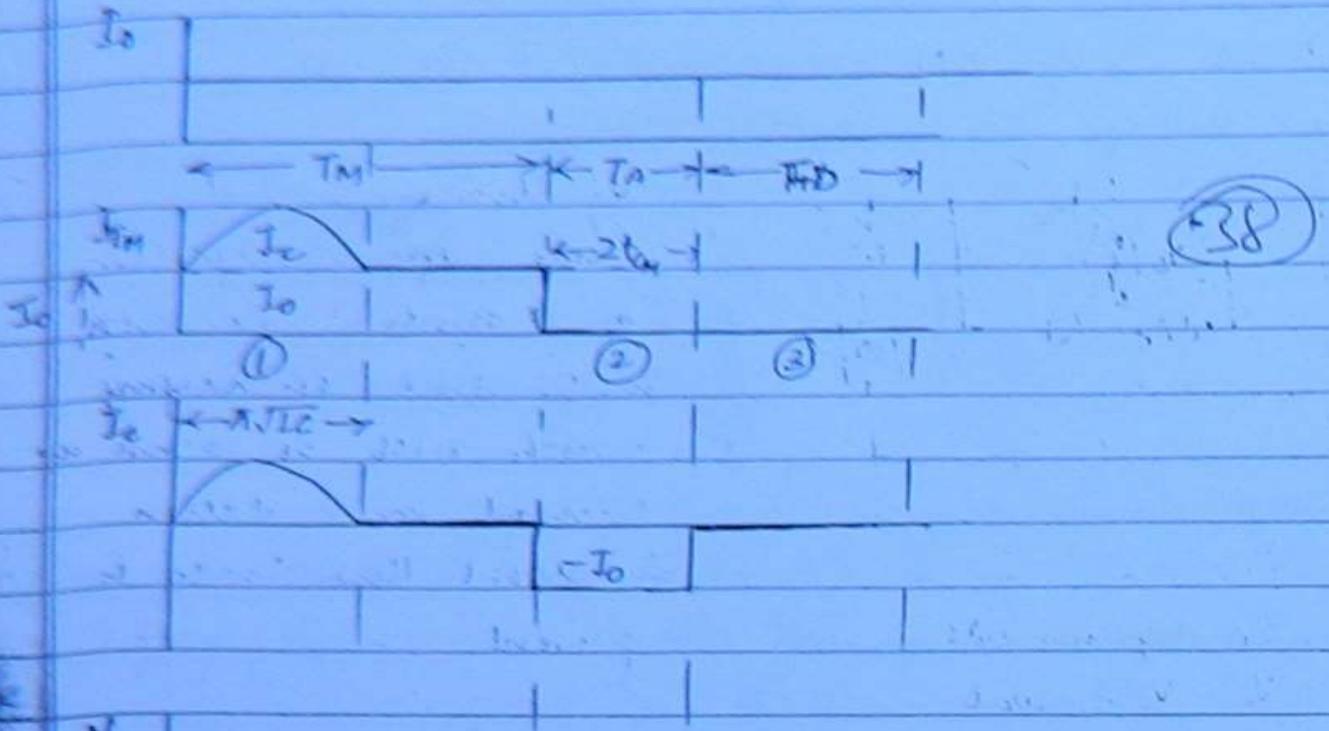
\rightarrow Consider highly inductive load so that load current $I_o = \text{constant}$



Mode ①

At $t=0$ $T_M \rightarrow ON$

③ q

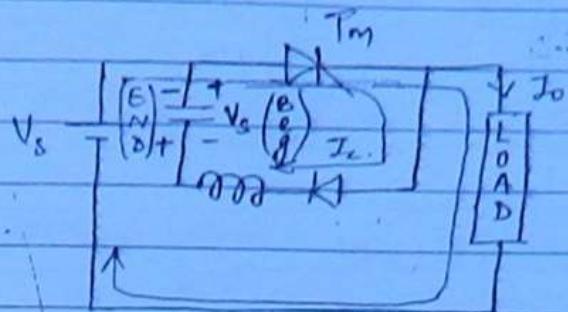

* If diode is not there, after completion of mode 1 capacitor will start discharging which will be same as current commutation.

To avoid this Diode is present.

$$I_{TM} = I_0 + I_c$$

$$I_c = I_p \sin \omega_0 t$$


$$V_c = V_s \cos \omega_0 t$$

$$Gnd \rightarrow V_c = -V_s$$

$$I_c = 0$$

Mode ②

At $t=T_{DN}$ $T_A \rightarrow ON$

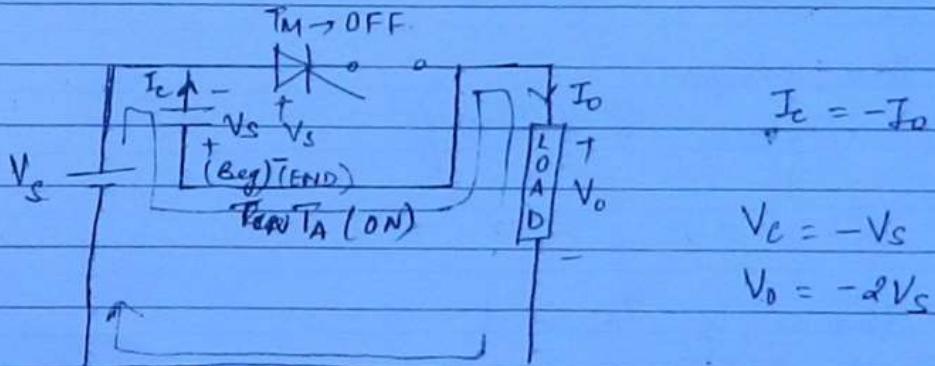

$$I_c = -I_0$$

$$V_c = -V_s$$

$$V_o = -2V_s$$


$$Gnd \rightarrow V_c = V_s$$

$$V_o = 0$$

$$I_c = 0$$

$$T_A \rightarrow OFF$$

Mode ③

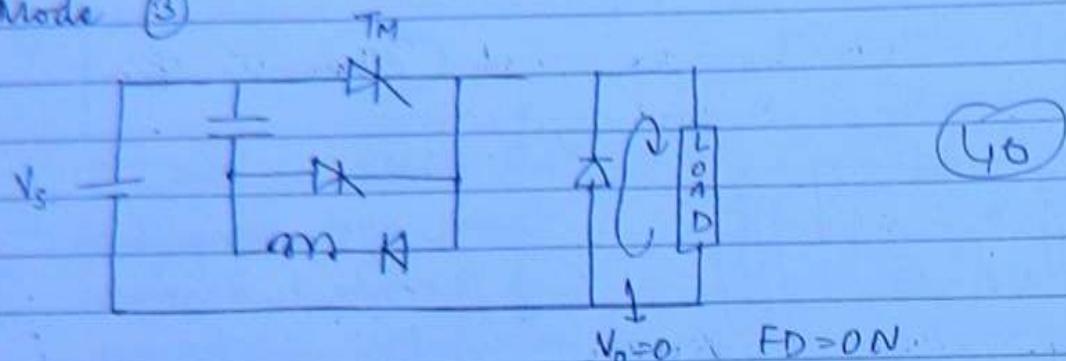

$$(I_{TM})_{peak} = I_o + V_s \sqrt{\frac{C}{L}}$$

$$(I_{TA})_{peak} = I_o$$

* Without completion of the 1st mode we cannot turn off the T_M i.e. the "min" turn ON time of the transistor is $\pi \sqrt{LC}$ secs

(this is because the polarities will not change before the completion of 1st mode)

* Min duty cycle of the chopper

$$\delta = \alpha = \frac{(T_{ON})_{min}}{T} = \pi \sqrt{LC} f$$

* Circuit turn off time of T_M

$$V_c = \frac{1}{C} \int i dt \Rightarrow V_c = \frac{I_o t}{C} \text{ (linear)}$$

$$V_s = \frac{I_o t_{cm}}{C} \Rightarrow t_{cm} = \frac{C V_s}{I_o}$$

* Conduction time of $T_A > \alpha t_{cm}$

* Commutation interval = time taken to disconnect the load from the source once T_M is off.
 $= \alpha t_{cm}$

* PIV of FD is αV_s

since it's RB by the load, (when it's off)
so max voltage at load is αV_s

• 41

* PIV of TM = V_s

* Average value of voltage

$$V_o = V_s T_{ON} + \frac{1}{T} \times 2t_{cm} \cdot \alpha V_s$$

T

$$V_o = V_s \left[\frac{T_{ON} + 2t_{cm}}{T} \right] = \frac{V_s (T_{ON})_{eff}}{T}$$

* Effective turn-on time of chopper


i.e. $(T_{ON})_{effective}$

$$T_{ON(effective)} = T_{ON} + 2t_{cm}$$

* Minimum possible average voltage of chopper
is

$$(V_o)_{min} = V_s \left[\frac{\pi \sqrt{LC} + 2t_{cm}}{T} \right]$$

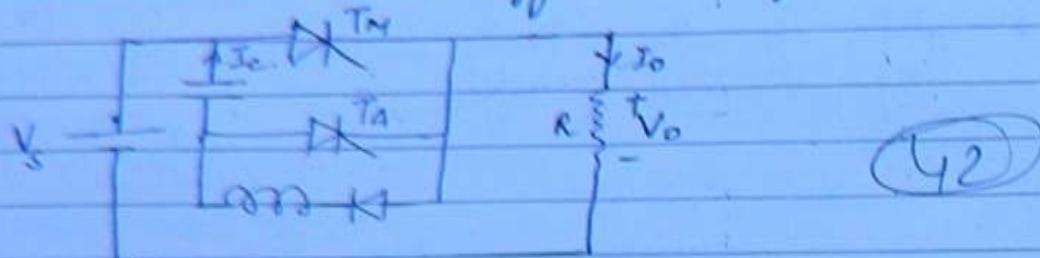Find the circuit turn off time of the main thyristor



Mode 1 is same as prev. case

Mode 2 \rightarrow is not same as $I_o \neq$ const due to R load.
(which forms RC ckt with cap C)

$$I_c = -I_o = -\frac{dV_o}{dt} e^{-t'/RC}$$

$$I_o = \frac{dV_o}{dt} e^{-t'/RC}$$

At $t' > 0$

$$I_o = \frac{dV_o}{dt}$$

If load current is exponentially reducing.



$$I_o = -\frac{dV_o}{dt} e^{-t'/RC}$$

amount current ↓
exponentially
 \uparrow
 V_o also.

$$V_o = V_s [1 - 2 e^{-t/RC}]$$

At $t = t_{\text{cm}}$ $V_o = 0$

$$t_{\text{cm}} = RC \ln 2$$

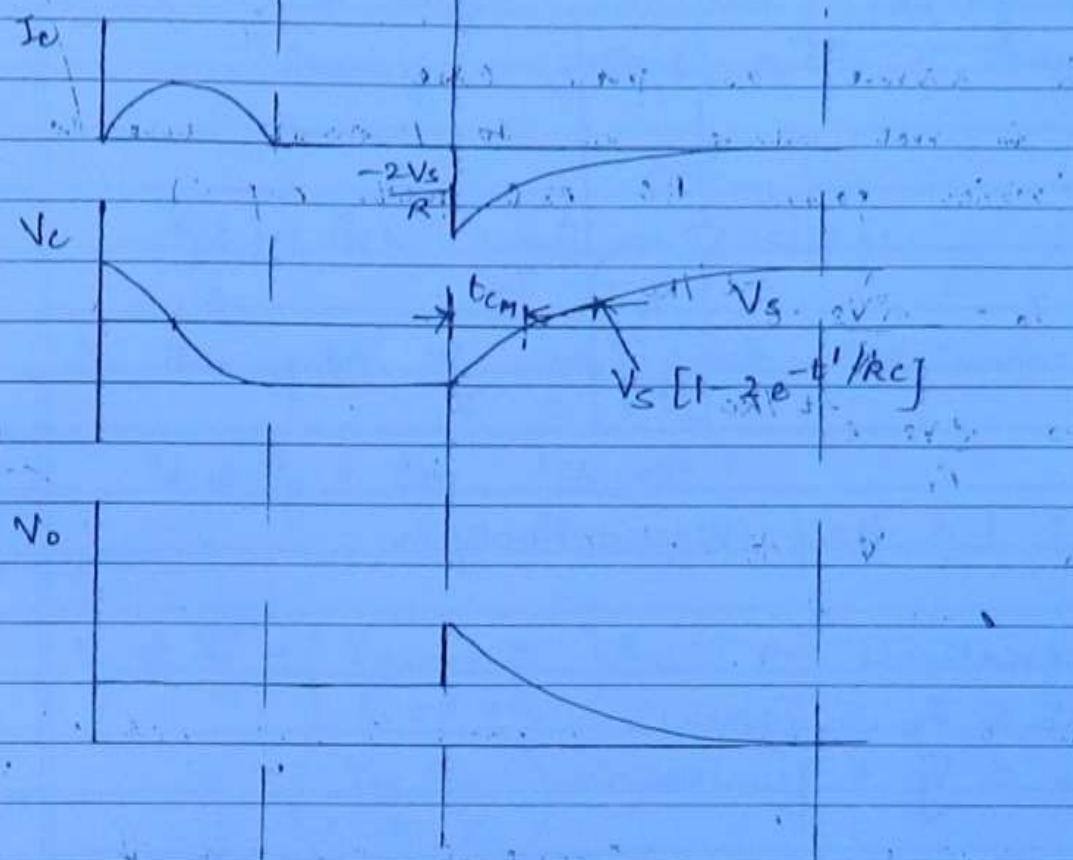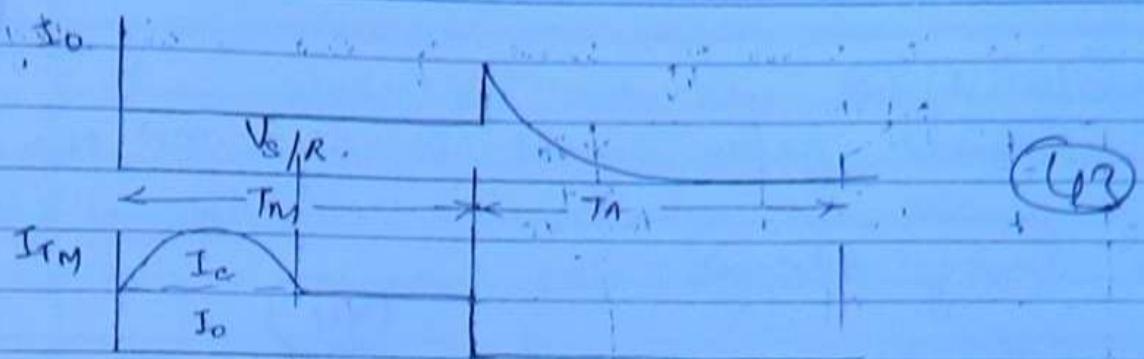


FIRING CIRCUITS

gives the required gate signal to turn ON the SCR.

1 Resistance Firing Circuit -

(Q4)

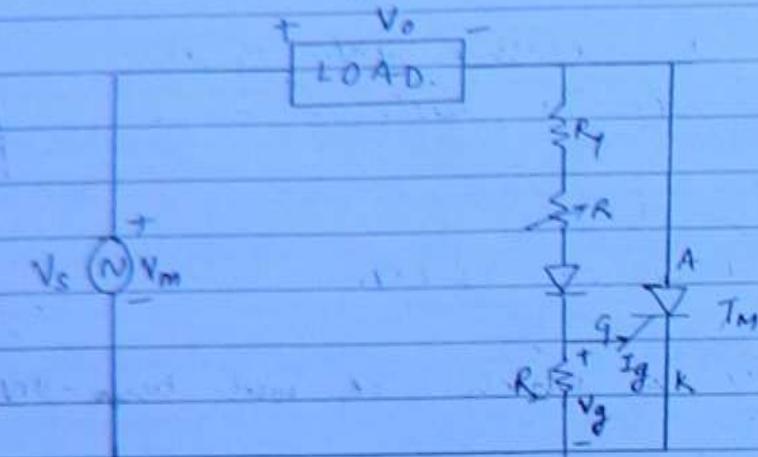

Main ckt : 1 ϕ Half Wave Rectifier

Gate specifications \rightarrow

$$I_{g\min} \leq I_g \leq I_{g\max}$$

$$V_{g\min} \leq V_g \leq V_{g\max}$$

$R_1 \rightarrow$ To limit gate current I_g within max^m value ($I_{g\max}$)

For worst condition.

$$\text{Maximum gate current} = \frac{V_m}{R_1} \leq I_{g\max}$$

$$\therefore R_1 \geq \frac{V_m}{I_{g\max}}$$

$$I_{g\max}$$

$R_2 \rightarrow$ To limit gate voltage V_g within max^m value ($V_{g\max}$)

For worst condition.

$$\text{Maximum gate voltage} = \left(\frac{V_m}{R_1 + R_2} \right) R_2 \leq V_{g\max}$$

From alone eqⁿ we can design value of R_2 .

Variable R → To change the tuning of gate signal ie α (P)

Diode → To avoid negative gate signal during negative cycle of source.

V_{gt} → Gate turn on voltage
↓

It's the gate V_g at which SCR will turn - ON

i.e. at $V_g = V_{gt}$ SCR → ON
($\omega t = \alpha$)

$$V_g = \left(\frac{V_m \sin \omega t}{R_1 + R + R_2} \right) R_2$$

$$V_g = \left(\frac{V_m R_2}{R_1 + R + R_2} \right) \sin \omega t$$

$V_g = V_{gm} \sin \omega t$ where $\downarrow V_{gm} = \frac{V_m R_2}{R_1 + R + R_2}$

$V_g = 0$
 $\downarrow T_{on} = ON$

At $V_g = V_{gt}$ SCR → ON

$$V_{gm} \sin \alpha = V_{gt}$$

$$\uparrow \alpha = \sin^{-1} \frac{V_{gt}}{V_{gm}}$$

$$\uparrow R \quad V_{gm} \downarrow \alpha \uparrow$$

for example

$$\text{I} \quad R = R_a \\ \alpha = \alpha_a$$

$$V_{gma} = \frac{V_m R_a}{R_1 + R_a + R_2}$$

$$V_{ga} = V_{gma} \sin \omega t$$


$$\text{II} \quad \text{fR} = R_b$$

$$\alpha = \alpha_b$$

$$V_{gmb} < V_{gma}$$

$$V_{gb} = V_{gmb} \sin \omega t$$

(4b)

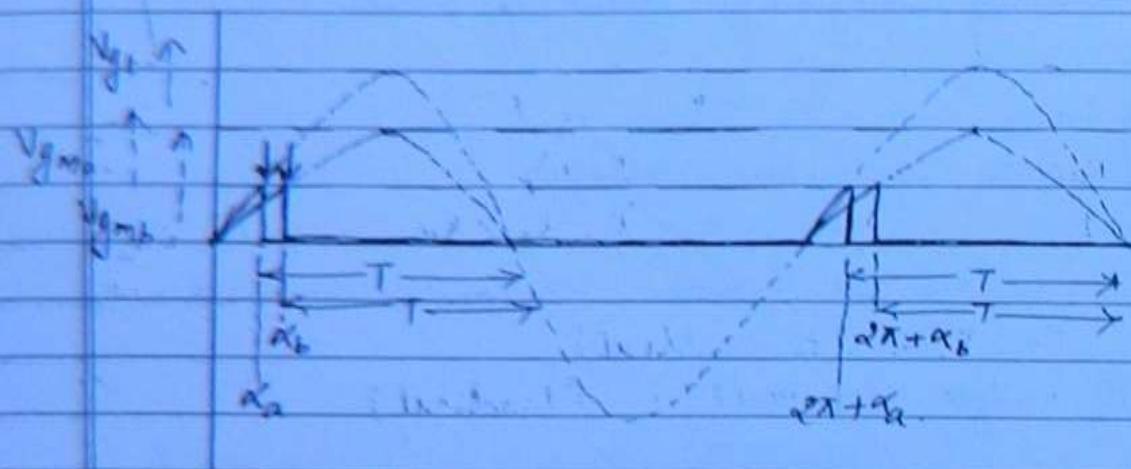


$$\text{fR } V_{gm} \downarrow \therefore \alpha \uparrow$$


limitation of R firing circuit.


The maximum firing angle is limited to 90° .

? RC firing circuit -

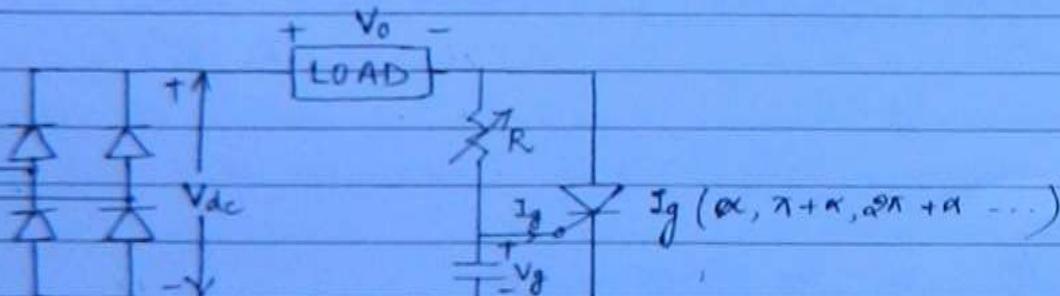

Main circuit: Full wave Rectifier

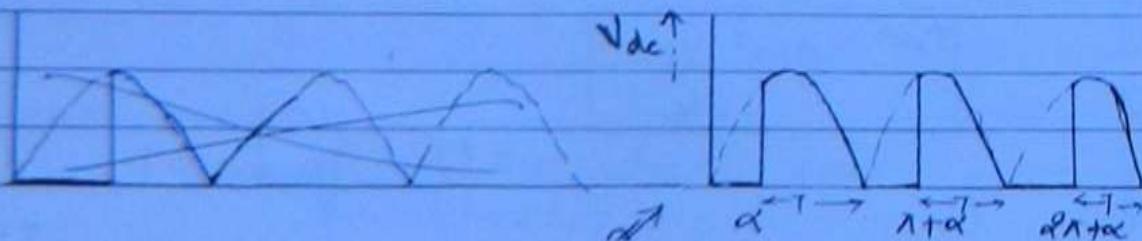

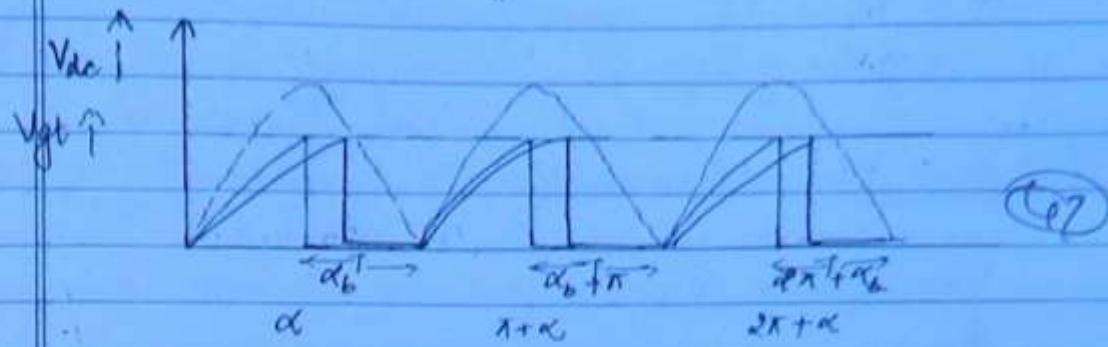

$$\text{I} \quad R = R_a$$

$$T = R_{ac}$$

$$V_{ga} \uparrow$$


$$\text{II} \quad V_{gb} T$$

$$T = R_{ec} C$$

$$R = R_b > R_a$$

$0 < \alpha < 180^\circ$ (Ideal)
 $(5 \text{ to } 7^\circ) \leq \alpha \leq (165 \text{ to } 175^\circ)$ (Practical)

3 VJT firing circuit -

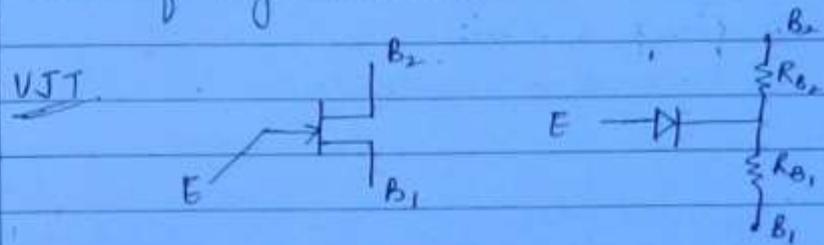


$B_1, B_2 \rightarrow$ Base terminals

$R_{B1}, R_{B2} \rightarrow$ Base resistances

$E \rightarrow$ Emitter terminal

When diode is ON
VJT ON

When diode is OFF
VJT OFF

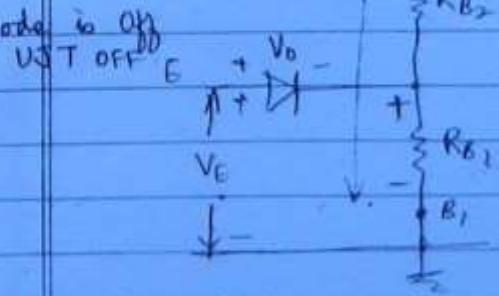

$$V_{RB_1} = \left(\frac{R_{B_1}}{R_{B_1} + R_{B_2}} \right) V_{BB}$$

$$V_{RB_1} = \eta V_{BB}$$

$$\eta = \frac{R_{B_1}}{R_{B_1} + R_{B_2}}$$

Intrinsic stand off ratio

$$V_E = V_{BE} + V_D \\ = \eta V_{BB} + V_D$$

$\uparrow V_E \Rightarrow V_p$

then $VJT \rightarrow ON$

(UJT)

(when $\uparrow V_E$ reaches)
 V_p $VJT \rightarrow ON$)

$$V_p = \eta V_{BB} + V_D$$

peak point voltage

OFF to ON state

* When UJT is switching from OFF to ON state
 V_E starts decreasing i.e. UJT exhibits negative resistance behaviour. This reduces emitter voltage.



$V_E \downarrow \Rightarrow V_V$

$\rightarrow UJT OFF$

(when $\downarrow V_E$ reaches)
 V_V $VJT \rightarrow OFF$)



Valley voltage

UJT working as Relaxation Oscillator -

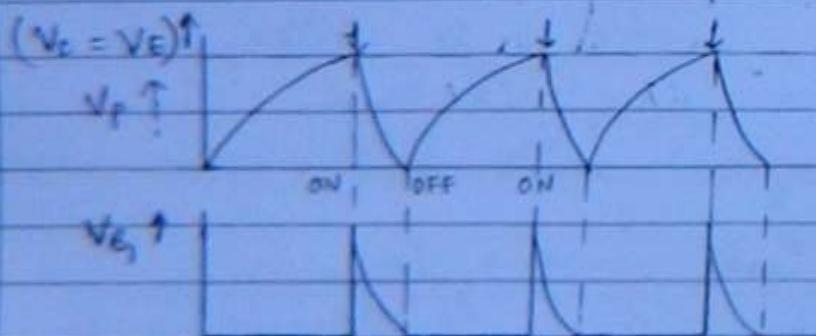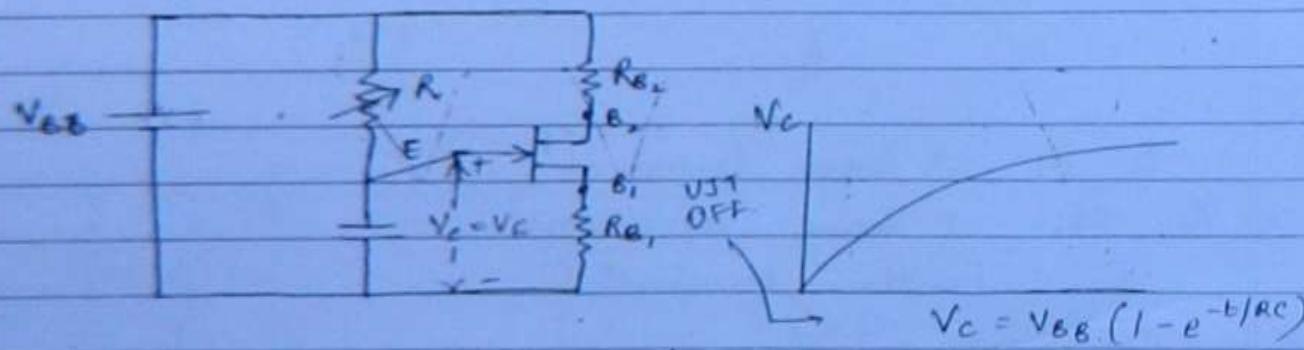


Synchronized UJT firing circuit - (Q9)

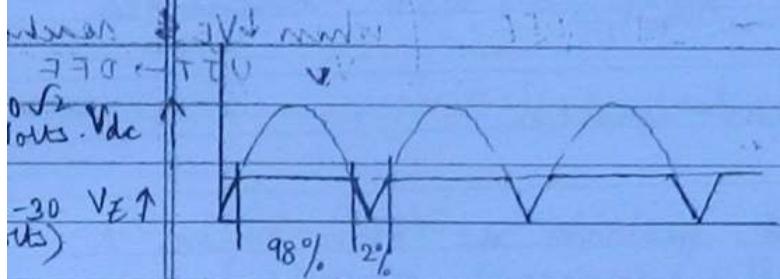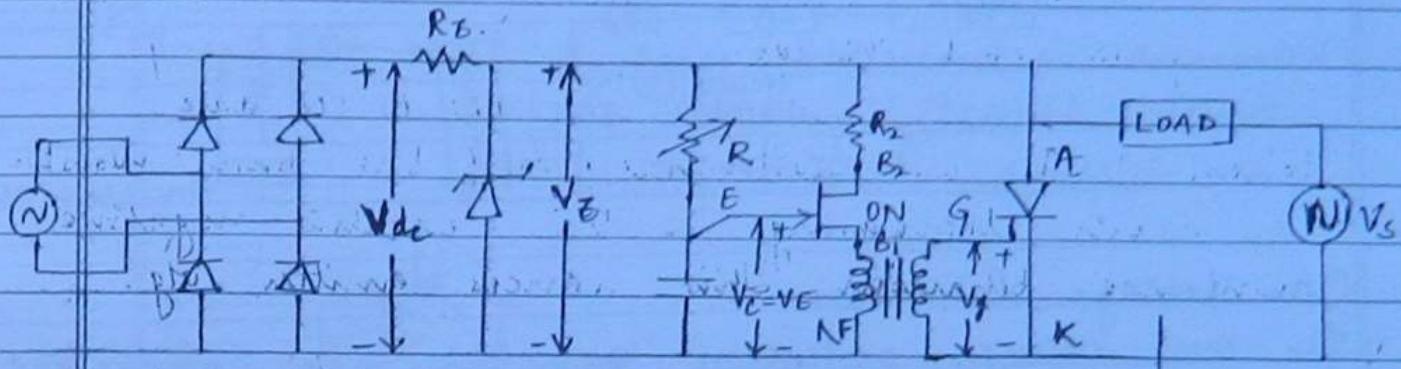We must synchronise the firing circuit with the main circuit in order to match the timing of 'gate pulse' in both the circuits. Here we must use same power supply in the main & firing circuits for the purpose of synchronization.



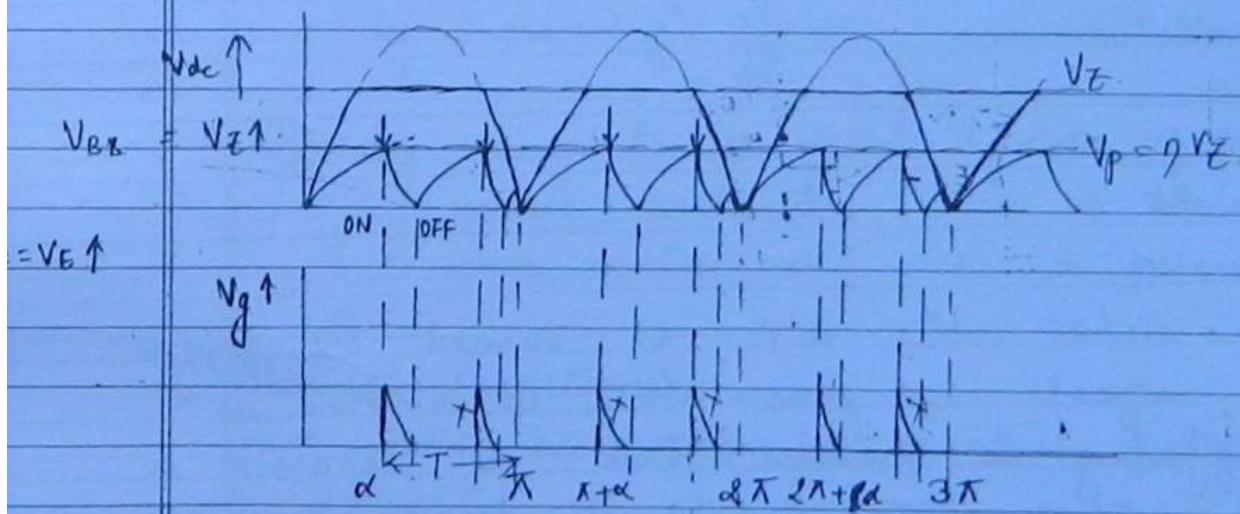main circuit
Half wave rectifier
 $I_g(\alpha, \alpha\pi + \alpha, \dots)$




PROTECTION OF THYRISTORS -

1 Over Current Protection -

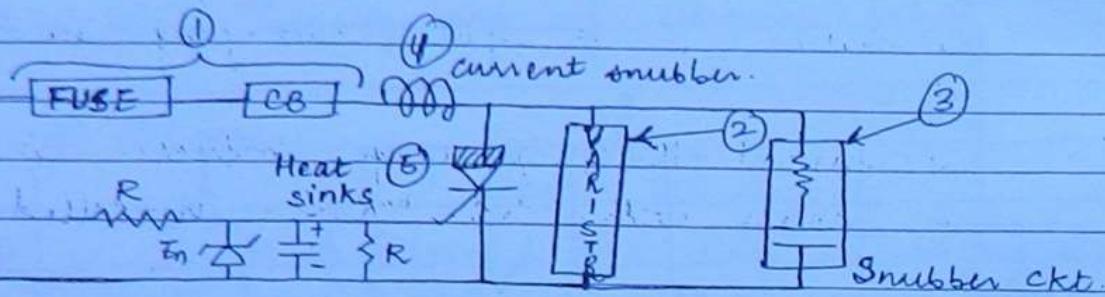(50)

For over current protection, we must connect fuse or circuit breaker in series with the SCR.



2 Over Voltage Protection -

For over voltage protection, varistors are connected across the SCR.

Varistors \rightarrow Non-linear resistor



All metal oxide varistors behave as non-linear R.

3 dv/dt Protection -

$$\uparrow I_c = g \frac{dV}{dt} \uparrow$$

A circuit diagram showing a capacitor C connected in parallel with the SCR. The top terminal of the capacitor is connected to the 'Anode' of the SCR, and the bottom terminal is connected to ground. The 'GATE' terminal (2) is connected to the top terminal of the capacitor. The 'In' terminal is connected to the 'Anode' of the SCR. The 'cathode' of the SCR is connected to ground.


At high dV/dt the SCR is turned ON before the gate signal is given. This is known as false triggering. To prevent this a capacitor is connected across SCR to limit dV/dt . A resistor is connected in series with the C, to reduce the discharge current magnitude. This is called Snubber circuit.

4 dV/dt Protection

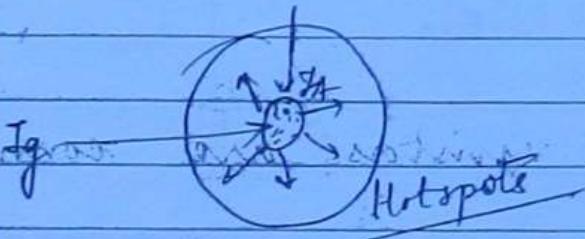(57)

When $dV/dt >$ (spread velocity of charge carriers) the charge accumulation increases cumulatively in a small conduction area & leads to the formation of hot spots. damaging the device.

To prevent this, a large inductor is connected in series with the SCR. This is called current snubber.



Initial conduction area ↑

* dV/dt capability of Thyristor can be improved by:




- i) → by increasing I_g or
- by increasing $\frac{dI_g}{dt}$

- ii) → by using Centre Gated Thyristor

(initial conduction area is increased when centre gated SCR is preferred)

5 Thermal Protection -

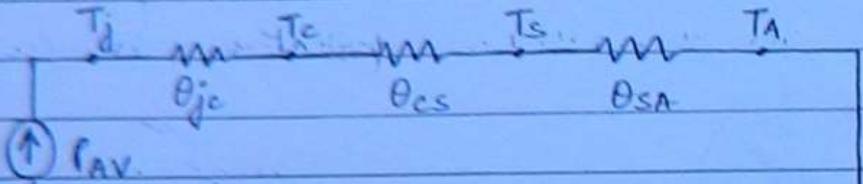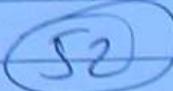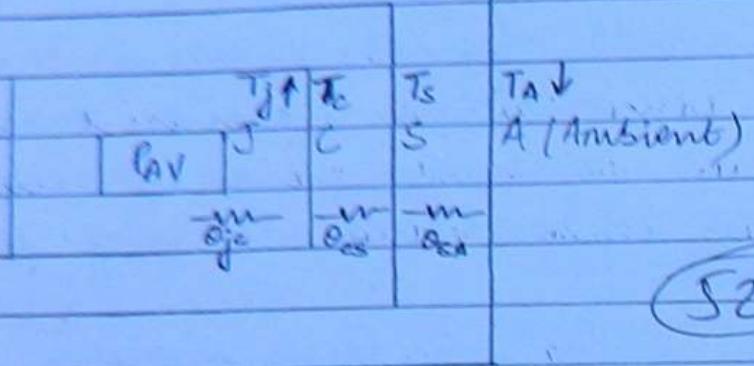Heat sinks are used for thermal protection.



$$\frac{P_{AV}}{\theta_{jc}} = \frac{T_j - T_{A1}}{\theta_{cs}} = \frac{T_A - T_S}{\theta_{SA}} = \frac{T_S - T_A}{\theta_{jc} + \theta_{cs}} = \frac{T_j - T_A}{\theta_{jc} + \theta_{cs} + \theta_{SA}}$$

$$\text{Rating of SCR} \propto \sqrt{P_{AV}} \propto \sqrt{\frac{T_j - T_A}{\theta_{ja}}}$$

* Rating of SCR is decided by cooling methods in the heat sink. Lesser the ambient temperature (T_A) higher the rating of the SCR.

6 Gate Protection. -

(S3)

a) Over Current Protection

A resistance is connected in series with the gate to limit the gate current within the permissible value.

b) Over Voltage Protection

Zener diode is connected across gate cathode terminals for overvoltage protection in the gate.

c) Protection against noise signals -

Noise is an unwanted signal passing through the gate terminal. It will false turn ON the SCR.

To prevent it, can connect a parallel RC across gate cathode terminals, to protect the SCR against noise signals.

CWB chapter 1

$$Q1 (b) \quad T_j = 125^\circ C$$

$$T_s = 70^\circ$$

$$\theta_{jc} = 0.16$$

$$\theta_{cs} = 0.08$$

$$P_{AV_1} = \frac{T_j - T_s}{\theta_{jc} + \theta_{cs}} = \frac{125 - 70}{0.16 + 0.08} = 289.167 \text{ W}$$


$$P_{AV_1} = \frac{125 - 60}{0.16 + 0.08} = 270.83 \text{ W}$$

$$\% \text{ Increase in Rating of SCR} = \frac{\sqrt{P_{AV_2}} - \sqrt{P_{AV_1}}}{\sqrt{P_{AV_1}}} \times 100$$

$$= \frac{\sqrt{270.83} - \sqrt{229.16}}{\sqrt{229.16}} \times 100$$

$$= 8.7\%$$

(54)

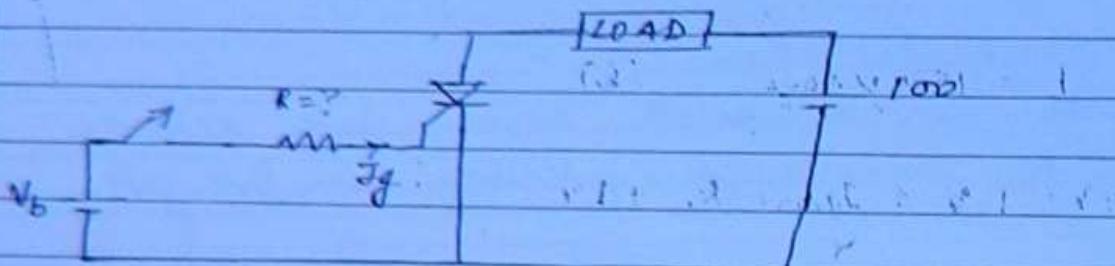

$$V_b = 12 \pm 4$$

$$I_g \text{ min} = 100 \text{ mA}$$

In worst condition


$$\text{Minimum possible } I_g = \frac{12 - 4}{R}$$

$$\frac{12 - 4}{R} > 10 \text{ mA}$$

$$R \leq 800 \Omega \quad (\text{d})$$

$$C = \frac{SF \times t_g}{R \ln 2} = \frac{2 \times 50 \times 10^{-6}}{50 \times \ln 2} = 2.88 \mu F \quad (\text{a})$$
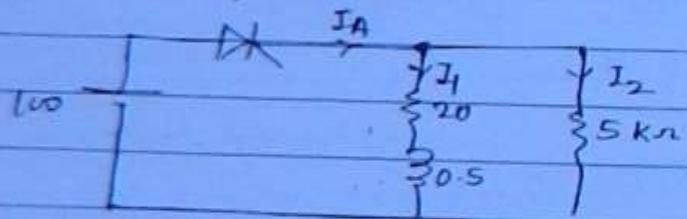
$$T_{ON} = 5 \mu \text{sec} \quad I_L = 50 \text{ mA} \quad I_H = 40 \text{ mA}$$



$$I_A = I_1 + I_2$$

$$= \frac{V_s}{R_1} (1 - e^{-t/T_1}) + \frac{V_s}{R_2}$$

$$T_1 = L_1 = \frac{0.5}{20} = \frac{1}{40}$$

$$I_A = \frac{100}{20} (1 - e^{-40t}) + 100 \frac{5 \times 10^3}{5 \times 10^3}$$

$$I_A = 5(1 - e^{-40t}) + (80 \times 10^{-3})$$

↓

thus $I_L = 5(1 - e^{-40t})$

(S)

$$50 \times 10^{-3} = 5(1 - e^{-40t}) + (80 \times 10^{-3})$$

$$\frac{30 \times 10^{-3}}{5} = 1 - e^{-40t}$$

$$t = 150 \mu\text{secs.} \quad (b)$$

Q3

$$9V = 1V + I_{gmax} R + 1V$$

$$I_{gmax} = 150 \text{ mA}$$

$$R \geq 46.67 \Omega$$

$$9V = 1V + I_{gmin} R + 1V$$

$$I_{gmin} = 100 \text{ mA}$$

$$R \leq 70 \Omega$$

$$46.6 \leq R \leq 70$$

Ans 47.2 (c)

Q8 Volt sec rating of pulse transformer

$$= 10V \times t_{gpw}$$

(gate pulse width)

$$t_{gpw} > t_{min}$$

$$I_A = \frac{\alpha \omega}{1} (1 - e^{-t/\tau})$$

$$\frac{L}{R} = 150 \times 10^{-3} = 0.15$$

$$I_A = \alpha \omega (1 - e^{-t/0.15})$$


$$I_A \rightarrow 150 \text{ mA} = \alpha \omega (1 - e^{-t/0.15})$$

$$t_{min} = 187 \mu\text{s}$$

$$t_{gpw} \geq 187 \mu\text{s}$$

Ans 187

-12 GTO (Gate Turn OFF Thyristor)

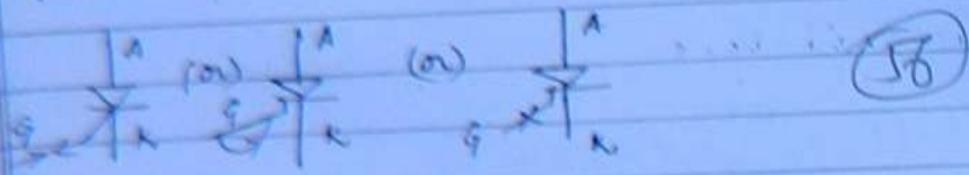

(56)


To turn ON $\rightarrow + I_A$ (when A gate voltage $> K$)

To turn OFF $\rightarrow - I_A$ (when $I_A \geq 20-25\% I_{MA}$ [if $I_{MA} > I_{MN}$])

The V-I characteristics of GTO are similar to conventional Thyristor (SCR) are similar.

Switching Characteristics of GTO - not work at

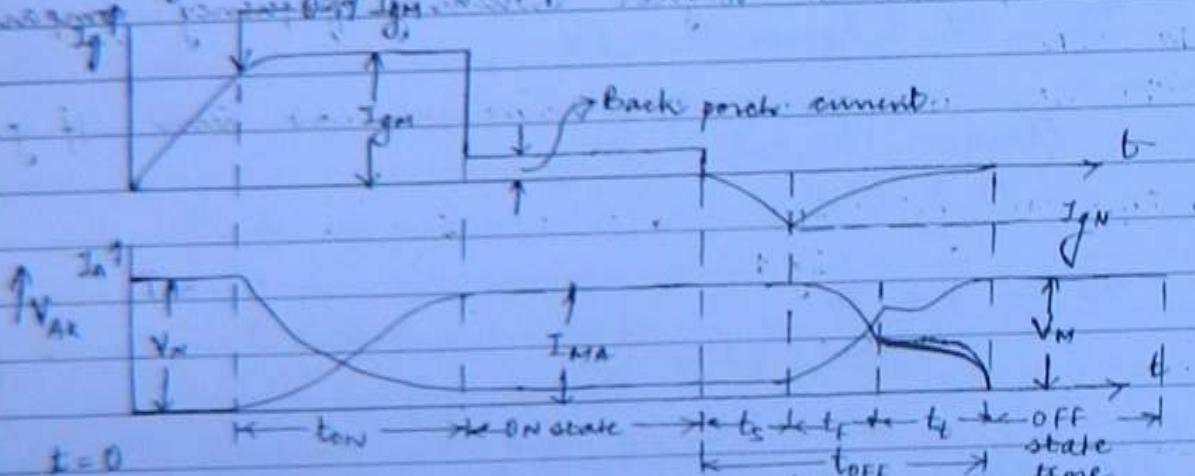ignition current I_{GN} because it is very small



turn ON char.

- During storage time the stored charge carriers are removed from the device

t_s = storage time

- During fall time rate of reduction of anode current is fast t_f = fall time

- * During tail time rate of reduction of anode current is slow.

t_t = tail time

(57)

Compare GTO with conventional Thyristor (SCR)

1. I_L & I_H are higher in GTO.
2. On state voltage drop is higher in GTO.
3. Gate signal requirement is higher in GTO.
4. Reverse voltage blocking capability is lesser than forward voltage blocking capability in GTO.
5. GTO is more efficient & compact compared to SCR.
6. GTO has fast turn-on \therefore faster turn-off
 \therefore it operates at higher switching frequency compared to SCR.
7. GTO has low turn-on gain & low turn-off gain.

$$\downarrow \text{turn-on gain} = I_{MA} \quad \downarrow \text{turn-off gain} = I_{MA}$$

$(+) Ig \uparrow$

$- Ig NT \uparrow$

Applications -

- * In inverters & choppers we can replace the SCR by using a GTO to avoid commutation circuit.


ASCR (Asymmetrical SCR)

It's a special diode with reduced reverse
voltage blocking capability.

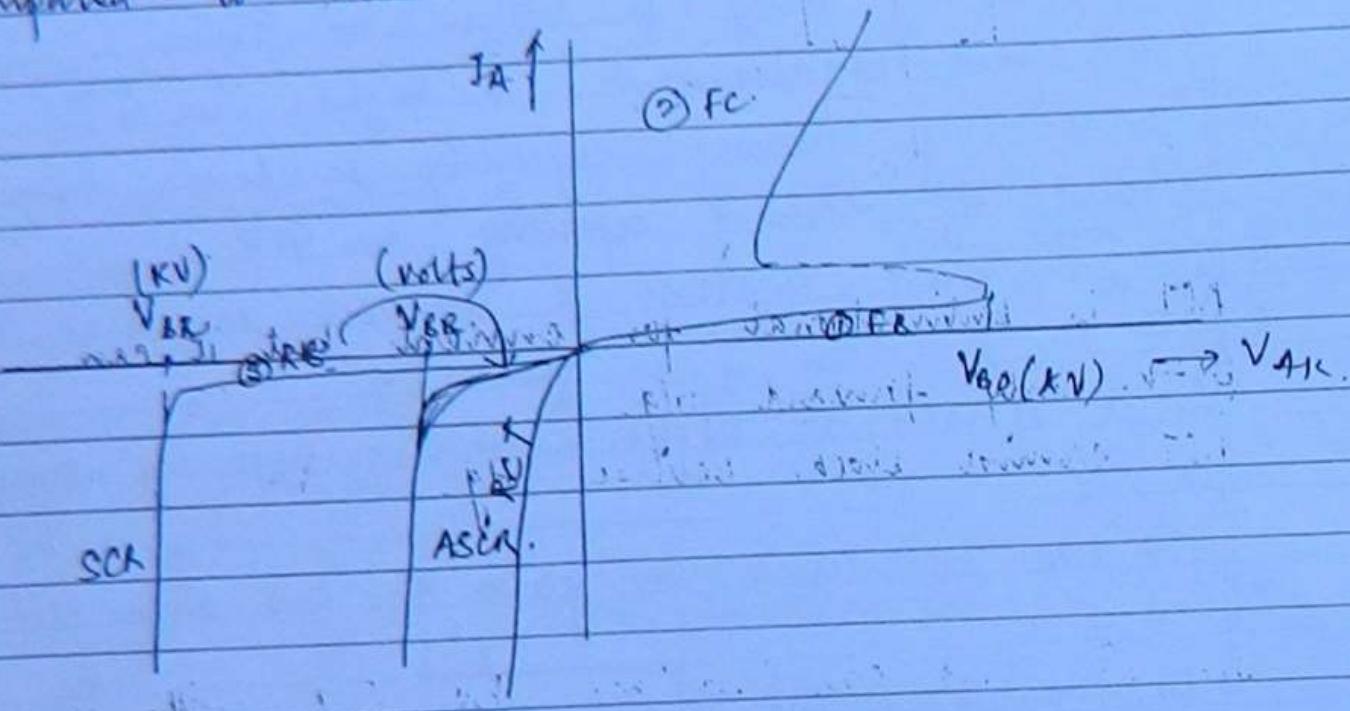(58)

ASCR has fast turn-on & turn-off times.

∴ it operates at higher switching frequency as
compared to SCR.




Applications -

In voltage source inverters (VSI) we can replace the
SCR by ASCR.

RCT (Reverse Conducting Thyristor)

An antiparallel diode is inbuilt across the SCR within the same structure.

(59)

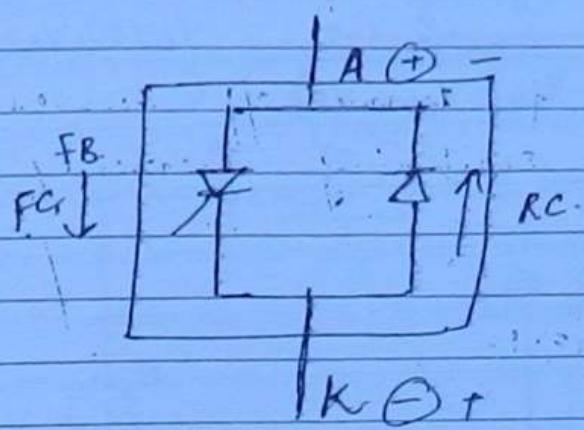


RCT is bidirectional for current but it can block (only) forward vlg.

RCT cannot block reverse vlg.

Applications -

In VSI, we can replace the SCR with an antiparallel diode by RCT.

TRIAC -

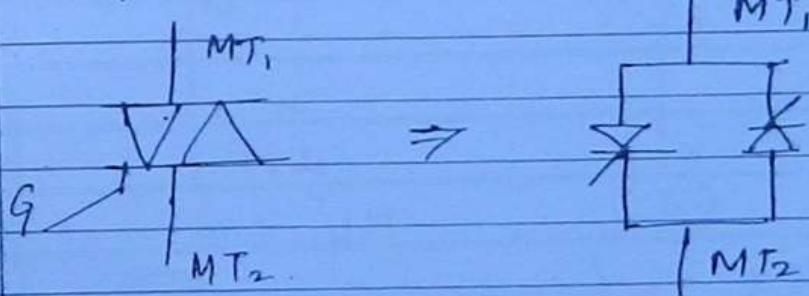

MT₁ +ve w.r.t MT₂.

(6)

JA ↑

② FC

[+y]

(0) V_{ER}

V_{ER}

③ KB

$J_g = 0$, J_{g1} , J_{g2}

-J_g

④ RC

MT₁ - ve w.r.t MT₂.

Applications -

used in AC v/f controllers as AC switch

Limitations of Triac -

In AC v/f controllers, it's used only for resistive loads and low inductive loads. It's not preferred for high inductive loads with high time constant.

DIAC

MT₁ (A) -



MT₂ (K) +

MT₁ +ve w.r.t MT₂

JA

② FC

V_{AK} → V_{BO}

V_{ER}

③ KB

Y_{AK} - Y_{ER}

① I_{FO}

V_{BO}

MT₁ - ve w.r.t MT₂.


④ RC

Applications -

Voice used in TRIAC firing circuit.


(61)

TRIAC firing circuit using DIAC :-

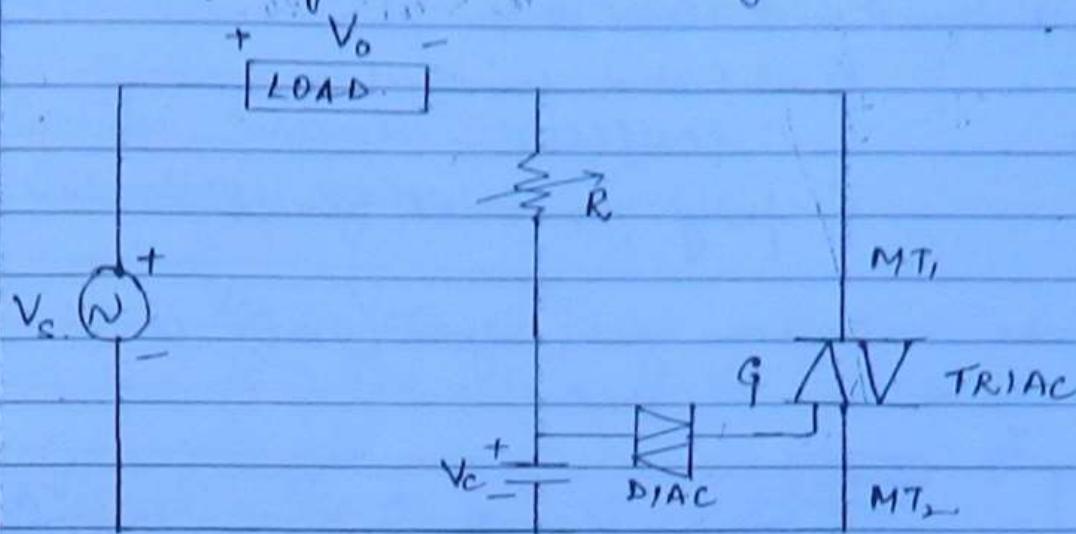

working principle and applications of TRIAC


main ckt \rightarrow AC vfg controller

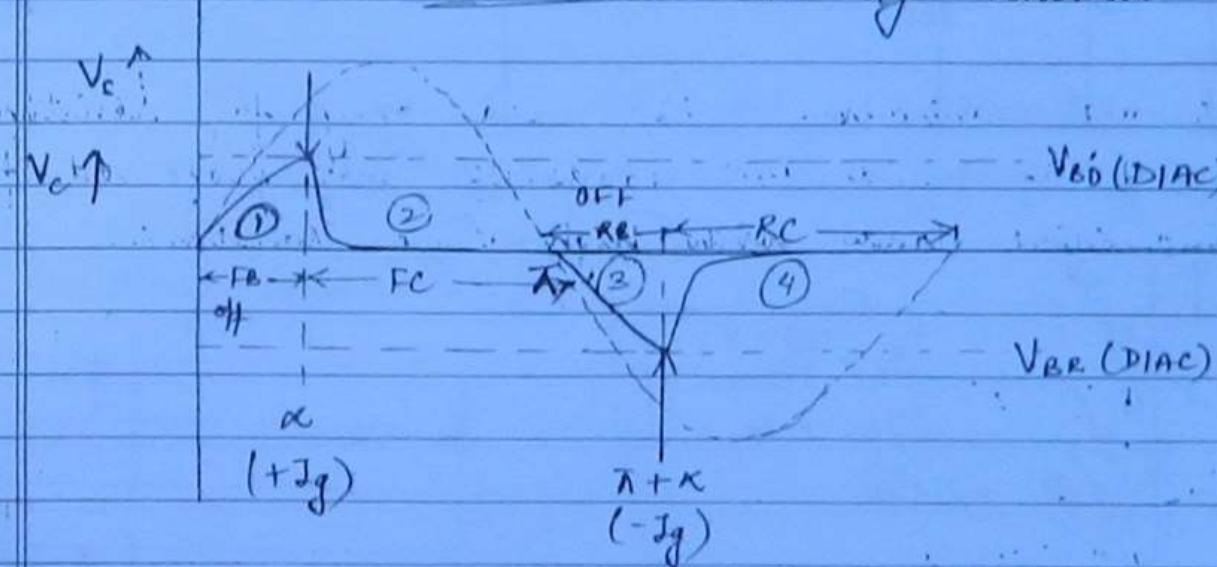

POWER TRANSISTORS -

(62)

POWERBJT -

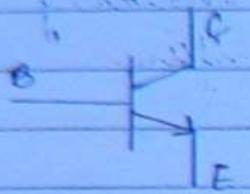



C, E → Major terminals

B → Control terminal.

(ON/OFF)

• fully controlled device

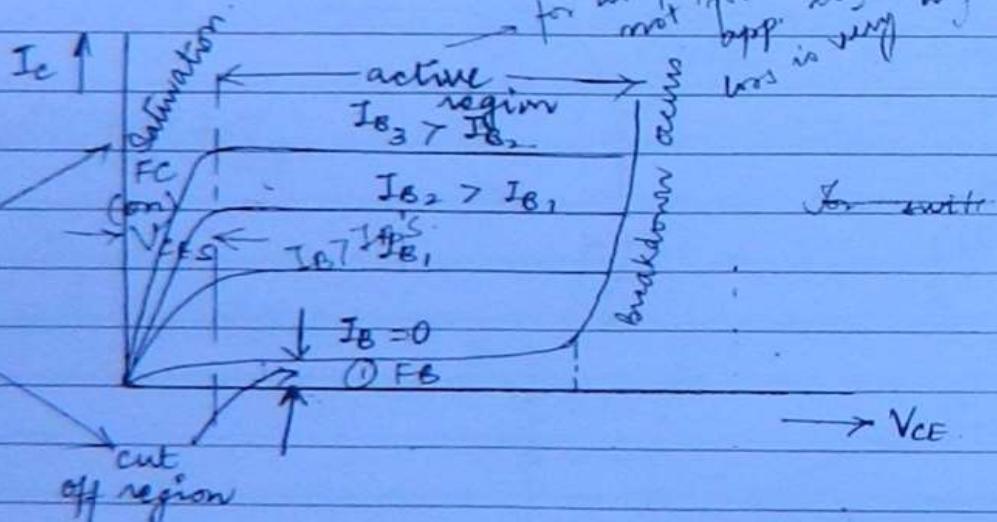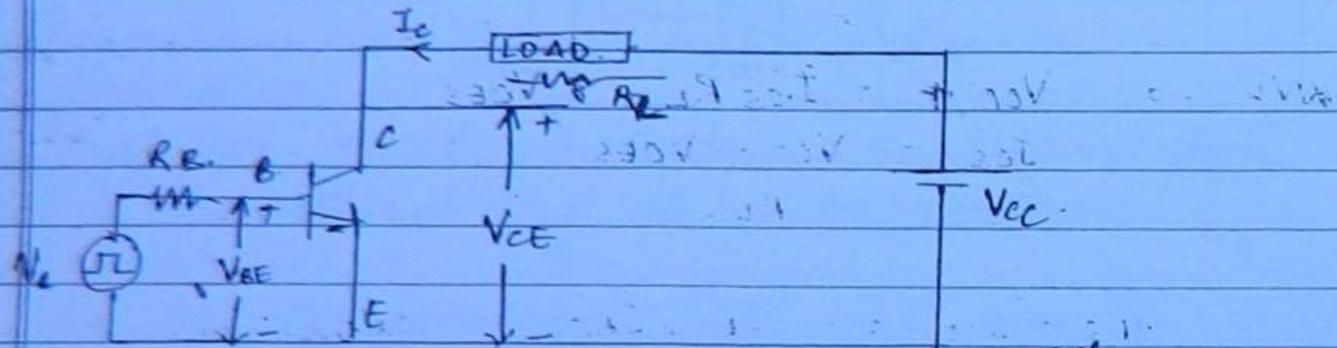- Here we require continuous gate signal (bias) to maintain the device in ON state.



$I_{BCS} \rightarrow \text{min}^m$ base current required to drive the transistor into saturation.

For switching applications in PE, the transistor should be operated in the cut-off region for OFF state & saturation region for ON state. Active region is not preferred for switching applications. It's only preferred in amplifiers.

Consider transistor in:

Saturation region:

$$V_{CE} = V_{CES}$$

$$I_C = I_{CS}$$


$$KVL \rightarrow V_{CC} = I_{CS} R_L + V_{CES}$$

$$I_{CS} = \frac{V_{CC} - V_{CES}}{R_L}$$

$$I_{BS} = I_{CS} \Rightarrow I_B \geq I_{BS} \rightarrow \text{saturation}$$

$$\beta \quad I_B \leq I_{BS} \rightarrow \text{active region}$$

Switching characteristics of BJT

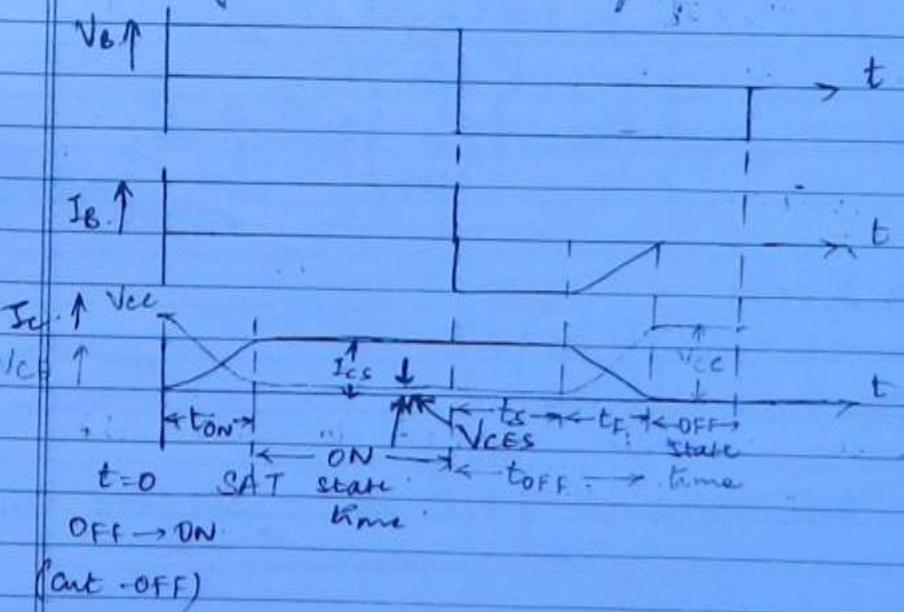


is during storage time, stored charges present in the base region is removed

(64)

$$\text{Instantaneous power loss during } t_{\text{ON}} \text{ process } P(t) = V_{CE}(t) I_c(t)$$

$$\text{Energy lost during turn-on process} = \int_0^{t_{\text{ON}}} P(t) dt.$$
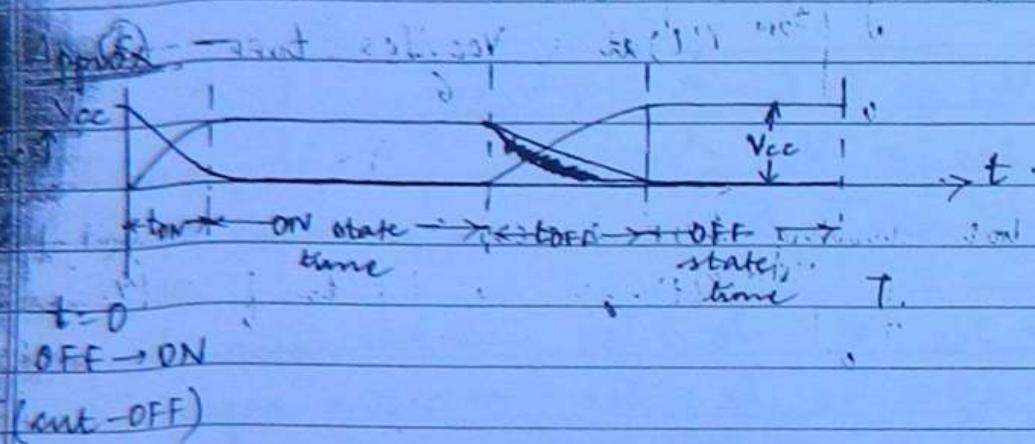
$$\text{Avg power lost during turn-on process} = \frac{1}{T_0} \int_0^{t_{\text{ON}}} P(t) dt.$$



t_{ON} process

$$I_c = \left(\frac{I_{cs}}{t_{\text{ON}}} \right) t$$

$$V_{CE} = \left(-\frac{V_{cc}}{t_{\text{ON}}} \right) t + V_{cc}$$

t_{OFF} process

$$I_c = \left(-\frac{I_{cs}}{t_{\text{OFF}}} \right) t + I_{cs}$$

$$V_{CE} = \left(\frac{V_{cc}}{t_{\text{OFF}}} \right) t$$

$$P(t) = V_{CE}(t) I_c(t)$$

$$= \left[\left(-\frac{V_{cc}}{t_{\text{ON}}} t \right) + V_{cc} \right] \left[\left(\frac{I_{cs}}{t_{\text{ON}}} t \right) \right]$$

$$\text{Energy lost during } t_{\text{ON}} \text{ process} = \int_0^{t_{\text{ON}}} P(t) dt = \frac{V_{cc} \cdot I_{cs} \cdot t_{\text{ON}}}{6} \quad (1)$$

$$\text{Avg power lost during turn process} = \frac{1}{T_0} \int_{0}^{t_{ON}} P(t) dt$$

(6.5)

$$= V_{CC} I_{CS} t_{ON} f \quad (2)$$

Instantaneous power loss during TOFF process

$$P(t) = V_{CE}(t) \cdot I_{CS}$$

$$= \left(\frac{V_{CC}}{t_{OFF}} t \right) \left(-I_{CS} t + I_{CS} \right)$$


Energy lost during TOFF process =


$$\int_{0}^{t_{ON}} P(t) dt = V_{CC} I_{CS} t_{OFF} f \quad (3)$$

Avg power lost during TOFF process =

$$\frac{1}{T_0} \int_{0}^{t_{ON}} P(t) dt = V_{CC} I_{CS} t_{OFF} f \quad (4)$$

2. POWER MOSFET -

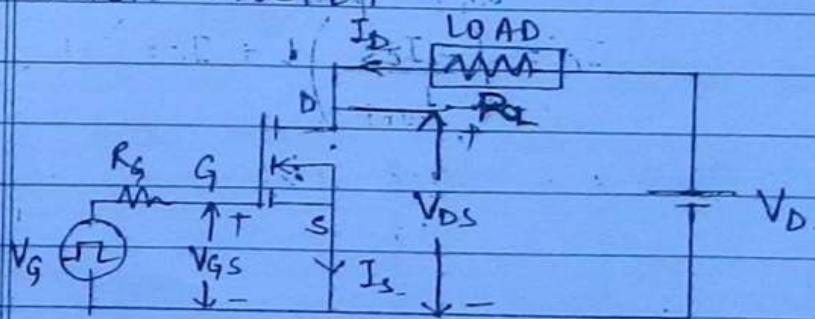

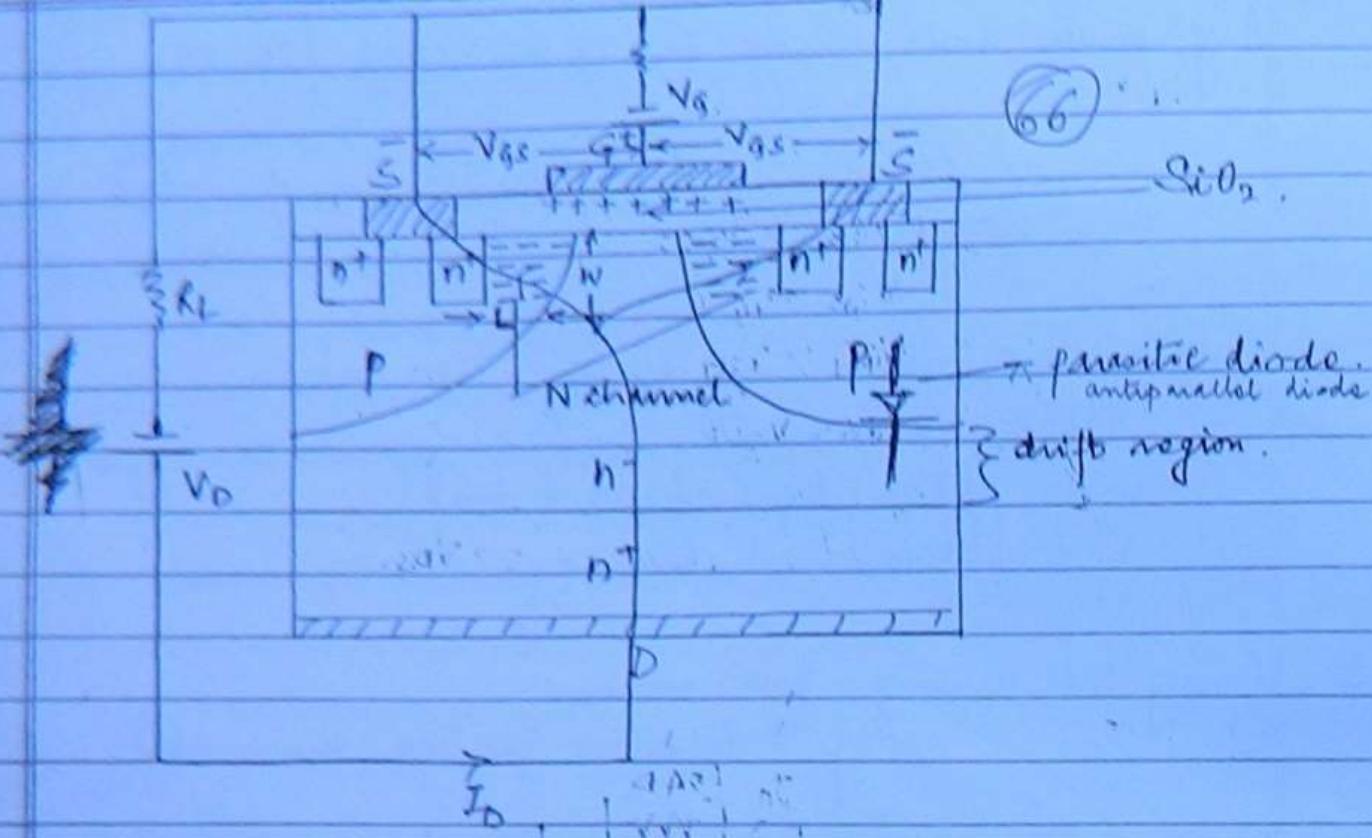

66
SiO₂

parasitic diode.
antiparallel diode
drift region.

Here since $V_{GS} > 0$,

the MOSFET starts conducting only after the formation of N-channel when positive gate signal is given. Here the conduction is only due to majority carriers, since there is no charge carriers f. i.e. the reverse recovery time delay is very much reduced. Hence Mosfet operates at high switching frequency.


$$V_{GS} \uparrow \therefore W \uparrow \therefore R_{on} \downarrow \therefore I_D \uparrow$$

$$V_{GS} \uparrow, I_D \uparrow$$


$$I_D \uparrow, I_C \uparrow$$

$$\text{channel resistance} \downarrow R_{on} \propto \frac{L}{W}$$


$$V_{GS} \uparrow, W \uparrow$$

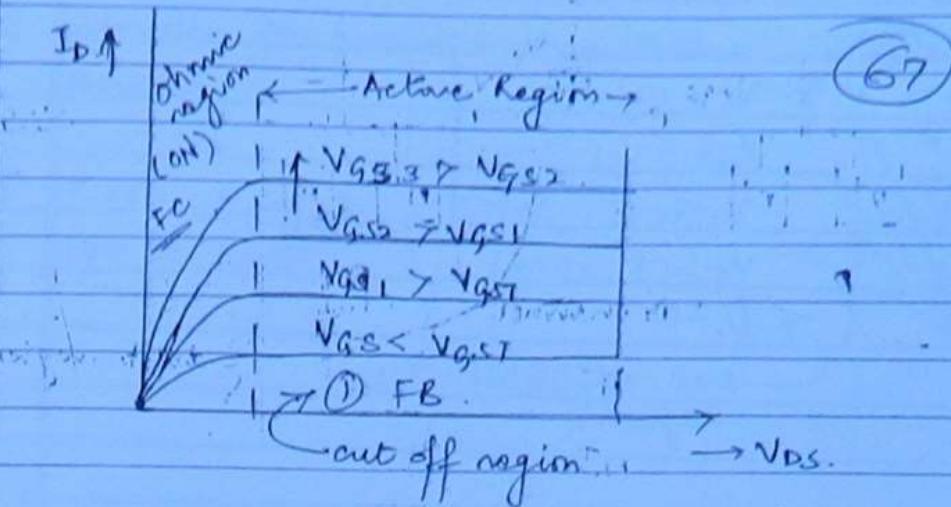


3 IGBT -

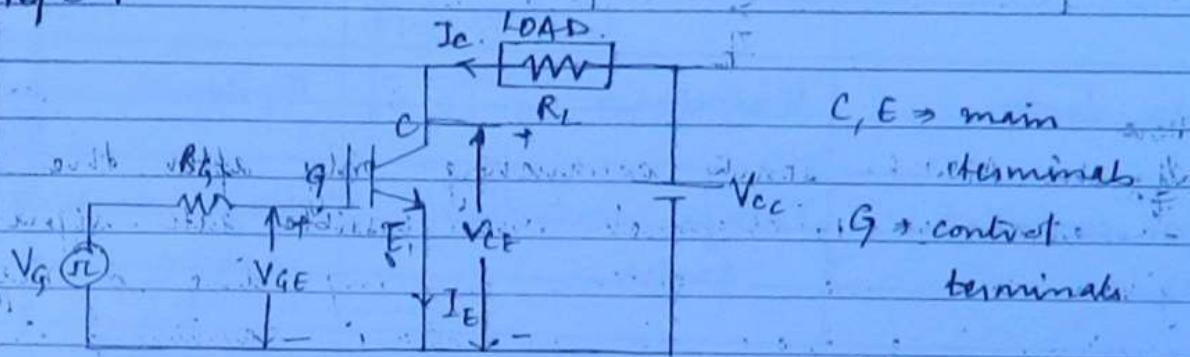

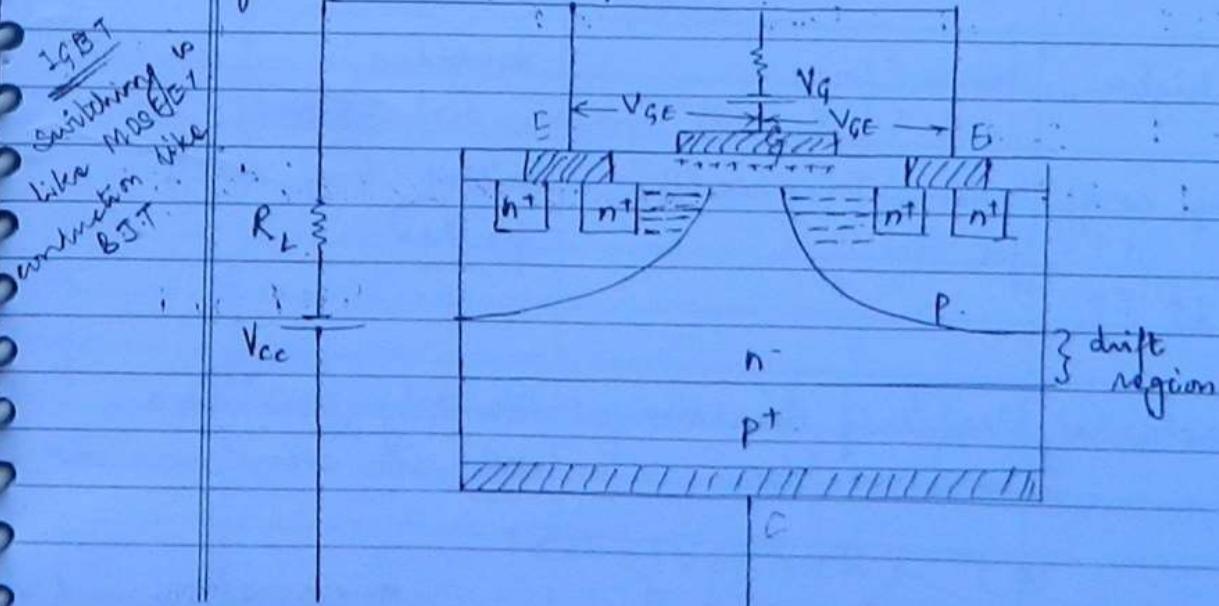IGBT is a hybrid device that gives the advantages of both MOSFET & BJT.



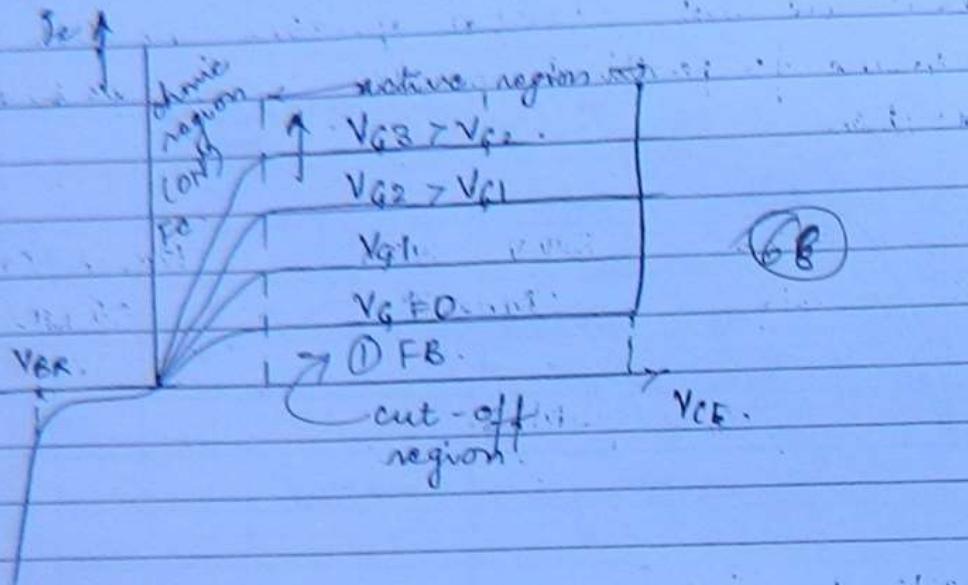

POWER BJT

1. Bipolar device

2. Current controlled device

3. Low i/p impedance

4. on state vfg drop f more
conduction loss is less

5. Switching loss higher

6. DISADV
Negative Temp co-eff
for Ron.

Temp ↑ Ron ↓ I↑ P↑

∴ Secondary breakdown
occurs

POWER MOSFET

Unipolar

Voltage controlled device

high i/p impedance

more

less

Positive Temp co-eff
for Ron.

P

Secondary breakdown
will not occur

IGBT

Bipolar

Voltage controlled device

high i/p impedance

less

less

Positive Temp co-eff
for Ron

Secondary breakdown
will not occur



7. BJTs are not advisable for parallel operation. Parallel operation is possible.

(69)

~~Eatings~~1200V, 800A
10 - 20 KHz500V, 100A
1MHz ↑1200V, 500A,
50 KHz~~App~~

SMPS.

chapter 1 CWB.

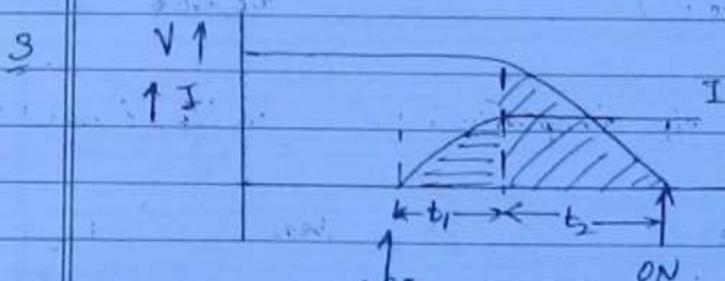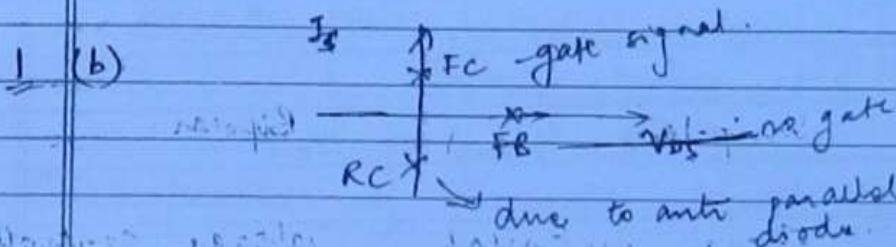


turn-on process

$$\text{Energy lost during } t_1 = V \int_0^{t_1} I \, dt$$

$$= V \cdot \frac{1}{2} I b_1 = \frac{1}{2} V I t_1$$

$$\text{Energy lost during } t_2 = I \left(\int_0^{t_2} V \, dt \right) = I \cdot \frac{1}{2} V t_2 = \frac{1}{2} V I t_2$$
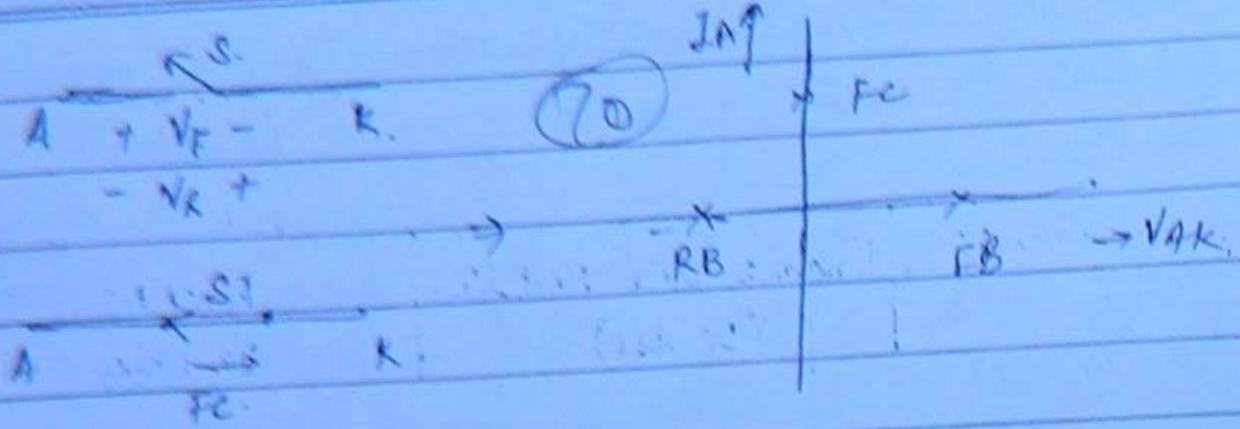
$$\text{Total} = \frac{1}{2} V I (t_1 + t_2) \quad (a)$$






Ans (c)

14

A	
p+	$J_1(r)$
n-	$J_2(r)$
n^+	$J_3(r)$ soil an alkaline soil island vegetation
K+	Pt temp r \approx 1


RECTIFIERS

(70)

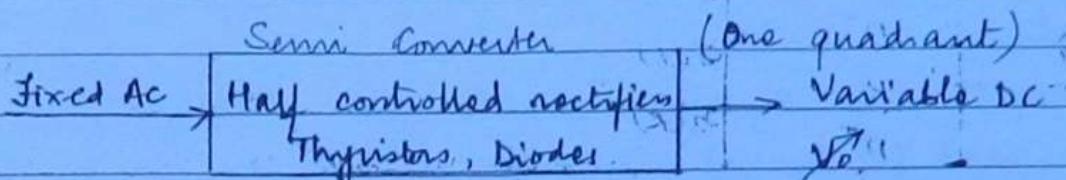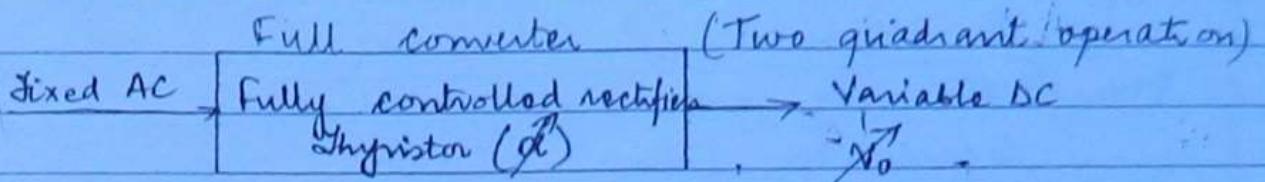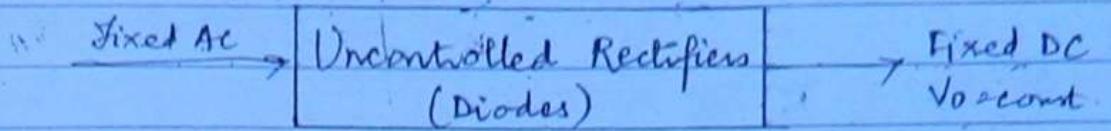


Classification of Converters based on Pulse number (m)


1 One pulse converter.

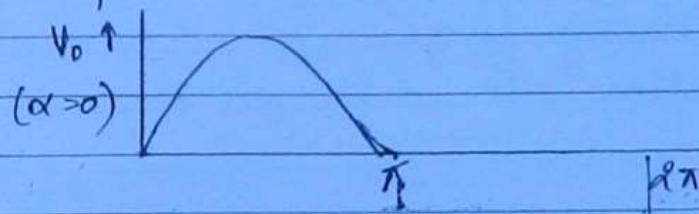

2 Two pulse converter:

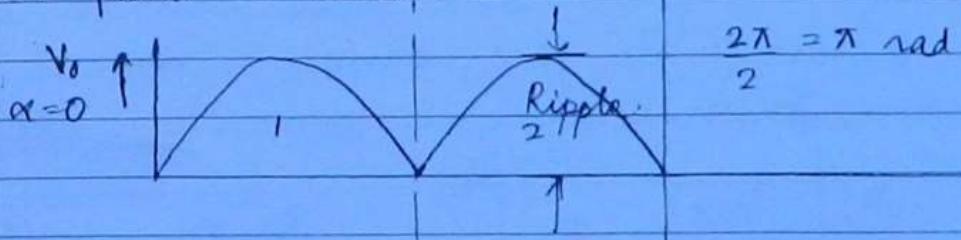

3 Three pulse converter.

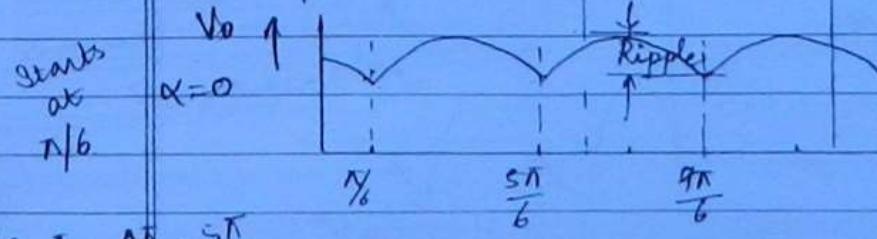


$$\frac{2\pi}{3} = 120^\circ \text{ or } \frac{4\pi}{6}$$

Date _____
Page _____

Output ripple frequency = $f_r = mfs.$
peak to peak.

4. 6 pulse converter.

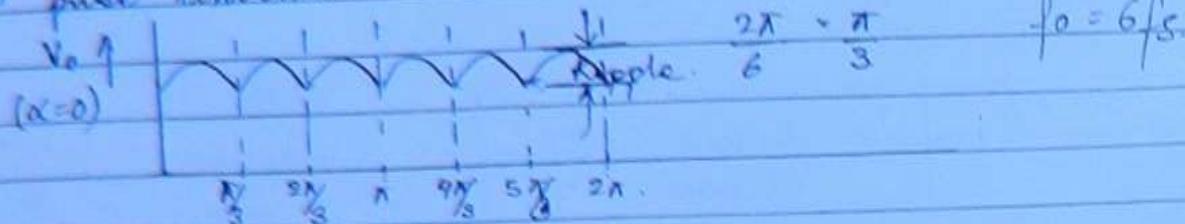

$m \uparrow$ ripple \downarrow \Rightarrow harmonics \downarrow

Now that's why we classify converters
based on pulse number.

Applications


Performance of a DC motor fed with converters -

for R loads (eg heater) harmonics are also useful so take V_{oN} not V_o .

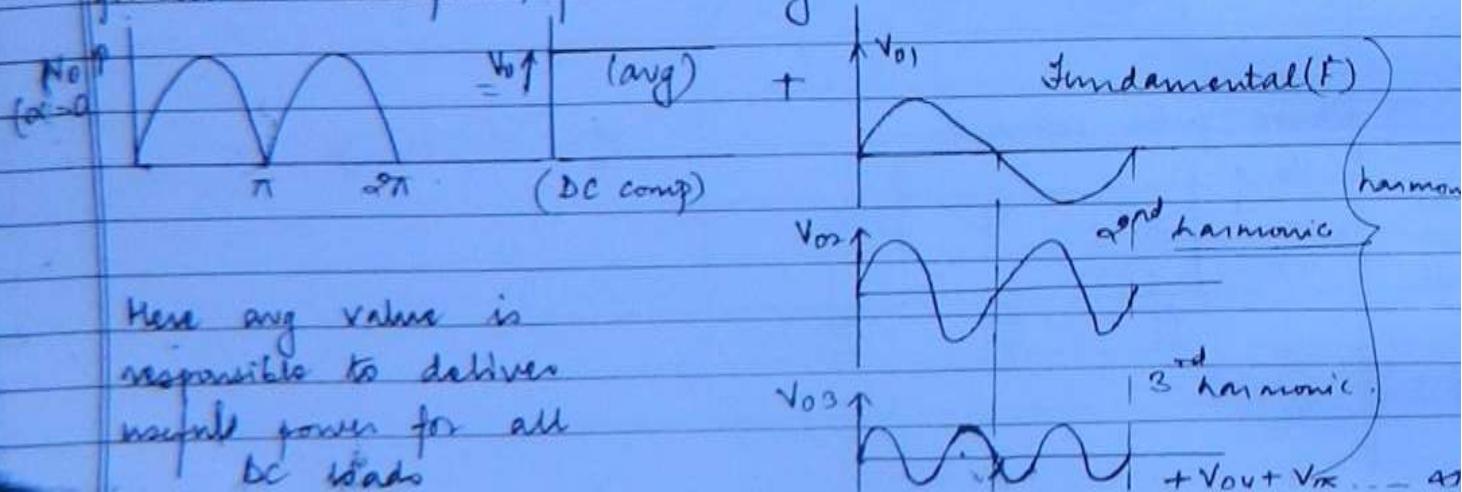- 1. Harmonics will overheat machine windings
 - \therefore we cannot utilise the m/c to its full capacity.
 - \therefore we must derate the m/c when fed with converters.
- 2. Harmonics produce pulsating torque in the motor & hence smooth rotation is not possible.

Harmonic Analysis on DC side of converter (V_o)

Output vlg waveform of a two pulse converter is distorted with harmonics. To find harmonic content present in waveform, fourier analysis is done.



Here avg value is responsible to deliver useful power for all DC loads

$$V_o = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

(73)

$$V_o = a_0 + \sum_{n=1}^{\infty} C_n \sin(n\omega t + \phi_n)$$

avg. where $C_n = \sqrt{a_n^2 + b_n^2}$
(DC comp)

$$V_{oR} = \sqrt{V_o^2 + (V_{o1})_{\text{rms}}^2 + (V_{o2})_{\text{rms}}^2 + (V_{o3})_{\text{rms}}^2 + \dots}$$

RMS avg

Squaring both sides

$$V_{oR}^2 = V_o^2 + (V_{o1})_{\text{rms}}^2 + (V_{o2})_{\text{rms}}^2 + (V_{o3})_{\text{rms}}^2 + \dots$$

$$\sqrt{V_{oR}^2 - V_o^2} = \sqrt{(V_{o1})_{\text{rms}}^2 + (V_{o2})_{\text{rms}}^2 + (V_{o3})_{\text{rms}}^2 + \dots}$$

RMS value of harmonics

VRF = Voltage Ripple Factor

→ It's the measure of harmonics on DC side
of converter.

$$VRF = \frac{\sqrt{V_{oR}^2 - V_o^2}}{V_o} = \sqrt{\left(\frac{V_{oR}}{V_o}\right)^2 - 1} = \sqrt{FF^2 - 1}$$

FF = form factor,
(rms)
(avg)

$$VRF = \sqrt{FF^2 - 1}$$

Quality of perfect DC -

1.	$V_o = V_{oA}$	(74)	without harmonics $FF = 1$ with harmonics $FF > 1$ $FF \downarrow$ approaching unity ⇒ smoothness of waveform is improved towards DC.
2.	$FF = 1$		
3.	$\text{VKF} = 0$		∴ no harmonics. no ripple.

- Form Factor → gives the information of shape of the waveform.

Harmonic analysis on AC side of converter -

- Consider an inverter. Output voltage waveform of inverter is not perfect AC. It's distorted with harmonics.
- For all AC loads, fundamental is responsible to deliver useful power.

$$V_{oA} = \sqrt{V_o^2 + (V_{o1})_{\text{rms}}^2 + (V_{o2})_{\text{rms}}^2 + (V_{o3})_{\text{rms}}^2 + \dots}$$

$\uparrow \quad \uparrow$
RMS avg

$$\sqrt{V_{oA}^2 - (V_{o1})_{\text{rms}}^2} = \sqrt{V_o^2 + (V_{o2})_{\text{rms}}^2 + \dots}$$


Total Harmonic Distortion Method of harmonics on AC side of the converter.

$$\text{THD} = \frac{\sqrt{V_{oA}^2 - V_{o1}^2}}{V_{o1}}$$

Distortion Factor (g) $\rightarrow g = \frac{(V_{01})_{\text{rms}}}{V_{0r}}$

73

w/o harmonics $g = 1$

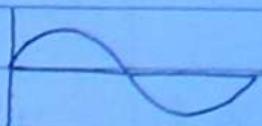

with harmonics $g < 1 [{}^{\circ\circ}(V_{01})_{\text{rms}} < V_{0r}]$

As $g \uparrow$ & approaches unity, smoothness of waveform is improved towards AC.

Qualities of perfect AC

1. $V_{0r} = (V_{01})_{\text{rms}}$


2. $g = 1$

3. $\text{THD} = \left(\frac{1}{g^2} - 1 \right)^{1/2}$


for perfect AC, THD = 0

\Rightarrow no harmonics

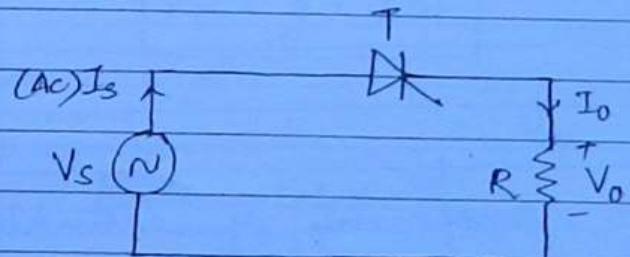1Φ Half Wave Rectifier (one pulse converter)



$$Ig(\alpha, 2\pi + \alpha, \dots)$$

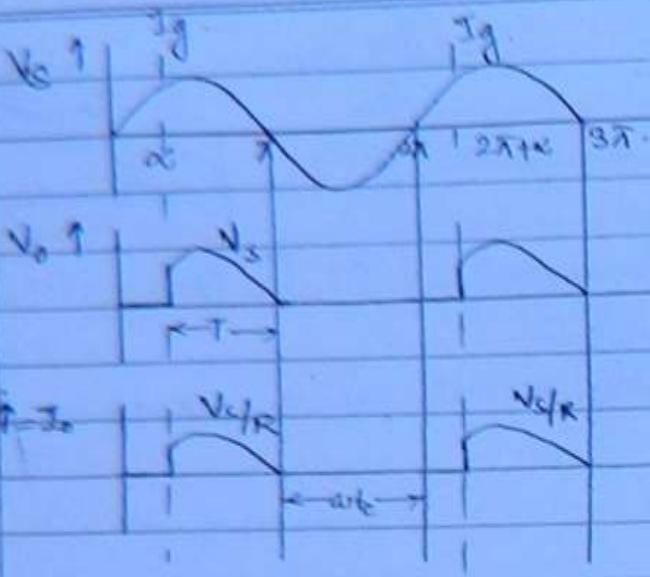

(76)

$$\omega tb_0 = \pi$$

$$t_0 = \frac{\pi}{\omega}$$

$$V_o = \frac{1}{2\pi} \int_{-\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$

$$V_o = V_m (1 + \cos \alpha)$$

$$(I_s)_{avg} = I_o = \frac{V_o}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

DC comp

Disadvantages -

- Source current contains DC component which saturates the supply transformer core.

$$V_{rms} = V_{oR} = \sqrt{\frac{1}{2\pi} \int_{-\alpha}^{\pi} V_m^2 \sin^2 \omega t d(\omega t)}^{1/2}$$

$$\Rightarrow V_{oR} = \sqrt{\frac{1}{2\pi} \int_{-\alpha}^{\pi} V_m^2 \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t)}^{1/2}$$

$$\Rightarrow V_{oR} = \frac{V_m}{2\sqrt{\pi}} \left\{ (\omega t)_{-\alpha}^{\pi} - \frac{1}{2} (\sin 2\omega t)_{-\alpha}^{\pi} \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$

(77)

$$P_{in} = V_{sr} I_{sr} \cos \phi$$

$$P_0 = V_{or} I_{or}$$

$$P_{in} = P_0$$

$$\cos \phi = \frac{V_{or} I_{or}}{V_{sr} I_{sr}}$$

$$\boxed{PF = \frac{V_{or}}{V_{sr}}}$$

$$PF = \frac{1}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$

Power factor depends on -

1. Firing angle - As $\alpha \uparrow$ PF \downarrow
2. PF also depends on the harmonics ie it depends on the shape of the source current waveform.

$$\boxed{PF = g \times FDF}$$

$$\boxed{FDF} = \text{fundamental displacement factor}$$

distortion
factor for source
current waveform

~~fundamental angle~~ ϕ_1

V_{sr}

I_{sr} (fund source current)

$$FDF = \cos \phi_1$$

$$P_{in} = V_{S1} I_{S1} (\text{PF}) = V_{S1} I_{sh} (\text{FDF})$$

$$\text{PF} = \frac{I_{S1}}{I_{S2}} (\text{FDF})$$

I_{S2}

$$\text{PF} = g (\text{FDF})$$

$$g = \frac{I_{S1}}{I_{S2}}$$

(78)


3. PF also depends on load parameters.

Drawback of PE converters -

1. The converters inject harmonics into the supply system (or utility system) & reduce the quality of supply line. To rectify this problem, we must use AC filters on AC side of converter.
2. The converter draws reactive power from supply line for its operation. We must compensate the reactive power required for converter operation by using reactive power source on the AC side of the converter.

(II) 1φ Half Wave Rectifier \rightarrow RL load.

① α to π $T \rightarrow \text{ON}$

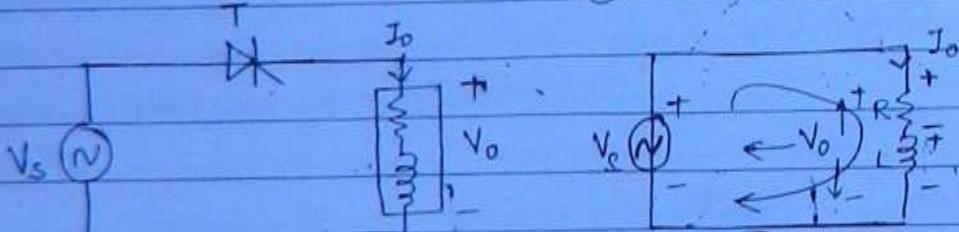

(P+)

$P_{\text{source}} \rightarrow P_{\text{load}}$

$$\therefore P = (I^2 R + \frac{1}{2} L I^2)$$

L stores energy.

$$V_m \sin(\omega t) = R\dot{I} + L \frac{di}{dt}$$

$$I_o = I_{\text{steady}} + I_{\text{transient}}$$

(79)

$$I_{\text{steady}} = \frac{V_m}{|Z|} \sin(\omega t - \phi)$$

$$\text{where } |Z| = \sqrt{R^2 + (\omega L)^2}$$

$$\phi = \tan^{-1} \frac{\omega L}{R}$$

$$I_{\text{transient}} = K e^{-t/\tau}$$

$$I_o = I_{\text{steady}} + I_{\text{trans.}}$$


$$I_o = \frac{V_m}{|Z|} \sin(\omega t - \phi) + K e^{-t/\tau}$$


$$\text{At } \omega t = \alpha \quad I_o = 0$$

$$\begin{matrix} t = \infty \\ \omega \end{matrix} \quad \begin{matrix} \tau = L \\ R \end{matrix}$$

$$0 = \frac{V_m}{|Z|} \sin(\omega t - \phi) + K e^{-R\alpha/\omega L}$$

$$K = \frac{-V_m \sin(\alpha - \phi)}{|Z|} e^{R\alpha/\omega L}$$

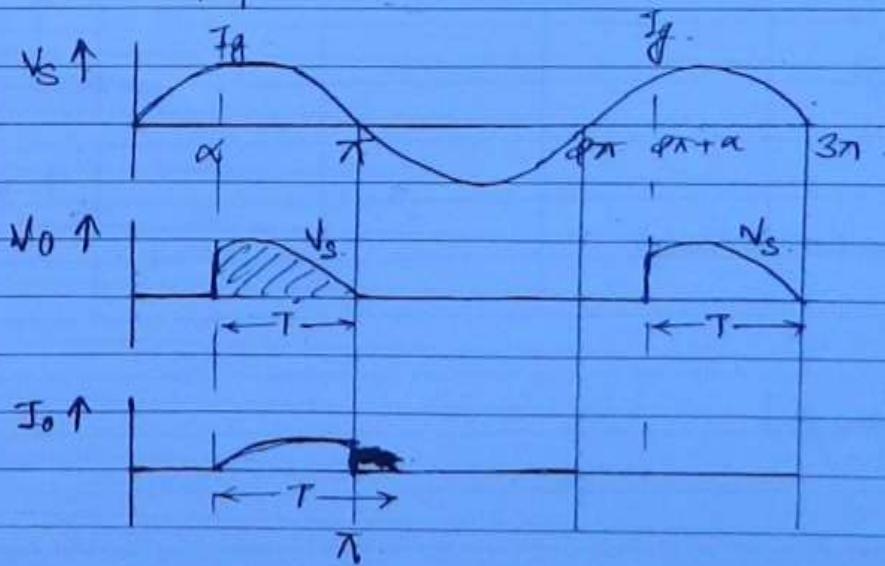


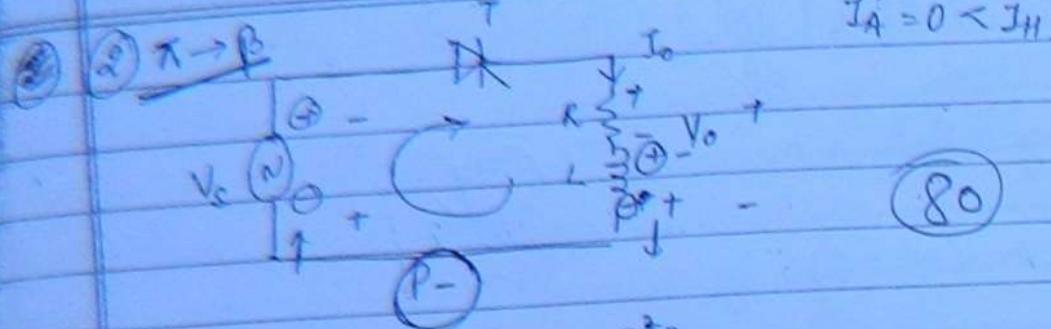

$$1. L I^2 \rightarrow \text{source} + I^2 R$$

2. \Rightarrow The inductance energy maintains conduction of thyristor even in the reverse cycle until it releases the complete energy at $\omega t = \beta$.

β = extinction angle.

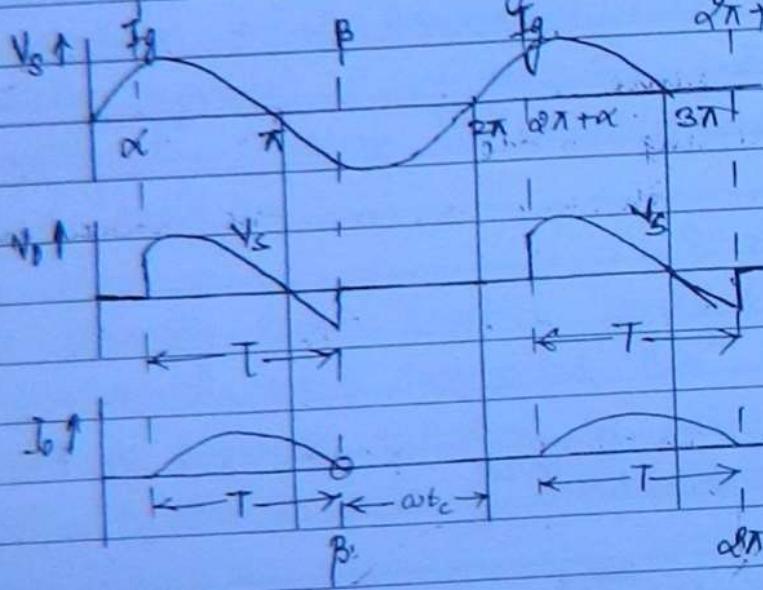

At $\omega t = \pi$ reverse $\alpha\pi + \beta$. vfg is applied across SCR but it'll still conduct, SCR doesn't get turned OFF until $I_A = 0$.
 L : does not accept sudden change in i . I_A continues to flow till $\beta \rightarrow$ the point $\alpha\pi + \beta$ where L loses its energy completely.

$$\omega t_c = \alpha\pi - \beta$$

$$t_c = \frac{\alpha\pi - \beta}{\omega}$$


$$V_o = \frac{1}{\alpha\pi} \int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t)$$

$$V_o = \frac{V_m}{\alpha\pi} [\cos \alpha - \cos \beta]$$

$$V_{ov} = \left\{ \frac{1}{2\pi} \int_0^T V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{ov} = \frac{V_m}{2\sqrt{\pi}} \left[(\beta - \alpha) + \frac{1}{2} (\sin^2 \alpha - \sin^2 \beta) \right] \quad (81)$$

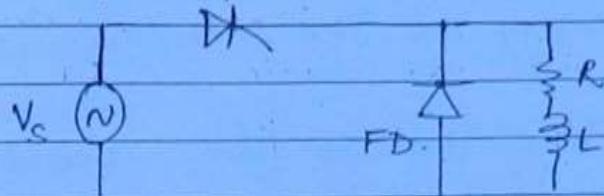(III) 1-φ Half Wave Rectifier \rightarrow RL load with FD.




① mode is same.

② ~~no~~ free wheeling mode.

During free wheeling action, -ve spikes are removed

L releases energy through $I^2R \rightarrow$ takes more time $\beta \uparrow$

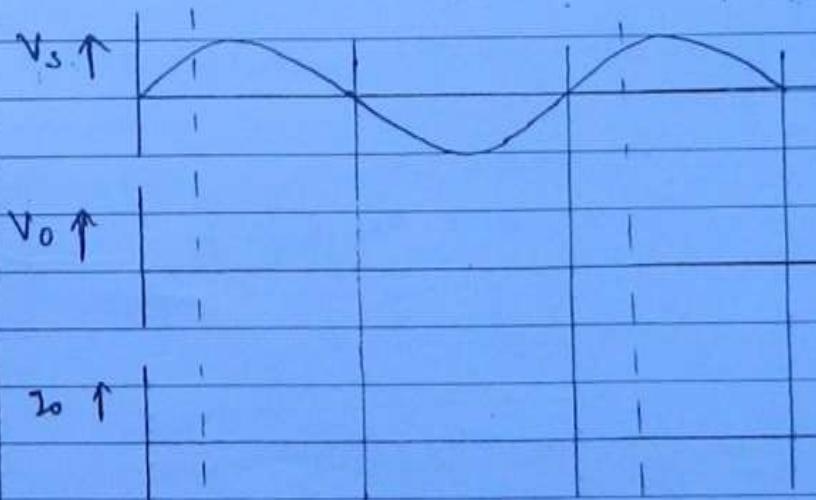smoothness improves $g \uparrow$ PF \uparrow




Advantages of FD -

(82)

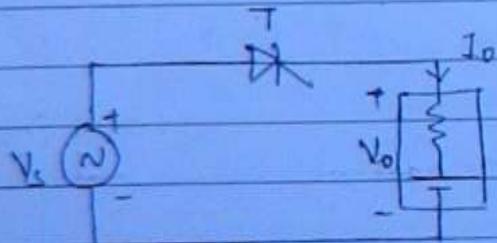1. PF is improved
2. No spikes in load vfg is improved & this ↑ avg vfg.
3. Smoothness of output current waveform is improved as $\beta \uparrow$
4. The overall performance of the converter is improved with FD.
5. There will be freewheeling action in semiconverter.
6. PF is better in semiconverter as compared to full converters.
7. Performance of semiconverter is superior to full converter.

1-φ Half Wave Rectifier - Charging a battery (RL load)



$$\text{At } \omega t = \theta_1,$$

$$V_s = E$$

$$V_m \sin \theta_1 = E$$

$$\alpha_{\min} = \theta_1 = \sin^{-1}\left(\frac{E}{V_m}\right)$$

$$\alpha_{\max} = \theta_2 = \pi - \theta_1$$

$$\theta_1 \leq \alpha \leq \theta_2$$


$\text{Ig}(\alpha, 2\pi + \alpha, \dots)$

$$T \rightarrow \underline{\text{ON}} \Rightarrow V_o = V_s \Rightarrow V_s = I_o R + E$$

$$I_o = \frac{V_s - E}{R} = \frac{V_m \sin \omega t - E}{R}$$

$$V_o \uparrow V_s$$
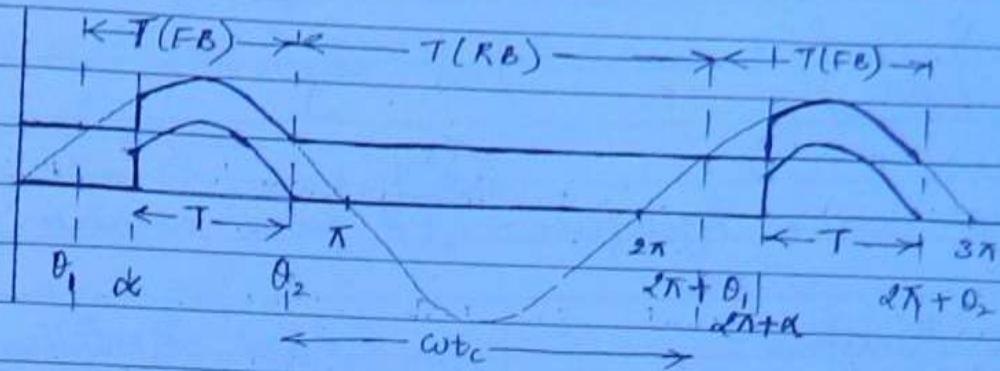
$$I_o \uparrow T \rightarrow \\ = I_{s1} \uparrow$$



(83)

$$\omega t_c = (2\pi + \theta_1) - \theta_2 \\ = (\alpha + \theta_1) - (\pi - \theta_2)$$

$$\boxed{t_c = \frac{\pi + 2\theta_1}{\omega}}$$

$$PIV_F, V_m + E$$

$$V_o = \frac{1}{2\pi} \left[\int_{\alpha}^{\theta_2} V_m \sin \omega t d(\omega t) + \int_{\theta_2}^{2\pi + \alpha} E d(\omega t) \right]$$

$$V_o = \frac{1}{2\pi} \left[V_m (\cos \alpha - \cos \theta_2) + E \underbrace{(\alpha + \alpha - \theta_2)}_{\text{radians}} \right]$$

* Avg charging current of the battery

$$I_o = \frac{1}{2\pi R} \int_{\alpha}^{\theta_2} V_m \sin \omega t - E d(\omega t)$$

$$I_o = \frac{1}{2\pi R} \left[V_m (\cos \alpha - \cos \theta_2) - E \underbrace{(\theta_2 - \alpha)}_{\text{radians}} \right]$$

$$Pin = V_{sr} I_{sr} (\text{PF})$$

$$P_o = I_{sr}^2 R + EI_o$$

$$PF = \frac{I_{sr}^2 R + EI_o}{V_{sr} I_{sr}}$$


$$PF = \frac{I_{sr}^2 R + EI_o}{V_{sr} I_{sr}}$$

$$I_{av} = \frac{1}{2\pi} \int_0^{\alpha} \left(\frac{V_m \sin \omega t - E}{R} \right)^2 d(\omega t) \frac{V_o}{2}$$

(84)

1-φ Full Wave Rectifiers - (2 pulse converter)


Midpoint Rectifiers -

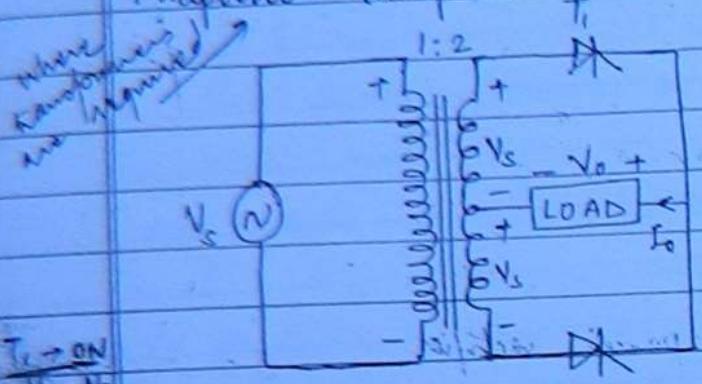

$$\begin{aligned} T_1 \rightarrow ON \\ V_o = V_s \\ I_o = V_s/R \end{aligned}$$

$$+ T_1 (\text{FB}) I_g(\alpha, 2\pi + \alpha \dots) \\ - T_2 (\text{FB}) I_g(\pi + \alpha, 3\pi + \alpha \dots)$$

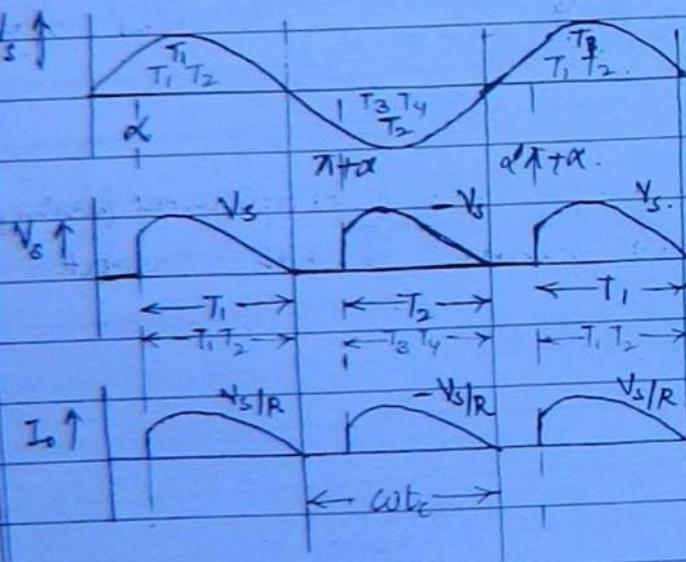
$$\begin{aligned} T_2 \rightarrow ON \\ V_o = -V_s \\ I_o = -V_s/R \end{aligned}$$



$$\omega t_c = \pi$$

$t_c = \pi / \omega$
sec

Bridge Rectifiers -

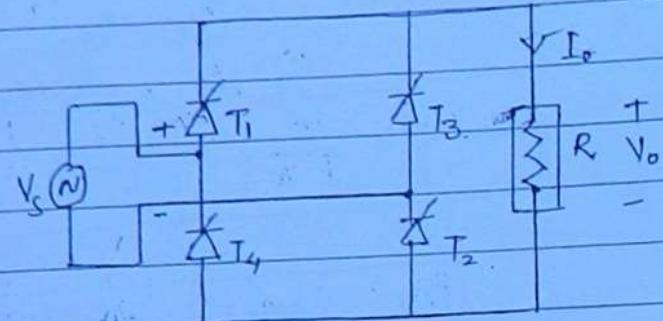

$$+ T_1, T_2 (\text{FB}) I_g(\alpha, 2\pi + \alpha \dots) \\ - T_3, T_4 (\text{FB}) I_g(\pi + \alpha, 3\pi + \alpha \dots)$$

$$\begin{aligned} T_1, T_2 \rightarrow ON \\ V_o = V_s \\ I_o = V_s/R \end{aligned}$$

$$\begin{aligned} T_3, T_4 \rightarrow ON \\ V_o = -V_s \\ I_o = -V_s/R \end{aligned}$$

$$\begin{aligned} T_3, T_4 \rightarrow ON \\ V_o = -V_s \\ I_o = -V_s/R \end{aligned}$$

$$V_o = \frac{1}{\pi} \int_{-\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

(85)

$$V_{oN} = \left\{ \frac{1}{\pi} \int_{-\alpha}^{\pi} V_m^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

$$V_{oN} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

\uparrow
 $\alpha \uparrow$



$$\begin{cases} PIV = \alpha V_m & \rightarrow \text{In mid-point rectifier} \\ PIV = V_m & \rightarrow \text{bridge rectifier} \end{cases}$$

Advantages of Bridge Rectifier -

1. PIV of thyristor in bridge rectifier is half that of mid-point rectifier.
2. If same thyristors with same specifications (same voltage ratings) are used in both converters then power handled by bridge rectifier is double that of mid-point rectifier.

1-Φ Full Wave Rectifiers (R-L Load) (Full converter)

Discontinuous conduction

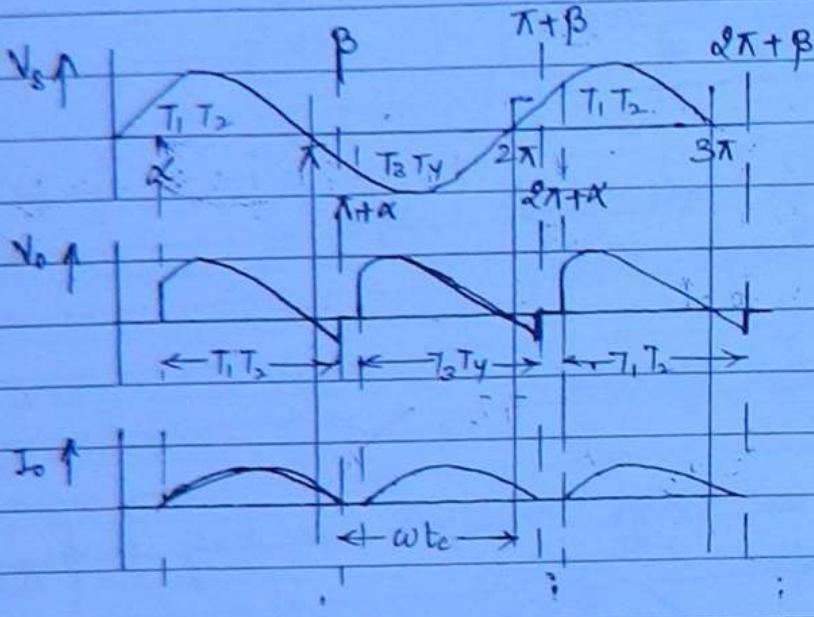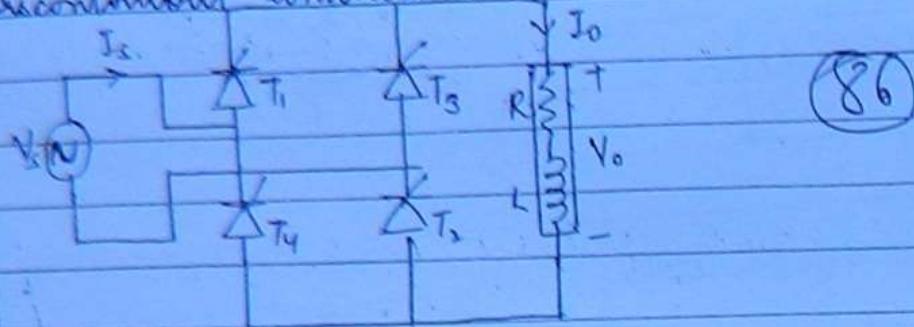

$$\omega t_c = 2\pi - \beta$$

$$t_c = \frac{2\pi - \beta}{\omega}$$

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin(\omega t) d(\omega t)$$

$$V_o = \frac{V_m}{\pi} (\cos \alpha - \cos \beta)$$

$$V_{o2} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2(\omega t) d(\omega t) \right\}^{1/2}$$

$$V_{o2} = \frac{V_m}{\sqrt{2\pi}} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]^{1/2}$$

Reasons for Discontinuous conduction -

1. $L \downarrow$ [Time constant $T \downarrow = \frac{L}{R}$] or $R \uparrow$
 $T \downarrow \therefore \beta \downarrow$ [$\beta < (\pi + \alpha)$]


(87)

2. $\alpha \uparrow$ (High value of firing angle) — less energy is stored in inductor.

3. $I_0 \downarrow \quad \downarrow E = \frac{1}{2} i^2 \downarrow$ not sufficient energy.

RL Load Continuous Conduction

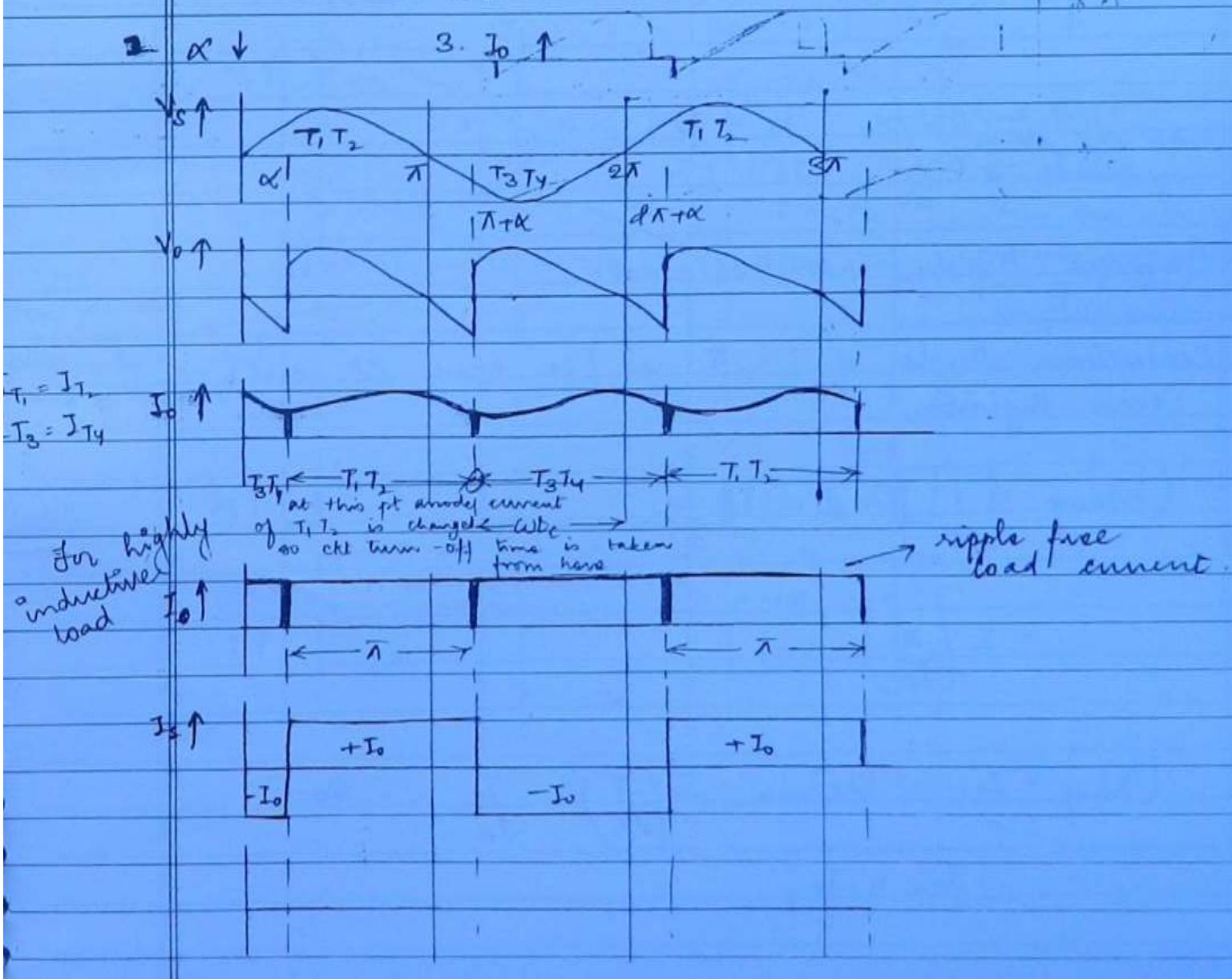1. $L \uparrow$ [$\uparrow T = \frac{\uparrow L}{R}$]
2. $\alpha \downarrow$
3. $I_0 \uparrow$



$$V_o = \frac{1}{\pi} \int_{-\pi}^{\pi} V_m \sin \omega t d(\omega t)$$

$V_o = \frac{2V_m \cos \alpha}{\pi}$

(88)

$$V_o = \sqrt{\frac{1}{\pi} \int_{-\pi}^{\pi} V_m^2 \sin^2 \omega t d(\omega t)}^{1/2}$$

$V_o = \frac{V_m}{\sqrt{2}}$

→ Equating V_s or V_o waveform gives same waveform so their rms values are equal.

Hence Rms value of $V_s = \frac{V_m}{\sqrt{2}}$.

$$\omega t_c = 2\pi - (\pi + \alpha)$$

so is that of V_o .

$t_c \Rightarrow \pi + \alpha$

ω

$T_1 T_2 \rightarrow ON$

$$I_s = I_0$$

$T_3 T_4 \rightarrow ON$

$$I_s = -I_0$$

Assume highly inductive load -

Conduction Angle of each thyristor = π rad [for every 2π rad]

$$(I_0)_{avg} = \frac{1}{2\pi} \int_{-\pi}^{\pi} I_0 d(\omega t) = \frac{I_0}{2}$$

$$= I_0 \left(\frac{\pi}{2\pi} \right)$$

$$(I_T)_{avg} = \frac{I_0}{2} \quad (I_T)_{rms} = I_0 \left(\frac{\pi}{2\pi} \right)^{1/2} = \frac{I_0}{\sqrt{2}} \quad Q_0$$


$I_{avg} = I_0$

1- ϕ Half Controlled Rectifier - (Semi Converter)

(89)

Symmetrical Connection -

Asymmetrical Connection -

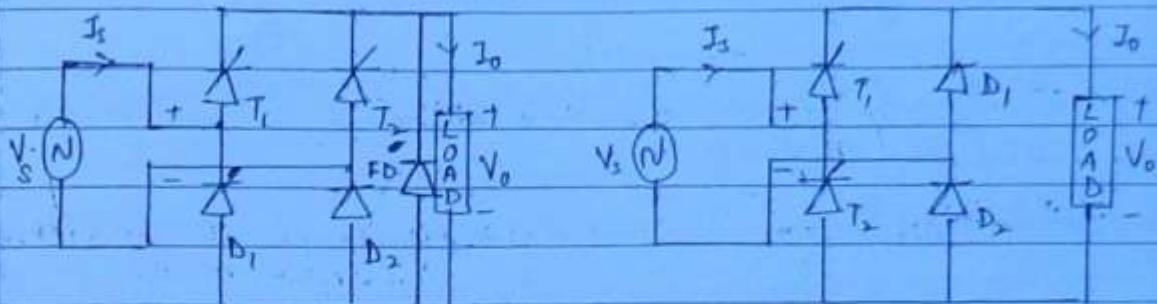


+ T₁, D₂ (F)

- T₂, D₁ (F)


+ T₁, D₂ (F)

- T₂, D₁ (F)

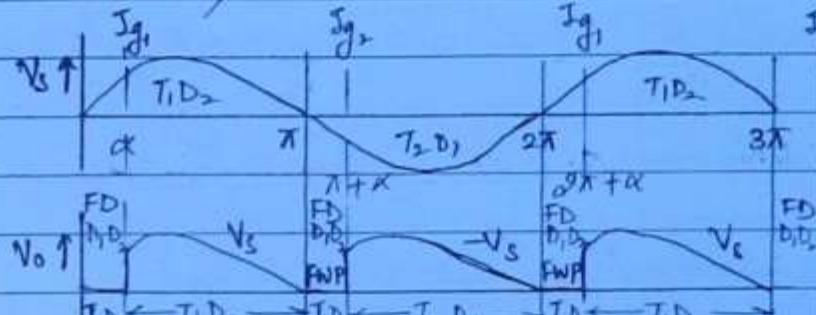

FNP

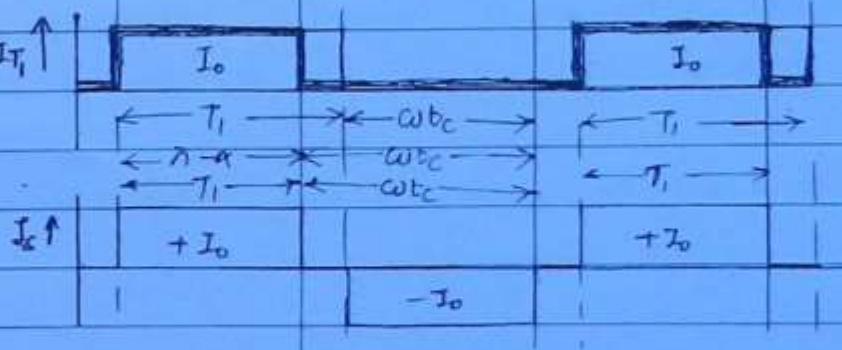Free wheeling period
(that's why no need of separate FD)



Due to Free-wheeling
diode -ve spikes
are removed.
Thus the V_o
becomes same as
that of R load
in full converter

For resistive load waveform remains same for full converter & semi converter

Assume highly inductive load -

(90)

$$\pi \text{ to } \pi + \alpha \quad T_1 D_1 \rightarrow \text{ON}$$

$$\text{FWP} \quad V_o = 0$$

$$\text{FWP} \quad I_S = 0$$

$$T_2 D_2 \rightarrow \text{ON} \quad I_S = I_0$$

$$T_2 D_1 \rightarrow \text{ON} \quad I_S = -I_0$$

$$t_{bc} > \omega t_{bc} = \alpha\pi - (\pi + \alpha) \quad \therefore \quad \omega t_{bc} = \alpha\pi - \pi$$

$$\boxed{t_{bc} = \frac{\pi - \alpha}{\omega}}$$

$$\boxed{t_{bc} = \frac{\pi}{\omega}}$$

* In symmetrical connection there's a possibility of SC action in the supply when the incoming thyristor starts conducting before the outgoing thyristor stops conducting. Here the problem is severe, because before the incoming thyristor starts conducting, the free wheeling action is through outgoing thyristor because of which SC period is more.

* To rectify this problem we must use a separate FD.

Symmetrical connection with FD.

$$V_o = \frac{1}{\pi \alpha} \int_{\pi}^{\pi} V_m \sin(\omega t) d(\omega t)$$

$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}\pi} \left[\frac{(\pi - \alpha)}{2} + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

(91)

Assume highly inductive load -

Conduction angle each thyristor = $(\pi - \alpha)$ rad [for every $\frac{\pi}{2}$ rad]

$$= \underline{\pi - \alpha}$$

$$/ d\pi$$

Conduction angle of FD = α rad [for every π rad]

$$= \underline{\alpha}$$

$$(I_T)_{avg} = I_0 \left(\frac{\pi - \alpha}{2\pi} \right)$$


$$(I_{FD})_{avg} = I_0 \left(\frac{\alpha}{\pi} \right)$$

$$(I_T)_{rms} = I_0 \left(\frac{\pi - \alpha}{d\pi} \right)^{1/2}$$

$$(I_{FD})_{rms} = I_0 \left(\frac{\alpha}{\pi} \right)^{1/2}$$

$I_{eq} = I_0 \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$

1φ Full Converter - Charging a Battery

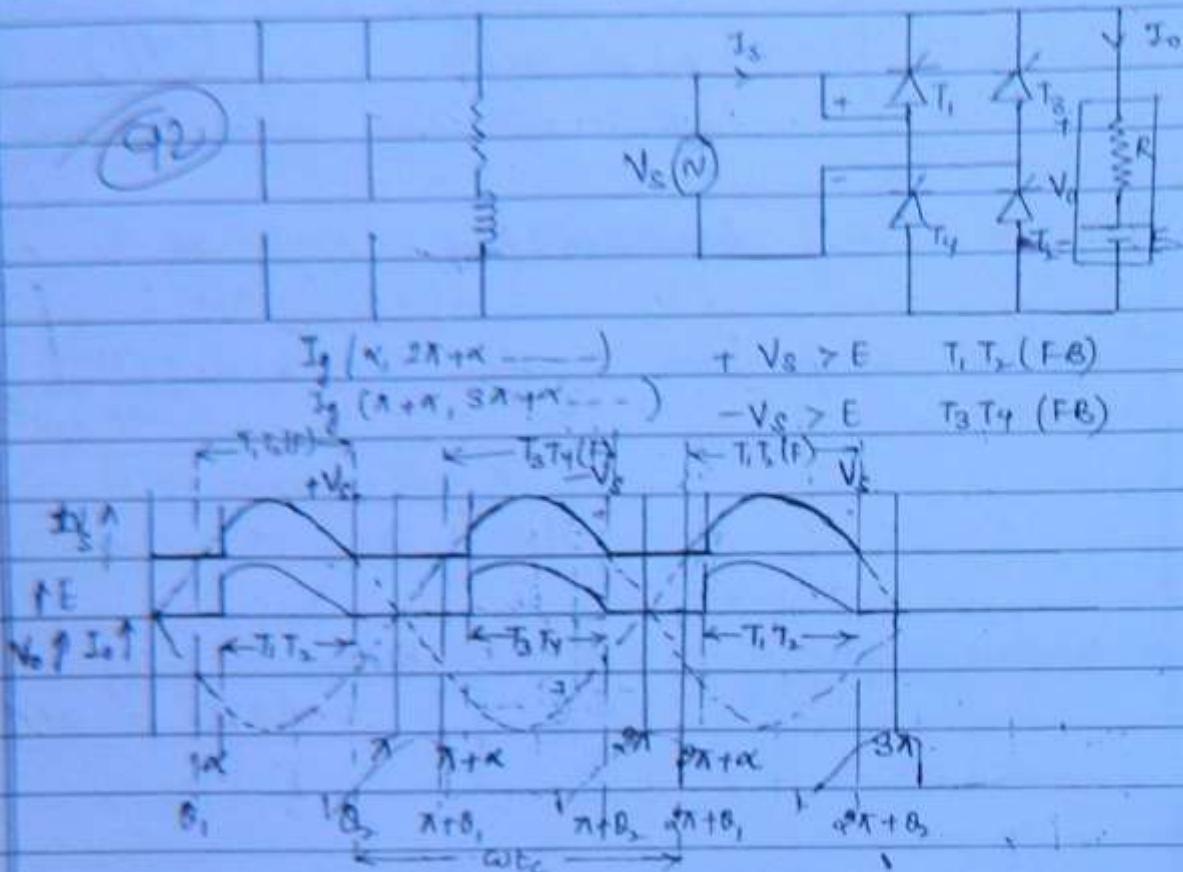

$$T_1, T_2 \rightarrow \text{ON}$$

$$V_B = V_S$$

$$I_S = V_S - E \\ R$$

$$\theta_1 = \sin^{-1} \frac{E}{V_m}$$

$$\theta_2 = \pi - \theta_1$$

$I_S = V_m \sin \omega t - E$
R

$$\omega t_c = (2\pi + \theta_1) - \theta_2 \\ = (2\pi + \theta_1) - (\pi - \theta_1)$$

$t_c = \pi + 2\theta_1$
$c\omega$


$$V_O = \frac{1}{\pi} \left[\int_{\theta_2}^{\theta_2} V_m \sin \omega t d(\omega t) + \int_{\theta_2}^{\pi + \alpha} E d(\omega t) \right]$$

$$V_O = \frac{1}{\pi} \left[V_m (\cos \alpha - \cos \theta_2) + E (\pi + \alpha - \theta_2) \right]$$


$$I_0 = \frac{1}{\pi} \int_{-\alpha}^{\alpha} \left[\frac{V_m \sin(\omega t - \theta)}{R} d(\omega t) \right]$$

$$I_0 = \frac{1}{\pi R} \int [V_m (\cos \alpha - \cos \theta_2) - E(\theta_2 - \alpha)]$$


1φ Full Converter - DC Motor (RLE Load)

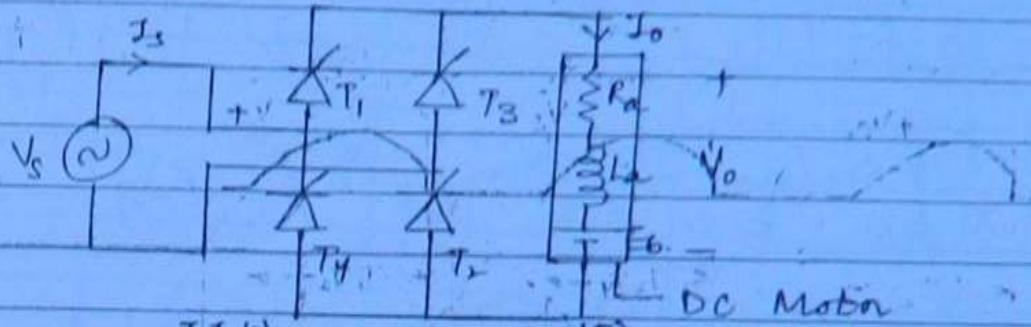

$\beta < \pi$

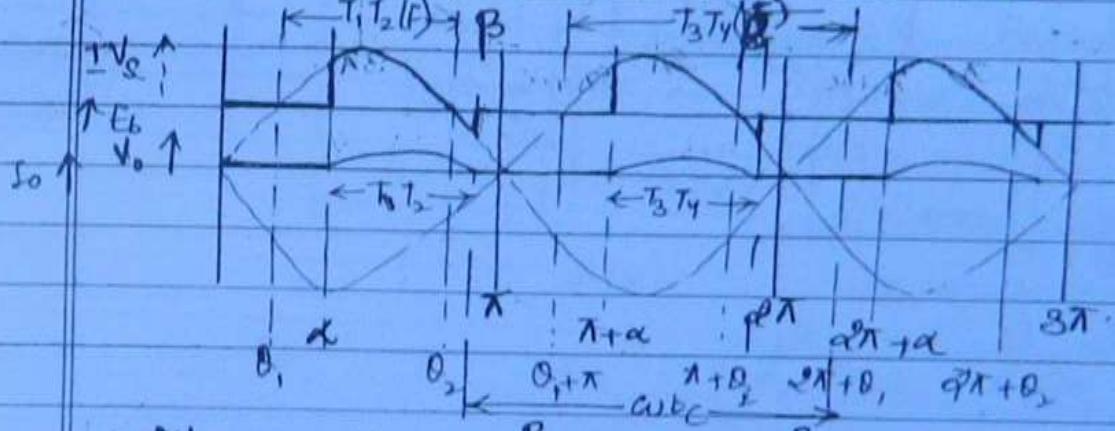

$\beta > \pi$

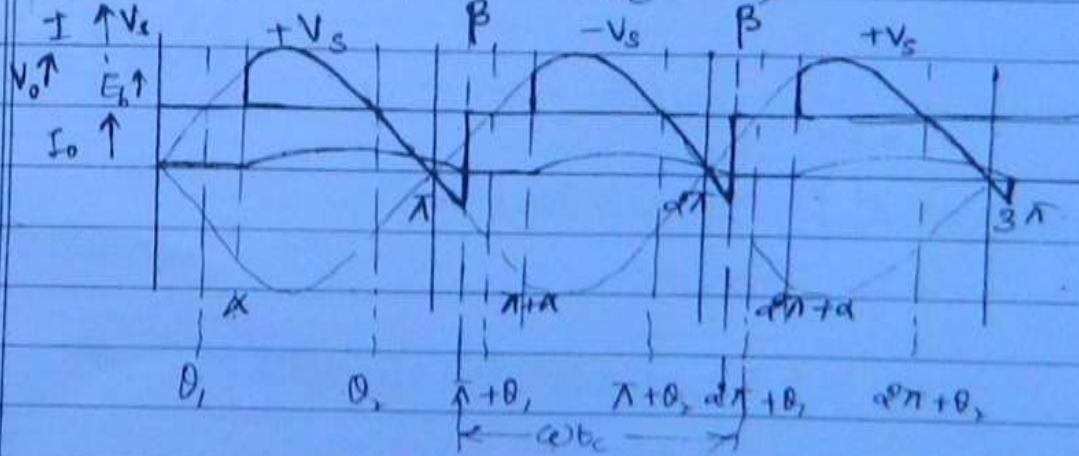

$$\omega t_0 = (\alpha\pi + \theta_1) - \beta.$$

$$\downarrow t_0 = \frac{\alpha\pi + \theta_1 - \beta}{\omega}$$

(94)

In continuous conduction waveform remains same for RL & RLE load.

$$V_o = \frac{1}{\pi} \left[\int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t) + \int_{\beta}^{\pi+\alpha} E_b d(\omega t) \right]$$

$$V_o = \frac{1}{\pi} [V_m (\cos \alpha - \cos \beta) + E_b (\pi + \alpha - \beta)]$$


In continuous conduction

$$V_o = \frac{\alpha}{\pi} V_m \cos \alpha \rightarrow \text{RL, RLE.}$$

$$I_o = \frac{V_o}{R} \rightarrow \text{RL}$$


$$I_o = \frac{V_o - E_b}{R_a} \rightarrow \text{RLG}$$

1φ Semicomverter - DC Motor (RLE load)

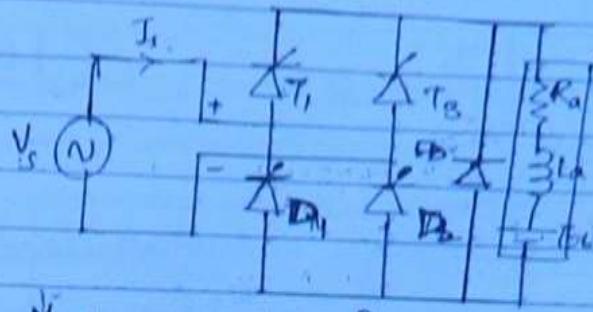

$$\beta < \pi$$

FD will not conduct

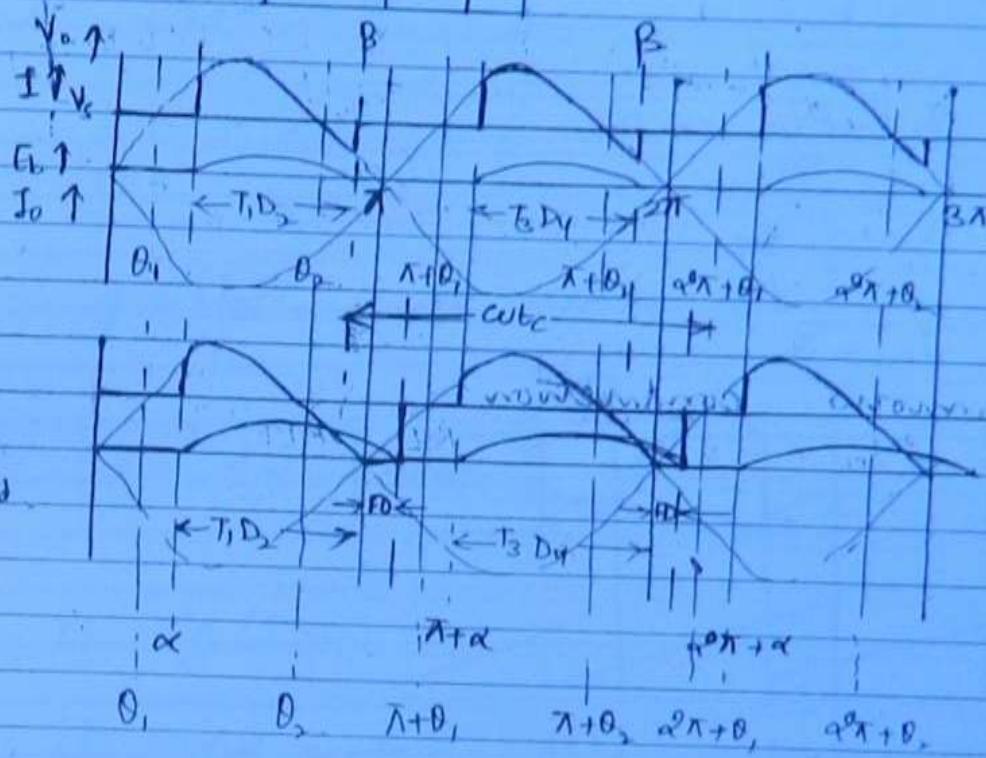

$$\beta > \pi$$

conduction of FD = $(\beta - \pi)$ rad.

for $\boxed{\beta > \pi}$

$$V_o = \frac{1}{\pi} \left[\int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) + \int_{\beta}^{\pi+\alpha} E_b d(\omega t) \right]$$

$$V_o = \frac{1}{\pi} \left[V_m (1 + \cos \alpha) + E_b (\pi + \alpha - \beta) \right]$$


for continuous conduction waveform remains same
for RL f RLE load.

Back emf will not affect the avg value

$$\boxed{V_o = \frac{V_m}{\pi} (1 + \cos \alpha)}$$

Performance of 1φ Full Converter -

(96)

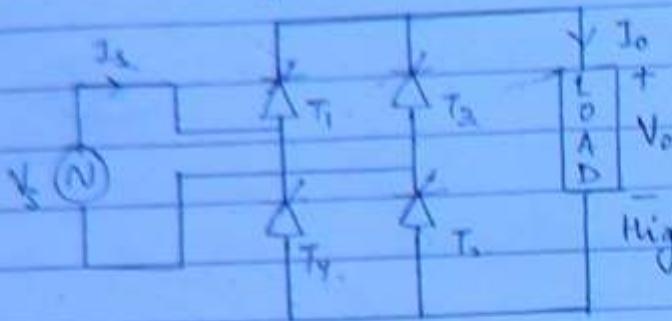


Highly inductive load.
(RL, RLE)

$$V_o = \alpha V_m \cos \alpha$$

π

$$V_{av} = \frac{V_m}{\sqrt{2}}$$

$$I_{S,A} = I_o$$

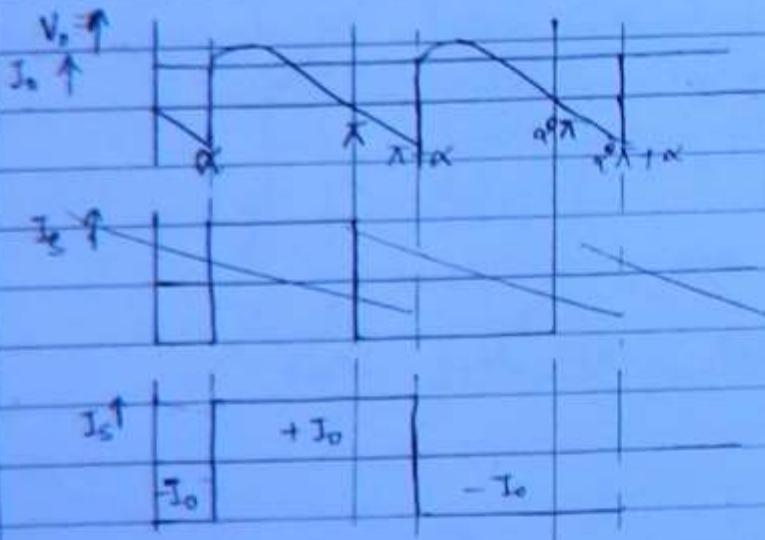

Harmonic Analysis on AC side of converter for source current (I_s)

$I_{S1}(F) \quad I_{S3}$

$$I_s = \sum_{n=1,3,5, \dots}^{\infty} \frac{4I_o \sin(n\omega t + \phi_n)}{n\pi} = \frac{4I_o \sin(\omega t - \alpha)}{\pi} + \frac{4I_o \sin(3\omega t - 3\alpha)}{3\pi} + \frac{4I_o \sin(5\omega t - 5\alpha)}{5\pi} \dots$$

$$\phi_n = -n\alpha$$

↳ n^{th} harmonic displacement angle.

$$I_{sn} = \frac{4I_0}{n\pi} \sin(nwt + \phi_n)$$

(67)

$$(I_{sn})_{rms} = \frac{\varrho\sqrt{2}}{n\pi} I_0$$

$$\left[(I_{sn})_{rms} = \frac{\varrho\sqrt{2}}{\pi} I_0 \right] - (1)$$

$$FDF = \cos \phi_1$$

$$\left[FDF = \cos(-\alpha) = \cos \alpha \right] - (2)$$

$$g = \frac{(I_{sn})_{rms}}{I_{SN}} \rightarrow \frac{\varrho\sqrt{2}}{\pi} \frac{I_0}{I_{SN}}$$

$$\left[g = \frac{\varrho\sqrt{2}}{\pi} \right] - (3)$$

$$PF = g(FDF)$$

$$\left[PF = \frac{\varrho\sqrt{2}}{\pi} \cos \alpha \right] - (4)$$

$$THD = \left(\frac{1}{g^2} - 1 \right)^{\frac{1}{2}}$$

$$THD = \left(\frac{\pi^2}{8} - 1 \right)^{\frac{1}{2}} = 0.4834$$

$$\left[THD = 48.34\% \right] - (5)$$

avg. current
useful power

avg. current
useful power.

Active power -

$$P = V_m I_m \cos \alpha = V_o I_o \quad \text{--- (6)}$$

$$= \left(\frac{V_m}{\sqrt{2}} \right) \left(\frac{2\sqrt{2} I_o}{\pi} \right) \cos \alpha$$

(98)

$$P = \frac{\pi}{4} V_m \cos \alpha, \quad I_o = V_o I_o$$

Reactive Power -

$$Q = V_m I_m \sin \alpha = V_o I_o \tan \alpha \quad \text{--- (7)}$$

$$= V_m I_m \cos \alpha, \sin \alpha$$

$$\cos \alpha$$

$$Q = P \tan \alpha$$

Harmonics on DC side of converter - (V_o)

$$VRF = \sqrt{FF^2 - 1}$$

$$FF = \frac{V_m}{V_o} \quad V_{oN} = \frac{V_m / \sqrt{2}}{\frac{\pi}{4} V_m \cos \alpha} = \frac{\pi}{4\sqrt{2}} \cos \alpha,$$

$$VRF = \sqrt{\pi^2 - 1}$$

$$\sqrt{8 \cos^2 \alpha}$$

When $0^\circ < \alpha < 90^\circ$


$\alpha \uparrow$ ripple \uparrow harmonics \uparrow

When $90^\circ < \alpha < 180^\circ$

$\alpha \uparrow$ ripple \downarrow harmonics \downarrow

Performance of 1 φ Semi Converter -


(79)

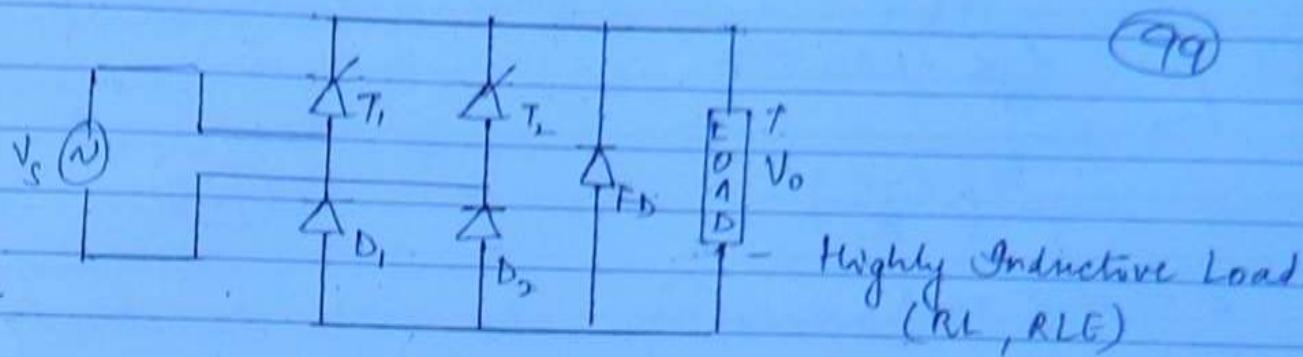

$$V_s = V_m \sin(\omega t) \quad V_{s\sqrt{2}} = V_m \sqrt{2}$$

$$V_o = V_m \left(1 + \cos \alpha \right)$$
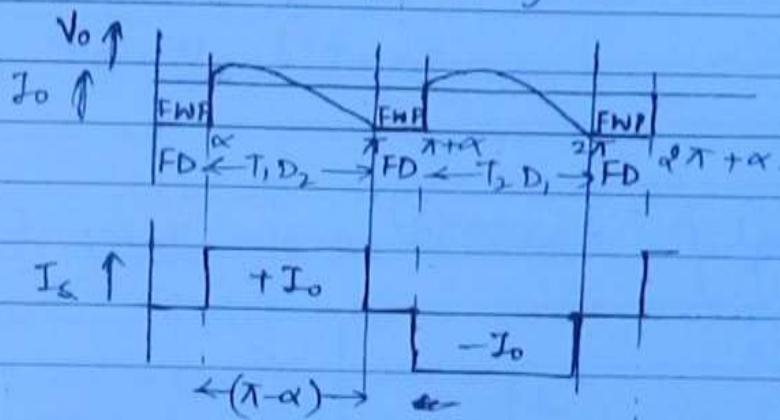
$$\therefore I_{s\sqrt{2}} = I_o \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$



Harmonic Analysis of on Ac side of Converter (I_s)

$$I_s = \sum_{n=1,3,5,\dots}^{\infty} \frac{4 I_o}{n \pi} \cos n \alpha \sin(n \omega t + \phi_n)$$

$$\text{where } \phi_n = -\frac{n \alpha}{2}$$

$$(I_{sn})_{nm} = \frac{2\sqrt{2}}{n \pi} I_o \cos n \alpha$$

$$(I_{s1})_{nm} = \frac{2\sqrt{2}}{\pi} I_o \cos \frac{\alpha}{2} \quad \text{--- (1)}$$

$$FDF = \frac{\cos \alpha}{2} \quad -\textcircled{2}$$

$$g = \frac{I_{S1}}{I_{S1}} = \frac{2\sqrt{2} I_0 \cos \alpha / 2}{\pi} \\ I_0 \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$

(102)

$$g = \frac{2\sqrt{2} \cos \alpha}{2} \quad -\textcircled{3}$$

$$\sqrt{\pi(\pi - \alpha)}$$

$$PF = g \quad (\text{FDF})$$

$$PF = \frac{2\sqrt{2} \cos \alpha}{2} = \frac{\sqrt{2}(1 + \cos \alpha)}{\sqrt{\pi(\pi - \alpha)}} \quad -\textcircled{4}$$

$$THD = \left(\frac{1 - 1}{g^2} \right)^{1/2}$$

$$THD = \left[\frac{\pi(\pi - \alpha) - 1}{8 \cos^2 \frac{\alpha}{2}} \right]^{1/2} \quad -\textcircled{5}$$

Active Power -

$$P = V_{S1} I_{S1} \cos \frac{\alpha}{2} = V_o I_o \quad -\textcircled{6}$$

$$= V_m \cdot \frac{2\sqrt{2}}{\pi} I_0 \cos \frac{\alpha}{2} \cos \frac{\alpha}{2}$$

$$= \frac{V_m}{\pi} (1 + \cos \alpha) I_0$$

$$P = V_o I_o$$

Reactive Power -

$$Q = V_{SN} I_{S1} \sin \frac{\alpha}{2} = V_0 I_0 \tan \frac{\alpha}{2} \quad \text{--- (7)}$$

$$Q = P \tan \frac{\alpha}{2}$$

(101)

Harmonics on DC side of converter (V_0)


$$VRF = \sqrt{FF^2 - 1}$$

$$FF = \frac{V_{0N}}{V_0}$$



$$V_{0N} = \frac{V_m}{\sqrt{2K}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$V_0 = \frac{V_m}{\pi} (1 + \cos \alpha)$$

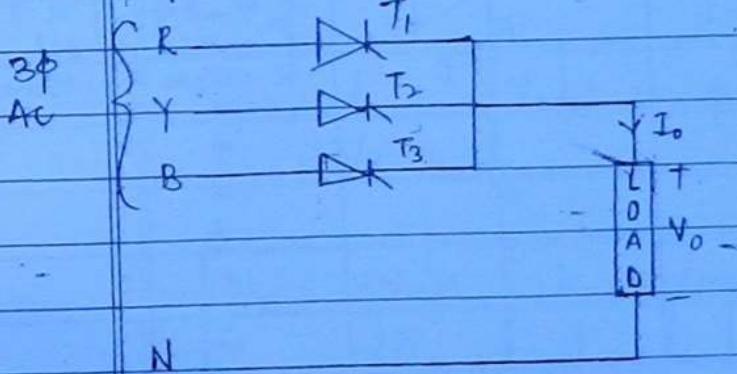3Φ HALF WAVE RECTIFIER (3 pulse converter)



RYB phase sequence

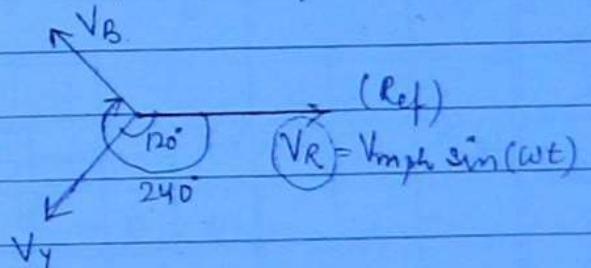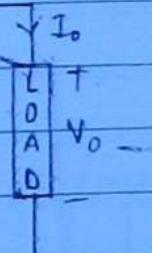





$$I_L = I_{ph} = I_T$$

$$V_{ML} = \sqrt{3} V_{MPH}$$

0° per phase
from cross over point
of thyristor

Date _____
Page _____

102

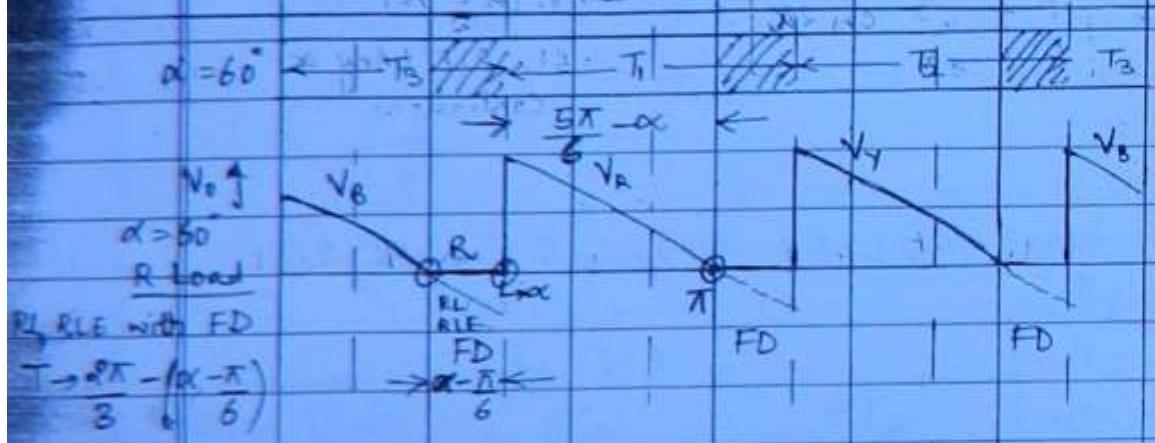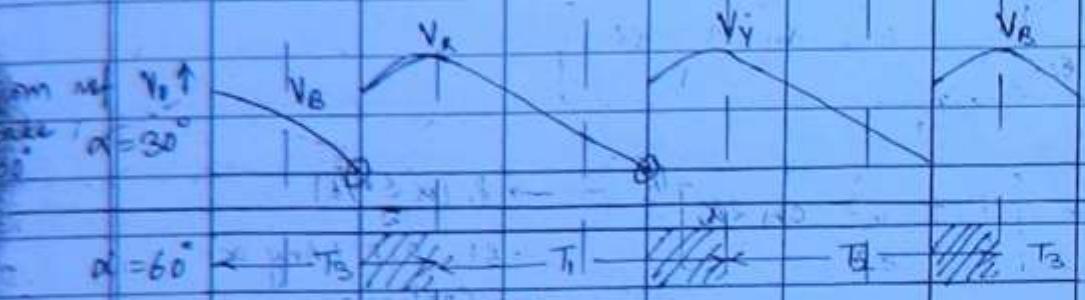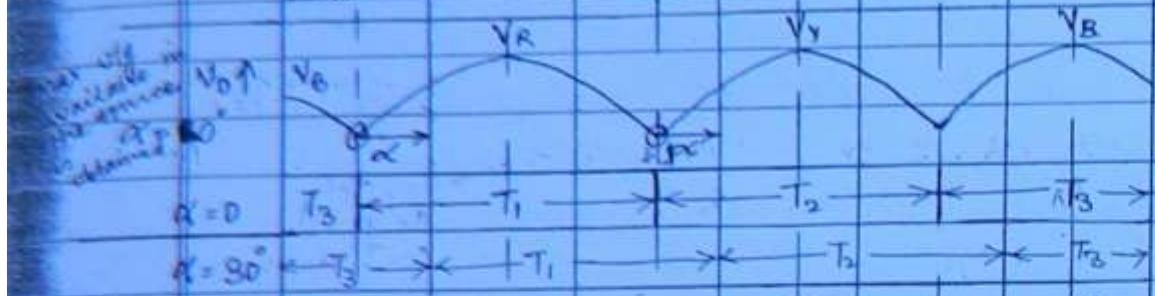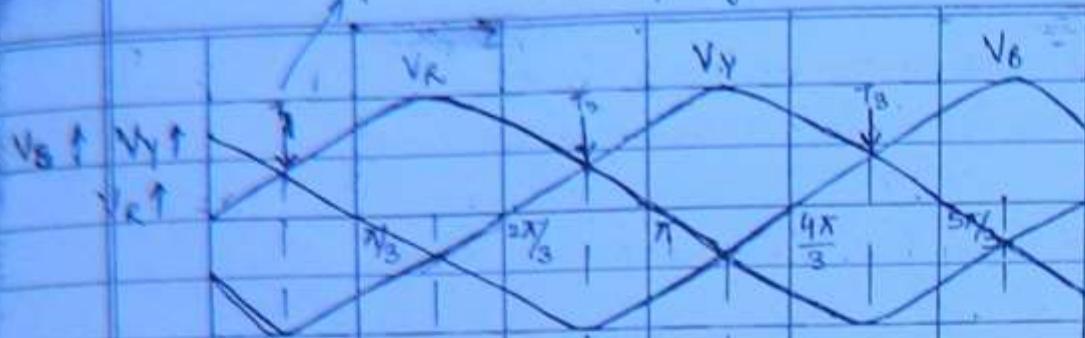


Always output voltage be taken
the max vdg (in which ever
phase it might be)

$$FD \rightarrow (\alpha - \frac{\pi}{6})$$

For Δ load,
upper limit
remains π only
as it's independent
of α . Even if α is
from 60° to 61°
be makes are remove
at π only.

Highly
inductive
w/o FD
 $I_R \uparrow$

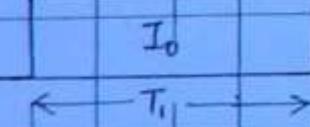

for L load -ve spikes occur.

I $\alpha \leq \frac{\pi}{6}$ \Rightarrow continuous conduction for R_L load

$$V_o = \frac{1}{\frac{2\pi}{3}} \int_{\alpha + \frac{\pi}{6}}^{\alpha + \frac{5\pi}{6}} V_{Mph} \sin(\omega t) d(\omega t)$$

(103)

$$V_o = \frac{3\sqrt{3} V_{Mph}}{2\pi} \cos \alpha = \frac{3V_m}{2\pi} \cos \alpha \rightarrow R, (\alpha \leq \frac{\pi}{6})$$

R_L, R_{LE}

(Any α)

continuous

$$V_{oR} = \left\{ \frac{1}{\frac{2\pi}{3}} \int_{\alpha + \frac{\pi}{6}}^{\alpha + \frac{5\pi}{6}} V_{Mph} \sin^2(\omega t) d(\omega t) \right\}^{1/2}$$

$$V_{oR} = V_{mL} \left[\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2} \rightarrow R, (\alpha \leq \frac{\pi}{6})$$

R_L, R_{LE} (Any α)

continuous

II $\alpha > \frac{\pi}{6}$ \Rightarrow discontinuous conduction for R Load.

$$V_o = \frac{1}{\frac{2\pi}{3}} \int_{\alpha + \frac{\pi}{6}}^{\pi} V_{Mph} \sin(\omega t) d(\omega t)$$

$$V_o = \frac{3V_{Mph}}{2\pi} \left[1 + \cos \left(\alpha + \frac{\pi}{6} \right) \right] \rightarrow R, (\alpha > \frac{\pi}{6})$$

R_L, R_{LE} with FD ($\alpha > \frac{\pi}{6}$)

$$V_{oR} = \left\{ \frac{1}{\frac{2\pi}{3}} \int_{\alpha + \frac{\pi}{6}}^{\pi} V_{Mph} \sin^2(\omega t) d(\omega t) \right\}^{1/2}$$

$$V_{oR} = V_{mL} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin \left(2\alpha + \frac{\pi}{3} \right) \right]^{1/2} \rightarrow R, (\alpha > \frac{\pi}{6})$$

R_L, R_{LE} with
FD ($\alpha > \frac{\pi}{6}$)

Assume highly Inductive Load with FD -

I $\alpha \leq \pi$
6

* FD will not conduct

(104)

∴ conduction angle of each thyristor = $\frac{2\pi}{3}$ i.e. 120°

[for every 2π rad.]

$$V_o \times (I_T)_{avg} = I_0 \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_0}{3}$$

$$(I_L = I_{ph} = I_T)_{avg} = \frac{I_0}{3}$$

$$(I_L = I_{ph} = I_T)_{rms} = \frac{I_0}{\sqrt{3}}$$

II

$$\alpha > \pi$$

6

Conduction angle of FD = $(\alpha - \pi)$ for every $\frac{2\pi/3}{2\pi/3}$ radians.

Conduction angle of each thyristor = $\left(\frac{5\pi}{6} - \alpha \right)$ for every $\frac{2\pi/3}{2\pi/3}$ radians

$$(I_L = I_{ph} = I_T)_{avg} = I_0 \left[\frac{\left(\frac{5\pi}{6} - \alpha \right)}{2\pi} \right]$$

$$(I_L = I_{ph} = I_T)_{rms} = I_0 \left[\frac{\left(\frac{5\pi}{6} - \alpha \right)}{2\pi} \right]^{1/2}$$

$$(I_{FD})_{avg} = I_0 \left[\frac{\left(\alpha - \frac{\pi}{6} \right)}{2\pi/3} \right]$$

$$(I_{FD})_{rms} = I_0 \left[\frac{\left(\alpha - \frac{\pi}{6} \right)}{2\pi/3} \right]^{1/2}$$

Assume highly Inductive Load without FB -
Any α

(105)

Conduction angle of each thyristor = $\frac{2\pi}{3}$ [for every α° rad]

$$(I_L = I_{ph} = I_T)_{avg} = I_0 \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_0}{3}$$

$$(I_L = I_{ph} = I_T)_{rms} = \frac{I_0}{\sqrt{3}}$$

$$\Rightarrow (I_S)_{avg} = \frac{I_0}{3} \text{ (DC comp)}$$

Drawback

The source current contains DC component of
saturates the main supply transformer core

RATINGS OF SCR -

1. $(I_T)_{RMS}$ Rating (RMS Rating of ON state current)
provided by manufacturer

$(I_T)_{RMS}$ Rating $\geq (I_T)_{rms}$ value of in a converter

e.g.

$$1-\phi \text{ full conv } (I_T)_{rms} = \frac{I_0}{\sqrt{2}}$$

$$1-\phi \text{ semi conv } (I_T)_{rms} = I_0 \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$3 \text{ phase } (I_T)_{rms} = \frac{I_0}{\sqrt{3}}$$

$(I_T)_{\text{avg}}$ Rating [Average ON state current rating]

$$(I_T)_{\text{avg}} = \frac{(I_T)_{\text{rms}} \text{ Rating}}{\text{FF}}$$



(106)

FF = form factor of ^{Thyristor} current waveform in a converter

depends on shape of waveform.

CWB chapter 1

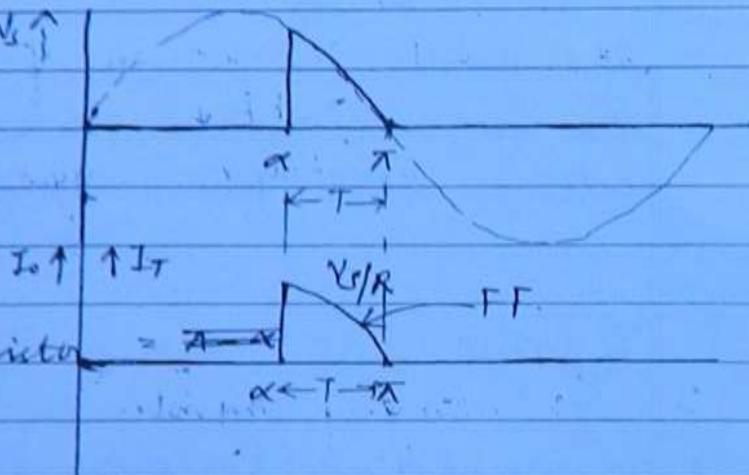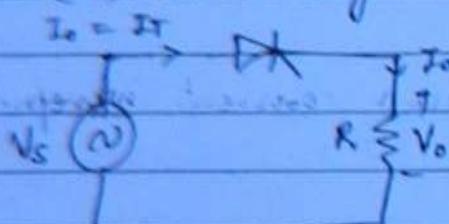Given $(I_T)_{\text{rms}} \text{ Rating} = 35 \text{ A}$



Conduction angle of thyristor

$$\pi - \alpha = 180^\circ - \alpha$$

$$\text{Given } 180^\circ - \alpha = 30^\circ$$

$$\alpha = 150^\circ$$

$$\text{FF} = \frac{(I_T)_{\text{rms}}}{(I_T)_{\text{avg}}} = \frac{I_0 \sqrt{2}}{I_0} = \frac{V_{0\text{R}}/R}{V_0/R} = \frac{V_{0\text{R}}}{V_0}$$

$$\text{FF} = \frac{V_m}{2\sqrt{\pi}} \cdot \left[\frac{\pi - \alpha}{2} + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$

$$\frac{V_m}{2\sqrt{\pi}} [1 + \cos \alpha]$$

$$= \frac{\sqrt{\pi}}{2} \left[\left(\frac{\pi}{6} \right) + \frac{1}{2} \sin \frac{300^\circ}{3} \right]^{\frac{1}{2}} = \frac{\sqrt{\pi}}{2} \cdot 9.98$$

$$[1 + \cos 150^\circ]$$

$$I_{TAV} = \frac{(I_T)_{\text{rms}} \text{ Rating}}{FF} = \frac{35}{3.98} = 8.79 \text{ A}$$

(d)

(107)

Avg rating depends on -

Conduction angle of thyristor

As conduction angle $\uparrow \Rightarrow$ (smoothness of I_T waveform) \uparrow
 $\Rightarrow FF \downarrow$

Thus avg rating of thyristor \uparrow

Load parameters.

e.g. $L \uparrow \Rightarrow$ (smoothness of thyristor current waveform) \uparrow
 $\Rightarrow FF \downarrow$
 (I_{TAV}) Rating of Thyristor \uparrow

$(I^2t$ rating of thyristor)
 provided by manufacturer - to select a proper fuse
 for the thyristor

I^2t rating of thyristor $>$ I^2t rating of fuse

Surge current Rating of Thyristor

i) n cycle surge current rating - (I_{sn})

It's the surge current that the SCR can withstand for n cycles.

at the most

$(I_{sn})^2 n T \frac{1}{2} \leq I^2t$ rating

(ii) one cycle surge current rating (I_{sn})
It is the surge current that the SCR can withstand for one cycle.

$$(I_{s1})^2 \cdot \frac{T}{2} = (I_{sn})^2 \cdot n \frac{T}{2}$$

$$I_{sn} = \sqrt{n} I_{s1}$$

(108)

(iii) Sub-cycle surge current rating ($I_{sn/n}$)
It is the surge current that the SCR can withstand for $1/n$ th period of a cycle.

$$(I_{sn/n})^2 \frac{T}{2 \cdot n} = (I_{s1})^2 \cdot \frac{T}{2}$$

$$I_{sn/n} = \sqrt{n} I_{s1}$$

(iv) Half cycle surge current.

$$I_{s1/2} = \sqrt{2} I_{s1}$$

CWE chapter 1

19

$$I_{sn/n} = 3000$$

$$I_{s1} = \frac{3000}{\sqrt{2}} = 2121.32 \text{ A} \quad (b)$$

21

(c)

CWB chapter 2

(2) (b) -ve spikes are removed.

(3) Half wave rectifier


109

PIV depends on secondary not on primary.

$$V_s = 50\text{V}(\text{rms}) \therefore V_m = 50\sqrt{2}$$

$$\begin{aligned} \text{PIV} &= \alpha V_m = 50\sqrt{2} (2) \\ &= 100\sqrt{2} (\text{a}) \end{aligned}$$

(4)

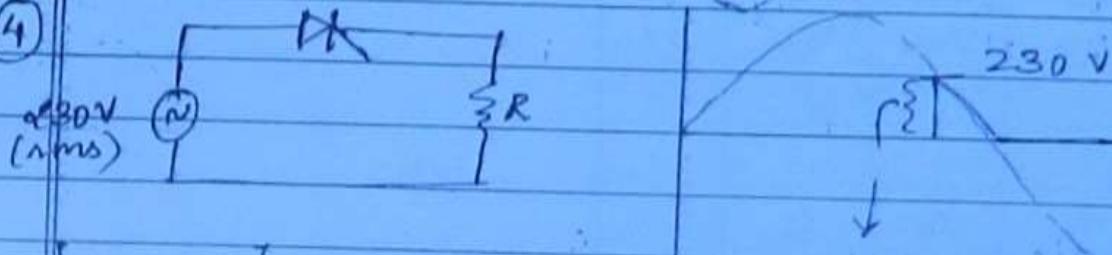

$$V_o (\text{wt})_{\text{peak}} = 230\text{V}$$

$$V_m \sin \alpha = 230^\circ$$

$$230\sqrt{2} \sin \alpha = 230^\circ$$

$$\sin \alpha = \frac{1}{\sqrt{2}}$$

V_o for $\alpha \leq 90^\circ$


$$V_m = 230\sqrt{2} \quad X$$

So $\alpha > 90^\circ$

$$\alpha = \cancel{45^\circ}, 135^\circ$$

Ans (b)

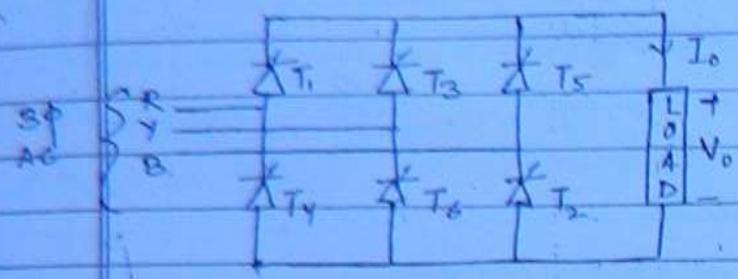3φ Fully Controlled Rectifier (6 pulse converter)



$V_{BR} \rightarrow V_{BY}$

(REF)




$$V_{RY} = V_{ML} \sin \alpha$$

110



V_{YR}

V_{YB}


V_{RB}

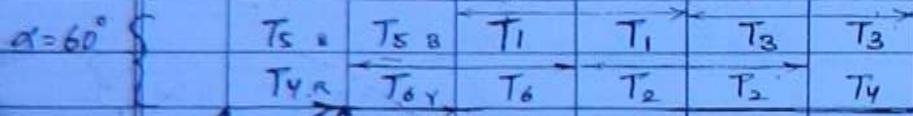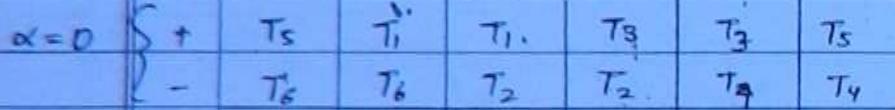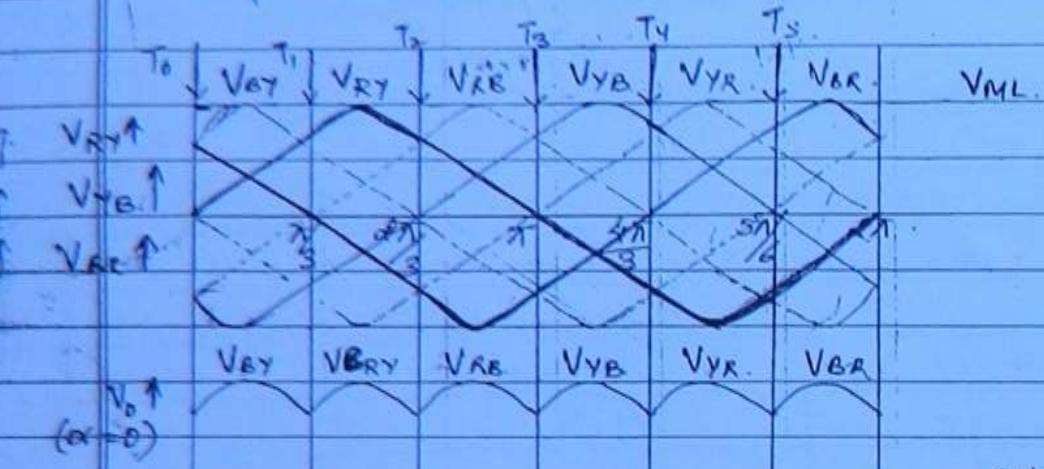

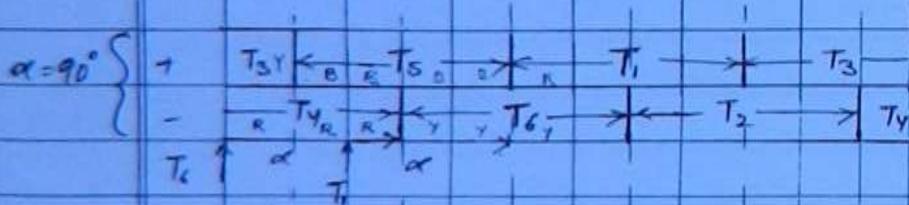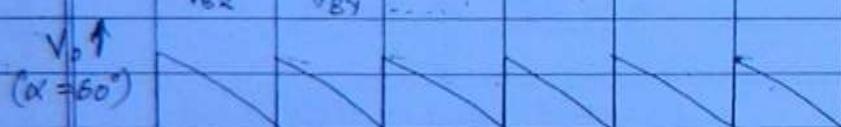count α from
crossover pt
+ T_1, T_2, T_5 { seq. remains
- T_4, T_6, T_2 } same.



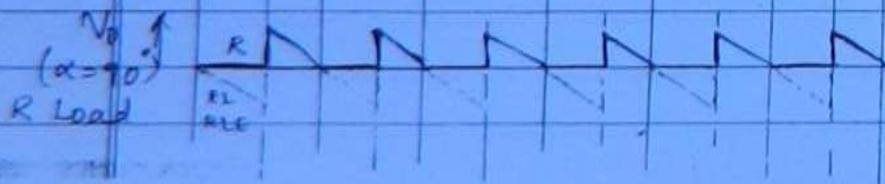$V_{YB}, V_{BR}, V_B, V_{RY}, V_{RB}, V_{YE}, V_{YR}$



$T_2 \rightarrow ON$

$$V_{T1} = V_{RY}$$

$T_5 \rightarrow ON$

$$V_{T1} \rightarrow V_{RE}$$

RL, RLE
Highly
Inductive

(II)

$I_R \uparrow$

$B \times V$

I_0

I_o

V_{RY}

WT_B



I_o

V_{RE}

$V_{T1} \uparrow$
($\alpha = 0$)

$I(\alpha < 60^\circ) \uparrow$
 $\alpha = 20^\circ$

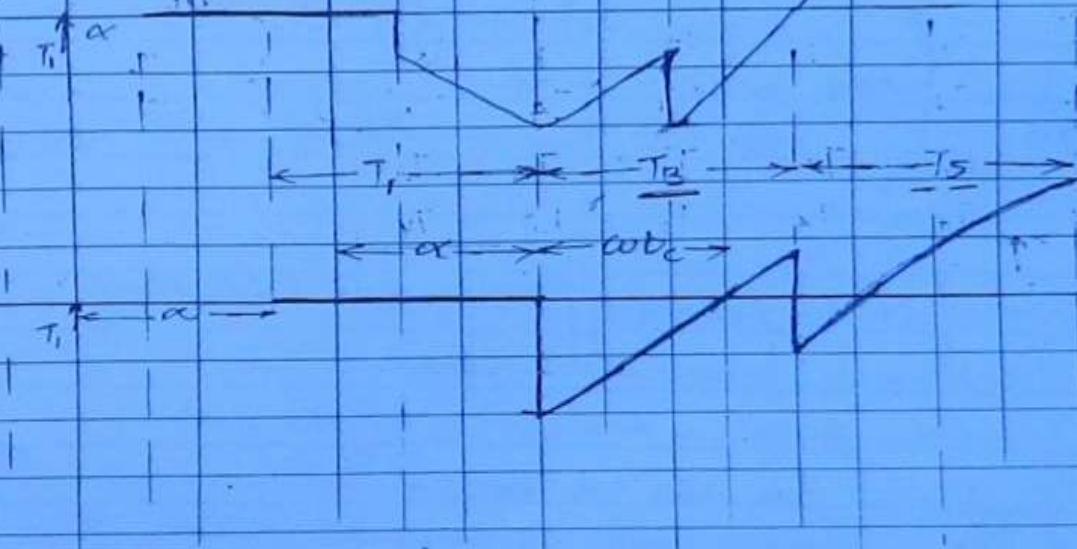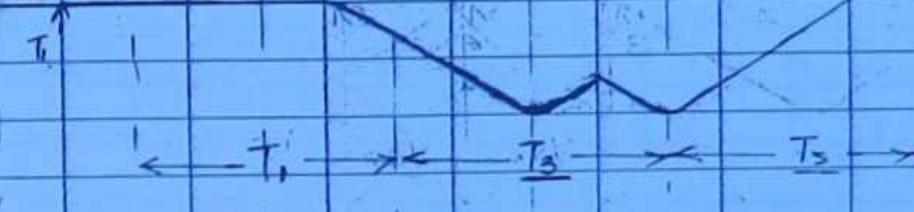II ($\alpha \geq 60^\circ$)
 $\alpha = 90^\circ$



$$\alpha < \frac{\pi}{3} \rightarrow \text{continuous conduction for R load}$$

$\alpha + \frac{2\pi}{3}$

$$V_o = \frac{1}{\frac{\pi}{3}} \int_{\alpha + \frac{2\pi}{3}}^{V_{ML} \sin \omega t} d(\omega t)$$

$V_o = \frac{3V_{ML} \cos \alpha}{\pi}$	$\rightarrow R (\alpha \leq \frac{\pi}{3})$
---	---

$\rightarrow RL, RLF (\text{Any } \alpha)$
continuous

(112)

$$V_{oR} = \left\{ \frac{1}{\frac{\pi}{3}} \int_{\alpha + \frac{2\pi}{3}}^{V_{ML} \sin^2 \omega t} d(\omega t) \right\}^{\frac{\pi}{2}}$$

$$= \frac{3}{2\pi} V_{ML} \left\{ \frac{\pi}{3} + \frac{1}{2} \left[\sin \left(\omega \alpha + \frac{\omega \pi}{3} \right) - \sin \left(2\alpha + \frac{4\pi}{3} \right) \right] \right\}^{\frac{\pi}{2}}$$

$\alpha > \frac{\pi}{3} \rightarrow \text{discontinuous conduction for R load -}$

$$V_o = \frac{1}{\frac{\pi}{3}} \int_{\alpha + \frac{2\pi}{3}}^{V_{ML} \sin \omega t} d\omega t$$

$$V_o = \frac{3V_{ML}}{\pi} \left[1 + \cos \left(\alpha + \frac{\pi}{3} \right) \right] \rightarrow R (\alpha > \frac{\pi}{3})$$

$$V_{oR} = \left\{ \frac{1}{\frac{\pi}{3}} \int_{\alpha + \frac{2\pi}{3}}^{V_{ML} \sin^2 \omega t} d\omega t \right\}^{\frac{\pi}{2}}$$

$$= \frac{3}{2\pi} V_{ML} \left\{ \left(\frac{2\pi}{3} - \alpha \right) + \frac{1}{2} \sin \left(2\alpha + \frac{2\pi}{3} \right) \right\}^{\frac{\pi}{2}} \rightarrow R (\alpha > \frac{\pi}{3})$$

Assume highly inductive load - (RL, RLE)

Conduction angle of each thyristor = $2\pi/3$ (for every 3, 2π rad)

$$(I_T)_{avg} = I_0 \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_0}{3}$$

(T13)

$$(I_T)_{rms} = \frac{I_0}{\sqrt{3}}$$

$$(I_R)_{rms} = I_0 \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$I_{SR} = (I_R)_{rms} = I_0 \sqrt{\frac{2}{3}}$$

Harmonic Analysis on AC side of converter
for source current (I_S) waveform.

$$I_S = \sum_{n=1,3,5}^{\infty} \frac{4I_0}{n\pi} \sin \frac{n\pi}{3} \sin(n\omega t + \phi_n)$$

\downarrow
 $n = 6K \pm 1$

Since $\sin \frac{3\pi}{3} = 0$ so 3rd harmonic & multiples of 3 harmonics (triple harmonics) are absent. So are even harmonics

NOTE: Even & triple harmonics are absent

$$\phi_n = -n\alpha \quad \phi_1 = -\alpha$$

$$(I_{Sn})_{rms} = \frac{4\sqrt{2}}{n\pi} I_0 \sin \frac{n\pi}{3}$$

$$(I_{S1})_{rms} = \frac{2\sqrt{2}}{\pi} I_0 \sin \frac{\pi}{3}$$

$$(I_{S1})_{\text{rms}} = \frac{\sqrt{6}}{\pi} I_0 \quad - (1)$$

$$\text{FDF} = \cos \phi_1$$

$$\text{FDF} = \cos \alpha \quad - (2)$$

$$g = (I_{S1})_{\text{rms}} = \frac{\sqrt{6}}{\pi} \cdot I_0$$

(174)

$$\frac{I_{S1}}{I_{SN}} = \frac{I_0}{\sqrt{\frac{2}{3}}}.$$

$$g = \frac{3}{\pi} \quad - (3)$$

$$\text{THD} = \left(\frac{1}{g^2} - 1 \right)^{\frac{1}{2}} = \left(\frac{\pi^2}{9} - 1 \right)^{\frac{1}{2}}$$

$$\text{THD} = 31\% \quad - (4)$$

$m \uparrow \text{ THD} \downarrow \therefore \text{harmonics} \downarrow$

$$\text{PF} = g (\text{FDF})$$

$$\text{PF} = \frac{3}{\pi} \cos \alpha \quad - (5)$$

$$\text{Active power } P \Rightarrow \sqrt{3} V_{SN} I_{S1} \cos \alpha \quad - (6)$$

$$= \sqrt{3} V_{ML} \frac{\sqrt{6}}{\pi} I_0 \cos \alpha$$

$$= \frac{3 V_{ML}}{\pi} \cos \alpha \cdot I_0 = V_o I_o \cos \alpha$$

$$\text{Reactive power } Q = \sqrt{3} V_{SN} I_{S1} \sin \alpha = V_o I_o \sin \alpha \quad - (7)$$

$$= P \tan \alpha$$

To find t_c & PIV across thyristor we need to plot V_T .



$$T_1 \rightarrow ON \quad V_T = 0$$

$$T_3 \rightarrow ON \quad V_T = V_{RE}$$

$$T_F \rightarrow ON \quad V_T = V_{RB}$$

$$\omega t_c = \frac{4\pi}{3} \quad t_c = \frac{4\pi}{3\omega} \text{ sec.}$$

(I) $\alpha < 60^\circ$

~~$$\alpha + \omega t_c = \frac{4\pi}{3}$$~~

$$\omega t_c = \frac{4\pi}{3} - \alpha$$

$$t_c = \frac{4\pi}{3} - \alpha$$

w.


(II) $\alpha \geq 60^\circ$

~~$$\alpha + \omega t_c = \pi$$~~

$$\omega t_c = \pi - \alpha$$

$$t_c = \frac{\pi - \alpha}{\omega} \text{ sec.}$$

3 pulse converter -

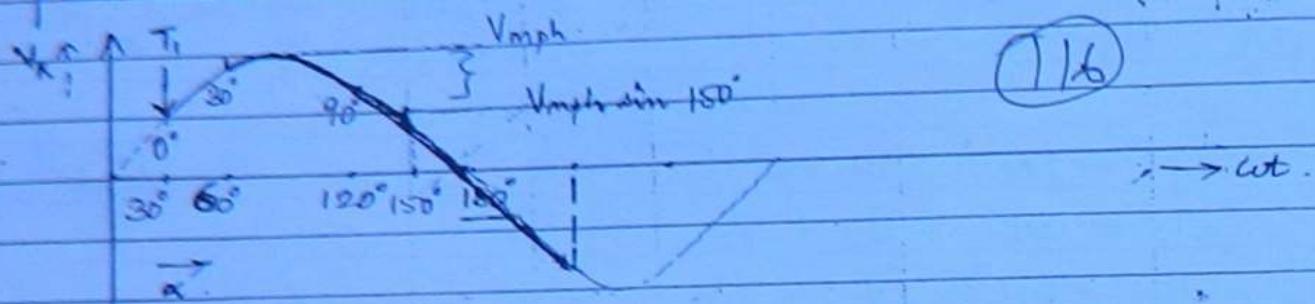

(116)

$$\alpha = wt - 30^\circ$$

$$\text{Length of pulse} = \frac{\alpha \pi}{3} = 120^\circ$$

$$0 \leq \alpha \leq 150^\circ$$


$\rightarrow R$ load.

$$0 \leq \alpha \leq 180^\circ$$

\rightarrow Inductive Load

~~3 pulse converter~~

V_M

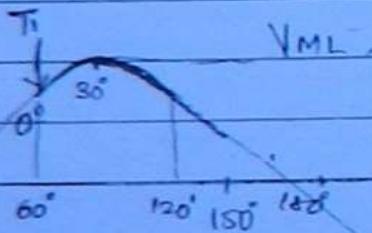

$$\alpha = wt - 60^\circ$$

$$\text{Length of pulse} = \frac{\pi}{3} \\ = 60^\circ$$

for R load $\rightarrow 0 \leq \alpha \leq$




RL, RLE load $\rightarrow 0 \leq \alpha \leq 150^\circ$


CWB chapter 2

$$\begin{aligned} ① \text{ Peak to peak vlg ripple} &= \frac{V_{ML} - V_{ML \sin 150^\circ}}{V_{ML}} \\ &= 1 - \sin 150^\circ \\ &= 0.5 \quad (\text{a}) \end{aligned}$$

3φ Half Controlled Rectifier


112

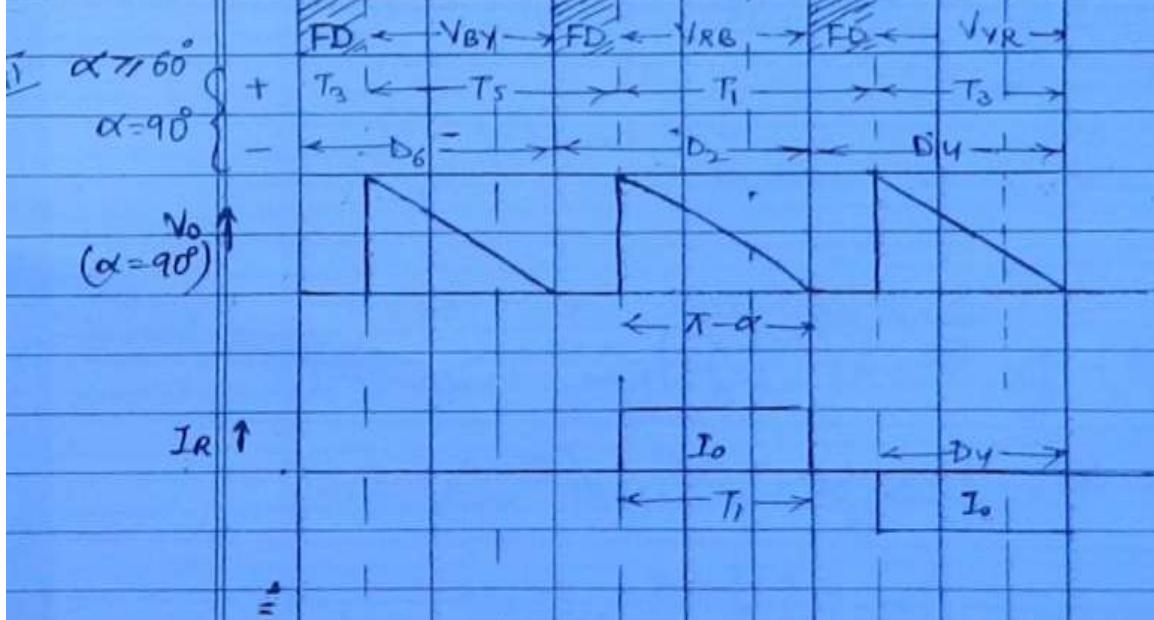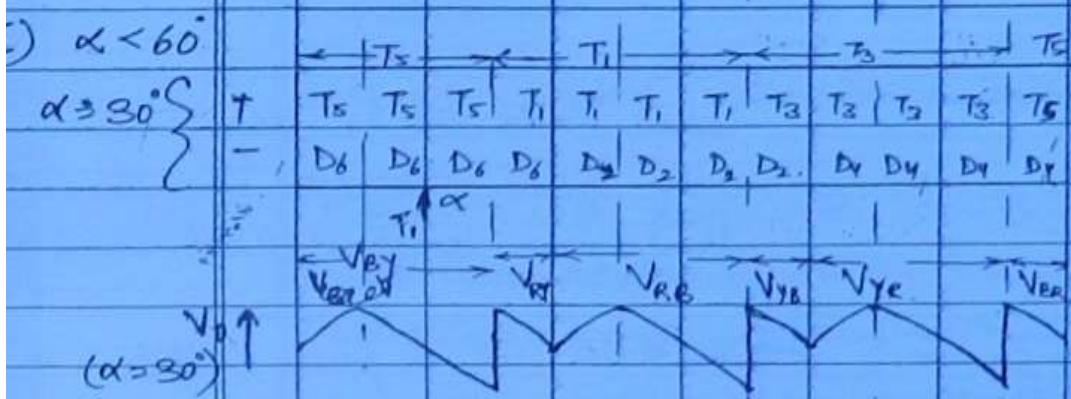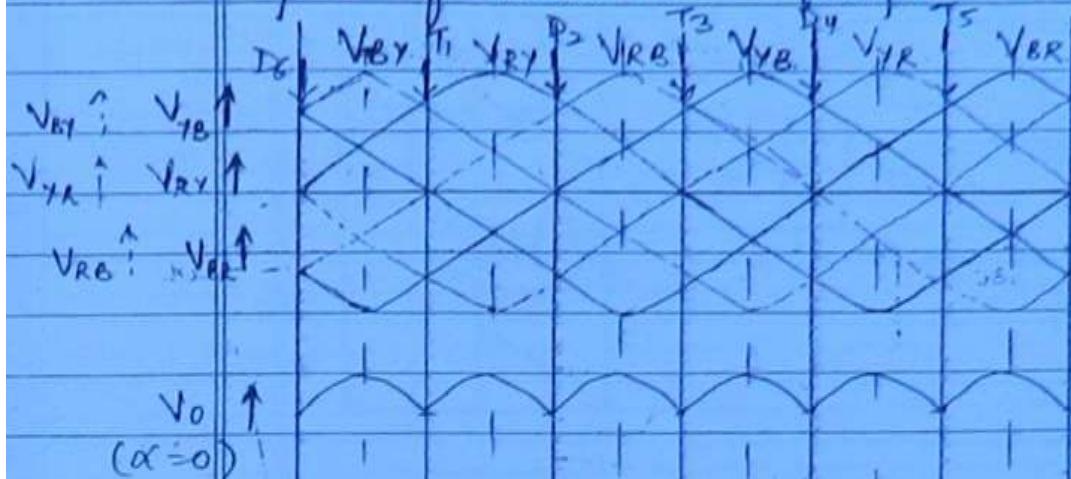

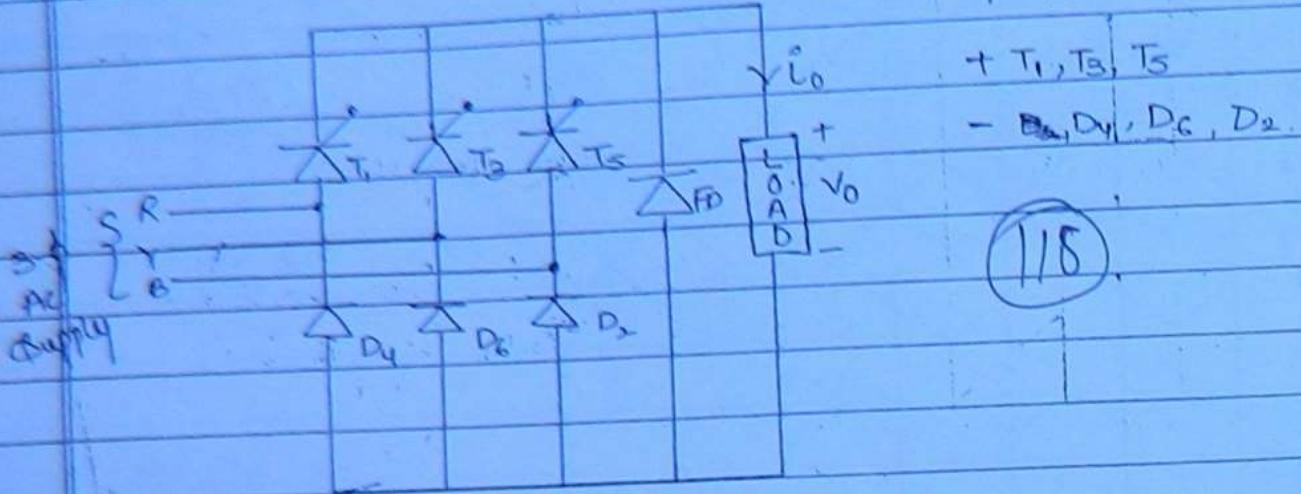

Short method - 1 mark
 $I \quad \alpha < 60^\circ$ FD will not conduct.

Take $V_0 (\alpha=0)$ as ref

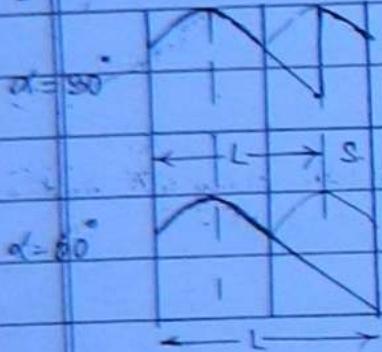

$$\rightarrow S = 60 - \alpha \\ = 60 - 60 \\ = 0$$

★	$\alpha < 60^\circ \Rightarrow 6 \text{ pulse}$	<u>IES</u>
	$\alpha \geq 60^\circ \Rightarrow 3 \text{ pulse.}$	

For $\alpha < 60^\circ$ FD will not conduct.

for $\alpha \geq 60^\circ$

conduction period of FD $= \left(\alpha - \frac{\pi}{3}\right)$ radians

conduction period of thyristor $= \frac{2\pi}{3} - \left(\alpha - \frac{\pi}{3}\right)$

$$= \pi - \alpha$$

\therefore Length of pulse $= \pi - \alpha$


(T19)

Take V_o ($\alpha = 60^\circ$) as ref

$$FD \rightarrow \alpha - \pi/3$$

$$\text{Pulse length} = \pi - \alpha$$

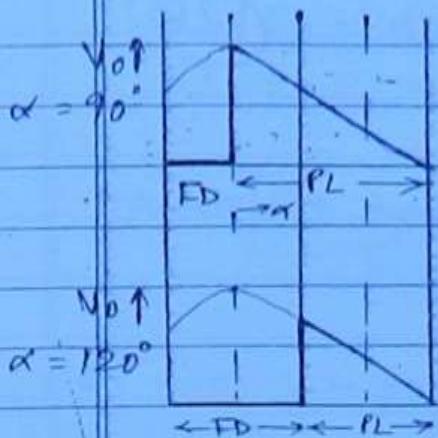$\Delta \alpha \uparrow$ Free wheeling \uparrow
 Pulse length \downarrow



Assume Highly Inductive Load

 $\alpha \leq 60^\circ$ FD will not conductConduction angle of FD $\alpha = \pi - \alpha - \pi/3$ Conduction angle of thyristor $= \frac{2\pi}{3}$ rad (for every $\alpha \pi$ radian)

$$(I_T)_{avg} = I_0 \left(\frac{\pi/3}{2\pi} \right) = \frac{I_0}{6}$$

$$(I_T)_{rms} = \frac{I_0}{\sqrt{3}}$$

$$I_{Sh} = I_0 \sqrt{\frac{2}{3}}$$

 $\alpha > 60^\circ$ FD will conductConduction angle of FD $= \alpha - \frac{\pi}{3}$ (for every $\frac{9\pi}{3}$ rad)Conduction angle of thyristor $= \pi - \alpha$ (for every $\alpha \pi$ rad)

$$(I_T)_{avg} = I_0 \left(\frac{\pi - \alpha}{\alpha \pi} \right)$$


$$(I_T)_{rms} = I_0 \left(\frac{\pi - \alpha}{\alpha \pi} \right)^{1/2}$$

$$I_{Sh} = I_0 / \left(\frac{\pi - \alpha}{\alpha} \right)^{1/2}$$

$$V_o = \frac{3V_m L}{2\pi} (1 + \cos \alpha)$$


(12a)

Representation of semi-converter.

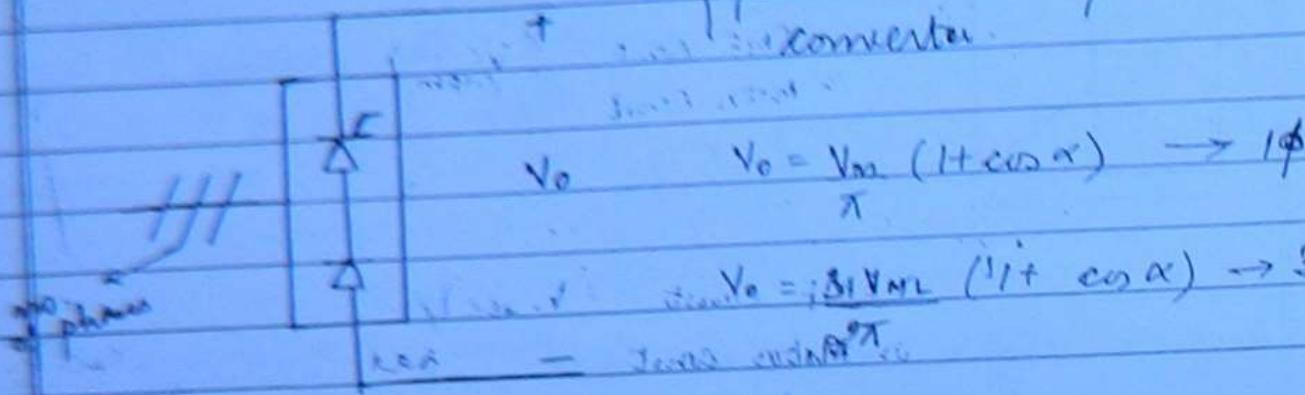

$$V_o = \frac{3V_m L}{2\pi} (1 + \cos \alpha) \rightarrow 3\phi$$


Representation of full converter.

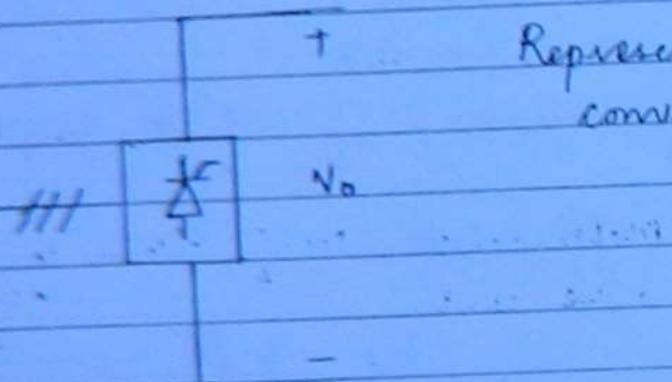

APPLICATIONS -

DC Drives -

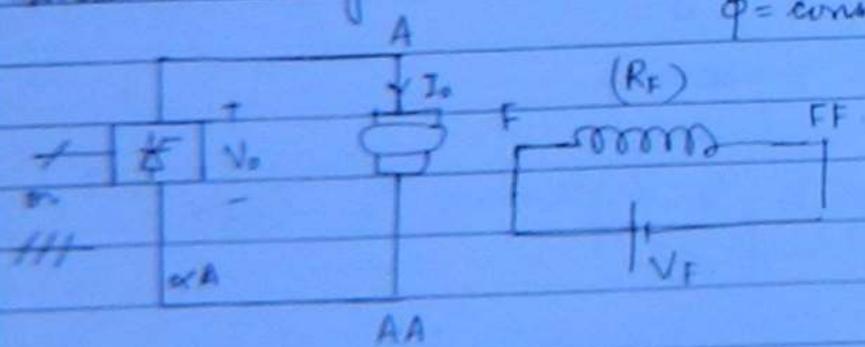I Armature Voltage Control ($\omega < \omega_n$)
 $\phi = \text{const}$



$$1\phi \quad V_o = d V_m \cos \alpha_A$$

$$E_b \propto \phi N$$

$$E \propto N \quad (\because \phi = \text{const})$$

(121)

$$\boxed{E = KN}$$

\rightarrow EMF const. (V/rpm)

or Motor const

$$\boxed{E = KCU}$$

\rightarrow EMF const. $(V/\text{sec})/\text{rad}$

or Motor const

$$T_a \propto \phi I_o$$

$$T_a \propto I_o \quad (\phi = \text{const})$$

$$\boxed{T_a = K_i I_o} \rightarrow I_o = T_a/K$$

\rightarrow Motor const $NM/A = (V \cdot \text{sec})/\text{rad}$

or Torque const

$$\omega = \frac{\theta}{t} \times N$$

60

$$N \rightarrow \text{rpm}$$

$$\omega \rightarrow \text{rad/sec}$$

For Motoring Mode

$$V_o = E_b + I_o R_a$$

$$V_o = K\omega + I_o R_a$$


$$\omega = \frac{V_o}{K} - \frac{I_o R_a}{K}$$

$$\boxed{\omega = \frac{V_o}{K} - \frac{R_a T_a}{K}}$$

$R_a \uparrow \quad V_o \downarrow \quad \therefore \omega \downarrow \quad (\omega \propto V_o)$

(1) Field Control Method ($\omega_F > \omega_N$)

(122)

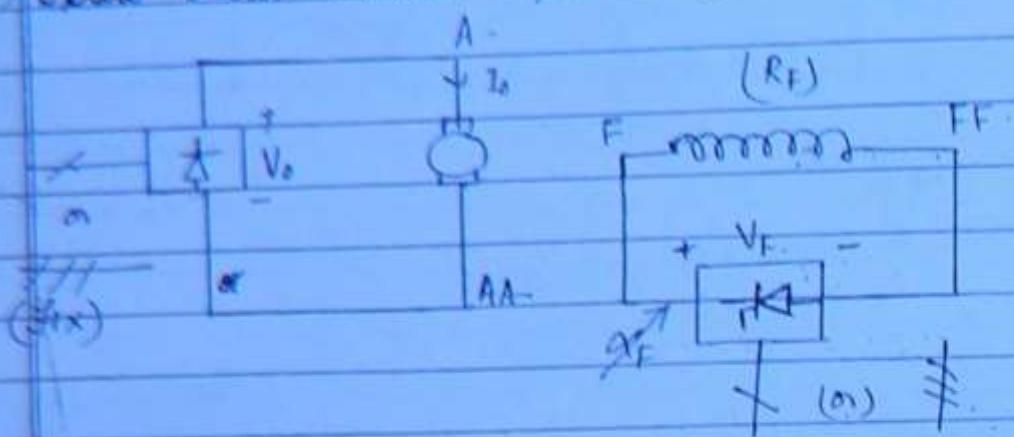

$$1) \frac{V_F}{\pi} = \alpha V_m \cos \alpha F$$

$$I_F = \frac{V_F}{R_F}$$

$$2) \frac{V_F}{\pi} = 3V_{ML} \cos \alpha F$$

$$\phi \propto I_F$$

$$E_b \propto \phi N \propto (K_F I_F) N$$

$$E_b = K_1 (K_F I_F) N$$

$$E = \underbrace{K_I}_{\text{EMF const}} I_F N$$

\rightarrow EMF const $V/\text{rpm. A}$
or Motor const

$$E = \underbrace{K_I}_{\text{EMF const}} I_F \omega$$

\rightarrow EMF const $\frac{V \cdot \text{sec}/}{\text{rad. A}}$
or Motor const

$$T_a \propto \phi I_o$$

$$T_a = K_I I_F I_o$$

$$T_a = \underbrace{K_I}_{\text{Motor const}} I_F I_o \rightarrow I_o = \frac{T_a}{K_I}$$

\rightarrow Motor const $\frac{V \cdot \text{sec}/}{\text{rad. A}}$
or Torque const

$$\omega = \frac{aTN}{60}$$

(123)

for Motoring Mode


$$V_o = E_b + I_o R_a$$

$$V_o = K_i F \omega + I_o R_a$$

$$\omega = \frac{V_o - I_o R_a}{K_i F + K_i F}$$

$$\omega = \frac{V_o - R_a T_a}{K_i F^2 (K_i F)^2}$$


$$\alpha_f \uparrow V_f \downarrow \Rightarrow I_f \downarrow \Rightarrow \omega_o > \omega_n$$

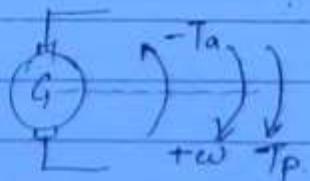for Motoring Mode \Rightarrow Torque developed is in same dirⁿ as speedCurrent enters at +ve terminal of back emf
so that electrical effect absorbed is transformed in mech. energy.for Generating Mode \Rightarrow Torque developed if speed in opp dirⁿ

Four Modes of DC M/C -

We can utilize DC m/c in 4 modes


124

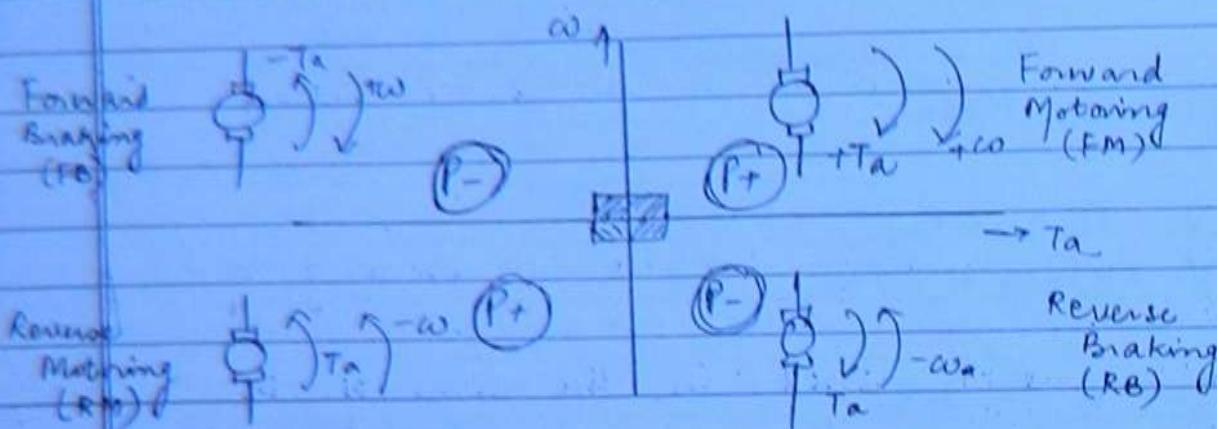


Quadrant Operation of Full converter - (Two Quadrant Operation)

$$1\phi, V_o = \frac{\pi}{2} V_m \cos \alpha \quad \alpha < 90^\circ \quad V_o + \\ \pi \quad \alpha > 90^\circ \quad V_o -$$

$$3\phi, V_o = 3V_{ML} \cos \alpha$$

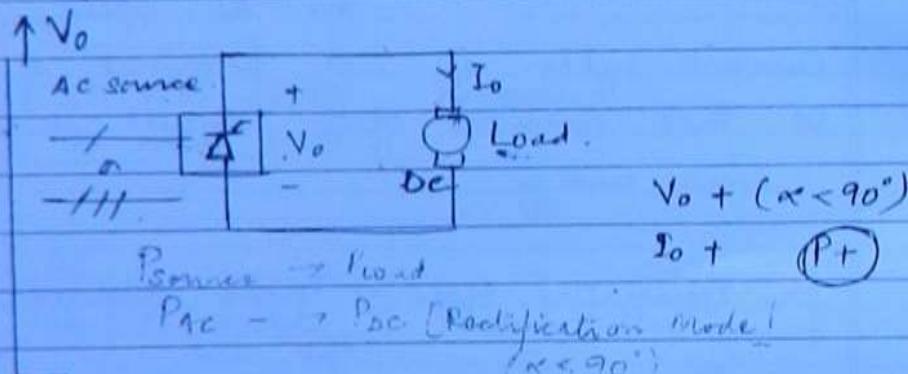

I_o (always) +

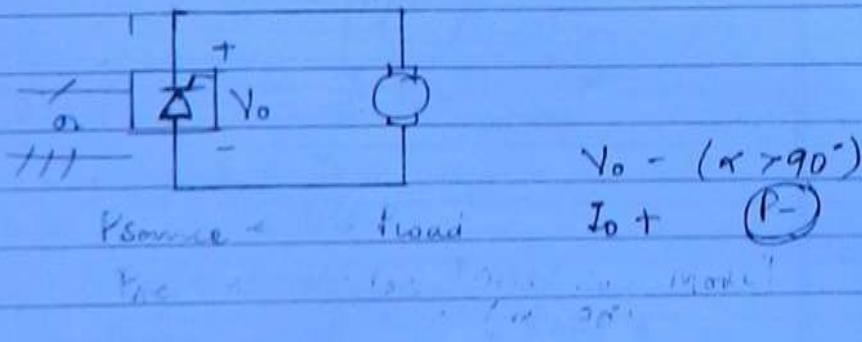

Rectification Mode -



(T25)

- can be used for motoring mode of a DC m/c.
- can also be used to charge a battery.

Inversion Mode

- can be used for regenerative braking of DC m/c.
- solar energy stored in the form of DC can be given to the AC side of utility system where the converter is operating in (inversion) mode.

Full converter feeding DC m/c -

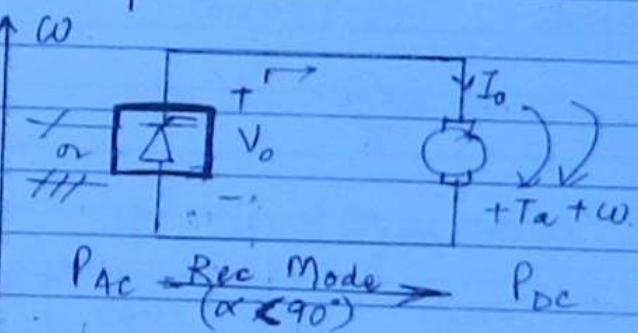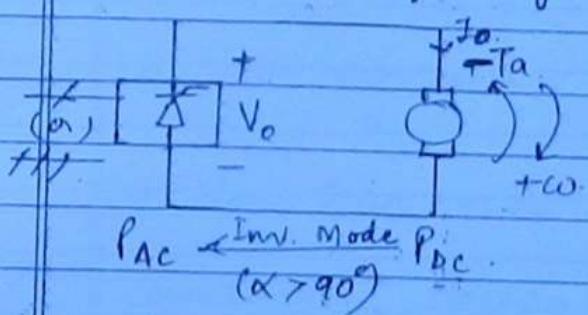

$\frac{P_{AC}}{P_{DC}}$ ← Braking Energy
(Regenerative Braking)

Converter will support the inversion if $\alpha > 90^\circ$
Load supports inversion if emf is having ability to deliver power.

$$\alpha < 90^\circ \quad V_o + E_b + \frac{d}{dt} W + I_a + \frac{d}{dt} T_a +$$

$$T_a \rightarrow \phi I_a$$

Converter will support the rectification if $\alpha < 90^\circ$
Load supports rectification if emf is having ability to absorb the power

$$V_o = -E_b + I_o R_a$$

$$V_o = E_b + I_o R_a$$

$$\omega = \frac{\alpha^2 V_m \cos \alpha}{\pi K} - \frac{R_a T_a}{K^2} \rightarrow 1\phi$$

(26)

$$\omega = \frac{3 V_m L \cos \alpha}{\pi K} - \frac{R_a T_a}{K^2} \rightarrow 3\phi$$

$$T_a + \omega t \therefore \textcircled{P+} \quad (\phi+)$$

Quadrant Operation of Semi converter
Supports

DUAL CONVERTER (Four Quadrant Operation)


(T27)

i) Non-Circulating Current Type -

In non-circulating current type dual converter, if one converter is in the ON state then other converter is in the OFF state.

Advantage -

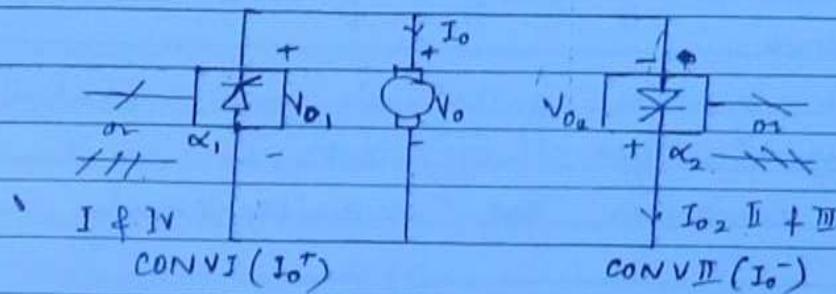There is no circulating current b/w the converters.



$$1\phi, V_{o1} = \frac{2V_m \cos \alpha_1}{\pi}$$





$$1\phi, V_{o2} = \frac{2V_m \cos \alpha_2}{\pi}$$

$$3\phi, V_{o1} = \frac{3V_m \cos \alpha_1}{\pi}$$

$$3\phi, V_{o2} = \frac{3V_m \cos \alpha_2}{\pi}$$

CONV I → OFF CONV II → ON
 $\alpha_2 > 90^\circ$ V_{o2-}, V_o+ $T_a \rightarrow \dot{\phi} I_o \therefore T_a+$ $E_b \rightarrow \dot{\phi} \omega \therefore E_b+$

RB

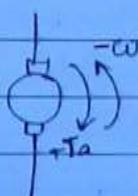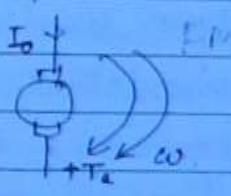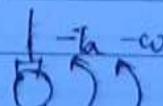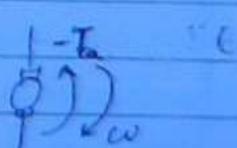CONV I → ON CONV II → OFF
 $\alpha_1 < 90^\circ$ $V_{o1+}, V_o+, E_b+, C_o+$ I_a+, T_a+, I_o+ CONV I → OFF CONV II → ON
 $\alpha_2 < 90^\circ$
 $(\dot{\phi}-) P_{RB-} \xrightarrow{RM} V_o+$
 $(\dot{\phi}+) P_{RB+} \xrightarrow{RM} I_o+$
 $(\dot{\phi}+) P_{FB+} \xrightarrow{RM} V_o- \xrightarrow{FB} I_o-$
 $(\dot{\phi}-) P_{FB-} \xrightarrow{RM} V_o+ \xrightarrow{FB} I_o+$
CONV I → ON CONV II → OFF $\rightarrow I_o$ RM $V_{o2+}, V_o-, E_b-, \omega-, I_o-, T_a-, I_o-$ $\dot{\phi} \omega$  V_{o1-}, V_o-, I_o+ $T_a \rightarrow \dot{\phi} I_o \rightarrow \therefore T_a = -ve$ 

Disadvantage -

- It gives slow speed response of the reversal of armature current if not smooth during switching transition of the converter.



We must provide commutation delay time (Δt_d) to the outgoing converter before the incoming converter is switched ON to avoid high circulating current during switching transitions of converter. This commutation delay time is responsible for slow speed response.


(ii) Circulating Current Type -

Here, both the converters are simultaneously in the ON state.

Disadvantage -

There will be circulating current b/w the converters & hence responsible for additional power loss.

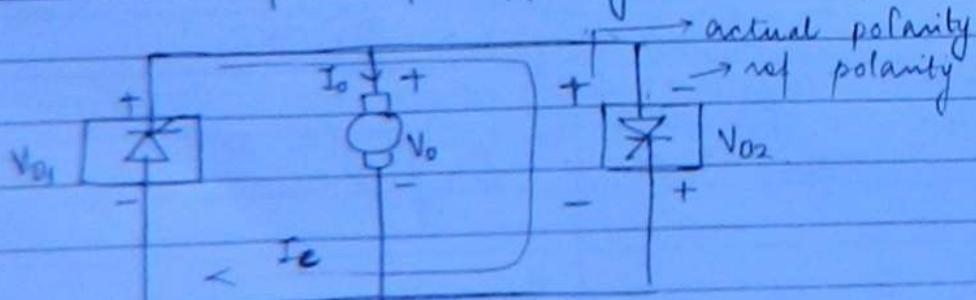Circulating current is due to the voltage difference b/w the two converters. We can reduce the circulating current if the output voltages of the converters are equal & opposing each other.



$$I_C \downarrow \rightarrow N_{D1} = -V_{D2} \quad \alpha_1 + \alpha_2 = 180^\circ$$

$$\frac{2V_m \cos \alpha_1}{\pi} = - \frac{2V_m \cos \alpha_2}{\pi}$$

(129)


$$\cos \alpha_1 + \cos \alpha_2 = 0$$

$$\alpha_2 = 180 - \alpha_1$$

$$\alpha_1 + \alpha_2 = 180^\circ$$

Even after maintaining $\alpha_1 + \alpha_2 = 180^\circ$, still there is some circulating current due to the instantaneous voltage difference b/w the converters.

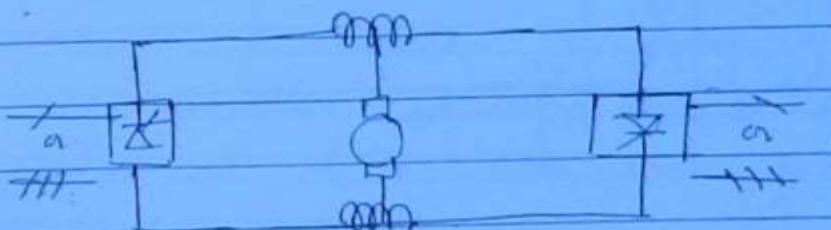- * To reduce this circulating current, we must connect a ~~reactive power~~ ^{reactor core} b/w the converters as shown.




- * In order to satisfy the relation $\alpha_1 + \alpha_2 = 180^\circ$ if one converter is operating in rectification mode then other converter must work in inversion mode.

Advantage -

It gives high speed response & the reversal of armature current is smooth during switching transition of converters.

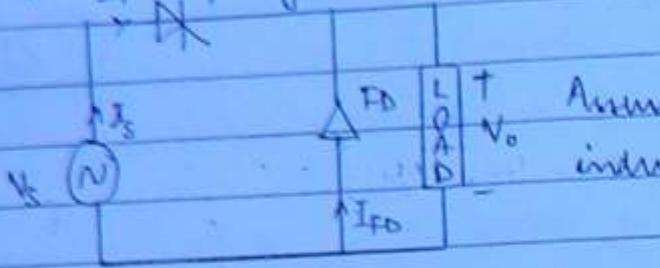Effect of Source Inductance (L_s) on one Pulse Converter




(135)


Assume highly
inductive load

Without $L_s \rightarrow V_0 = \frac{V_m}{2\pi} (1 + \cos \alpha)$

Reduction in vfg due to L_s .

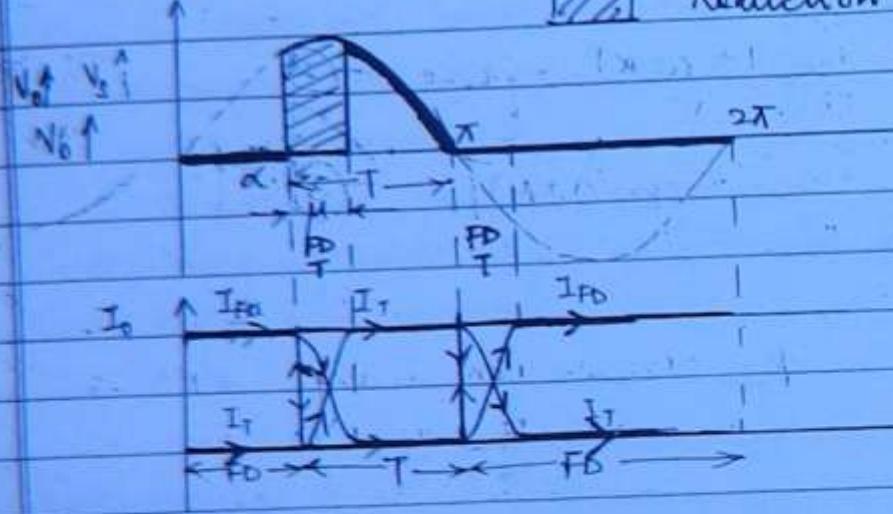

With L_s

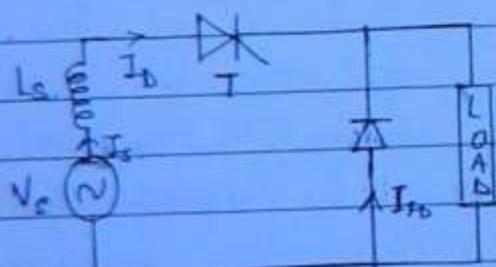

μ = overlap period

During overlap period both T & F_D are not
exchanging load current thus $v_{fg} = 0$

During Overlap \Rightarrow F_D & T \rightarrow ON $V_0 = 0$

$$V_S = L_s \frac{dI_S}{dt}$$

$\omega + \mu$ at merge I_0

$$\frac{V_m}{2} [\cos \alpha - \cos(\alpha + \mu)] = \omega L_s I_o$$

divide to give
avg reduction
in v/g.

(131)

$$\Delta V_{do} = \frac{V_m}{2\pi} [\cos \alpha - \cos(\alpha + \mu)] = \frac{\omega L_s I_o}{2\pi} = f L_s I_o \quad (1)$$

ΔV_{do} = Avg reduction in V_o due to L_s .

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha) - f L_s I_o \quad (2)$$

$$V_o = \frac{V_m}{2\pi} [1 + \cos(\alpha + \mu)] \quad (3)$$

* Overlap angle μ depends on fixing angle α
but avg reduction in v/g due to source
inductance ie ΔV_{do} does not depend on
fixing angle α .


* Avg reduction in v/g due to source inductance
depends upon frequency, L_s , f , I_o

* If $f \uparrow$ or $L_s \uparrow$ or $I_o \uparrow$ w/o changing V_s , f , α
then μ also \uparrow .

If $V_s \uparrow$ w/o changing f , L_s , I_o , f , α then $\mu \downarrow$
 \downarrow due to \uparrow in V_s height of pulse \uparrow so
maintain same area ΔV_{do} the width $\uparrow \downarrow$. Thus $\mu \downarrow$



Effect of Source Inductance for Two Pulse Converter

(132)

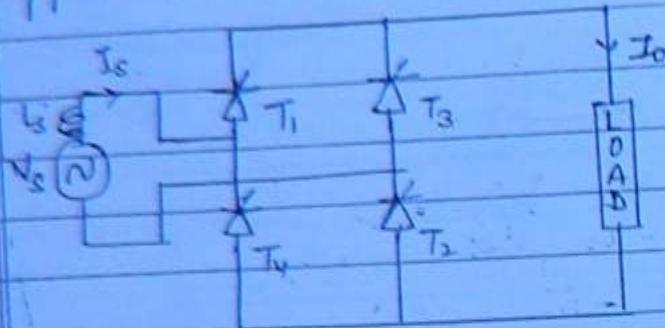

$$V_{d0} = \frac{\alpha N_m}{\pi} \text{ (max dc o/p voltage)}$$

Without L_s

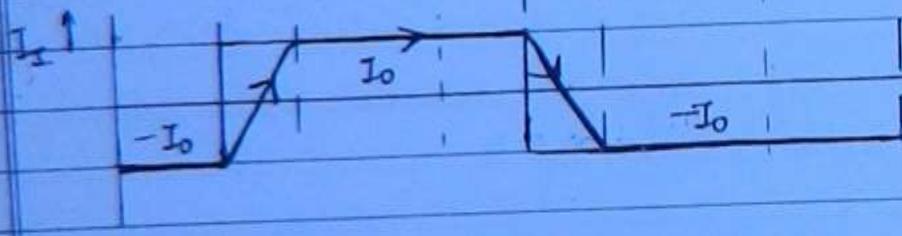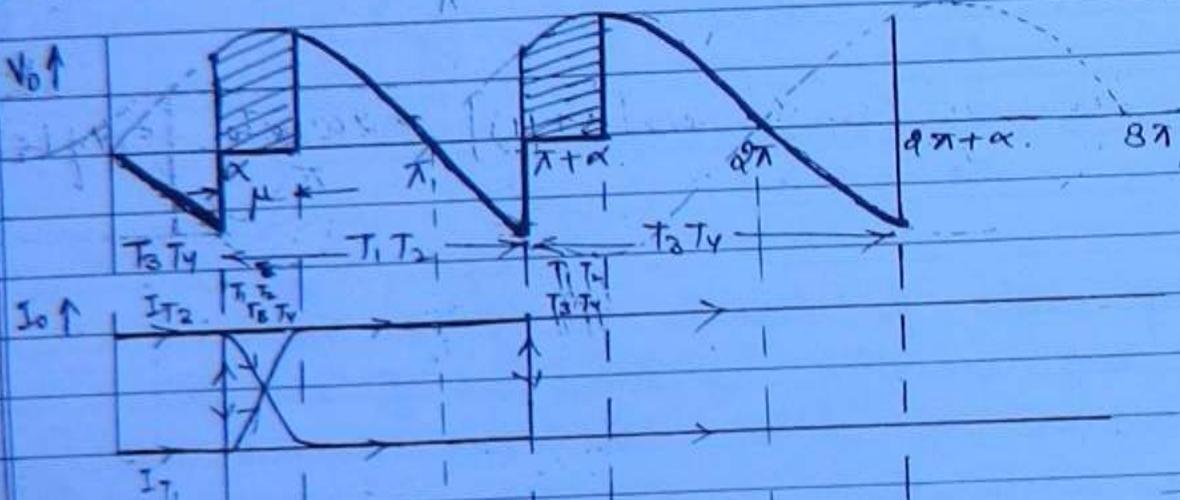

$$T_1, T_2 \rightarrow \text{ON} \quad I_{T_1} = I_{T_2} = I_0$$

$$T_3, T_4 \rightarrow \text{ON} \quad I_{T_3} = I_{T_4} = I_0$$

with L_s

During the overlap period w_{fg} is 0 as all thyristors are conducting simultaneously $\therefore w_{fg}$ is 0.

During μ T_1, T_2 & $T_3 T_4 \rightarrow ON$ $B_o V_o = 0$

(133)

$$V_o = L_s \frac{dI_s}{dt}$$

$$\int_{\alpha}^{\alpha+\mu} V_m \sin \omega t d(\omega t) = \omega L_s \int_{-I_0}^{+I_0} dI_s$$

Wrong in P.C.E.

$$\frac{V_m}{\pi} [\cos \alpha - \cos (\alpha + \mu)] = \omega \omega L_s I_0$$

$$\Delta V_{do} = \frac{V_m}{\pi} [\cos \alpha - \cos (\alpha + \mu)] = \frac{2 \omega L_s I_0}{\pi} = 4 f L_s I_0 \quad (1)$$

$$V_{do} = \frac{V_m \cdot \alpha}{\pi} \Rightarrow \frac{V_{do}}{2} = \frac{V_m}{\pi}$$

$$\Delta V_{do} = V_{do} [\cos \alpha - \cos (\alpha + \mu)] = \frac{2 \omega L_s I_0}{\pi}$$

$$V_o = V_{do} \cos \alpha - 4 f L_s I_0 \quad (2)$$

$$V_o = \frac{V_{do}}{2} [\cos \alpha + \cos (\alpha + \mu)] \quad (3)$$

From (1)

$$\frac{V_m}{\pi} [\cos \alpha - \cos (\alpha + \mu)] = 2 \omega L_s I_0$$

$$I_0 = \frac{V_m}{2 \pi \omega L_s} [\cos \alpha - \cos (\alpha + \mu)]$$

$$I_0 = \cos \alpha - \cos (\alpha + \mu) \quad (4)$$

Inductive Voltage Regulation -

Measure of reduction in vfg due to the source inductance.

(134)

$$\Rightarrow \Delta V_{dc}$$

$$V_{dc}$$

$$= N_{dc} [\cos \alpha - \cos(\alpha + \mu)]$$

2.

$$= \frac{N_{dc}}{2} \alpha - \cos(\alpha + \mu)$$

ΔV_{dc} does not depend on α .

$$\text{At } \alpha = 0 \quad \text{let } \mu = \mu_0$$

$$\text{Inductive V/f Reg} \Rightarrow \frac{\cos 0 - \cos(0 + \mu_0)}{2}$$

$$\Rightarrow \frac{1 - \cos \mu_0}{2}$$

Effect of L_s on the performance of converter -

* Reduces avg output vfg of the converter

* It limits the range of α

$$\alpha_{max} = 180 - (\omega t_g + \mu_0)$$

t_g = device turn off time

~~Due to L_s~~


$$\text{EDF} = \cos\left(\alpha + \frac{\mu}{2}\right)$$

L_s

$\uparrow t_g$ = gives smoothness of waveform towards sine wave,
 \therefore $\uparrow t_g$ waveform approaches towards sine wave
 \therefore with L_s , $\eta \uparrow$ THD \downarrow
However, it \downarrow AC side of converter.

Here the \uparrow in g value is dominating the \downarrow in FDF. i.e. the PF is slightly \uparrow (135)

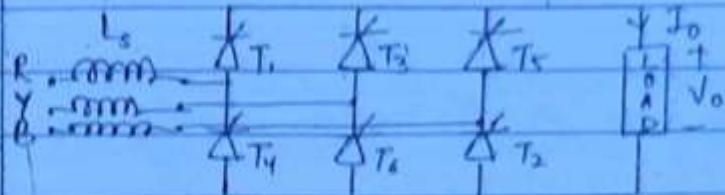
Effect of Source Inductance \rightarrow 6 pulse converter.



Without L_s

With L_s

Reduction in V_o due to L_s

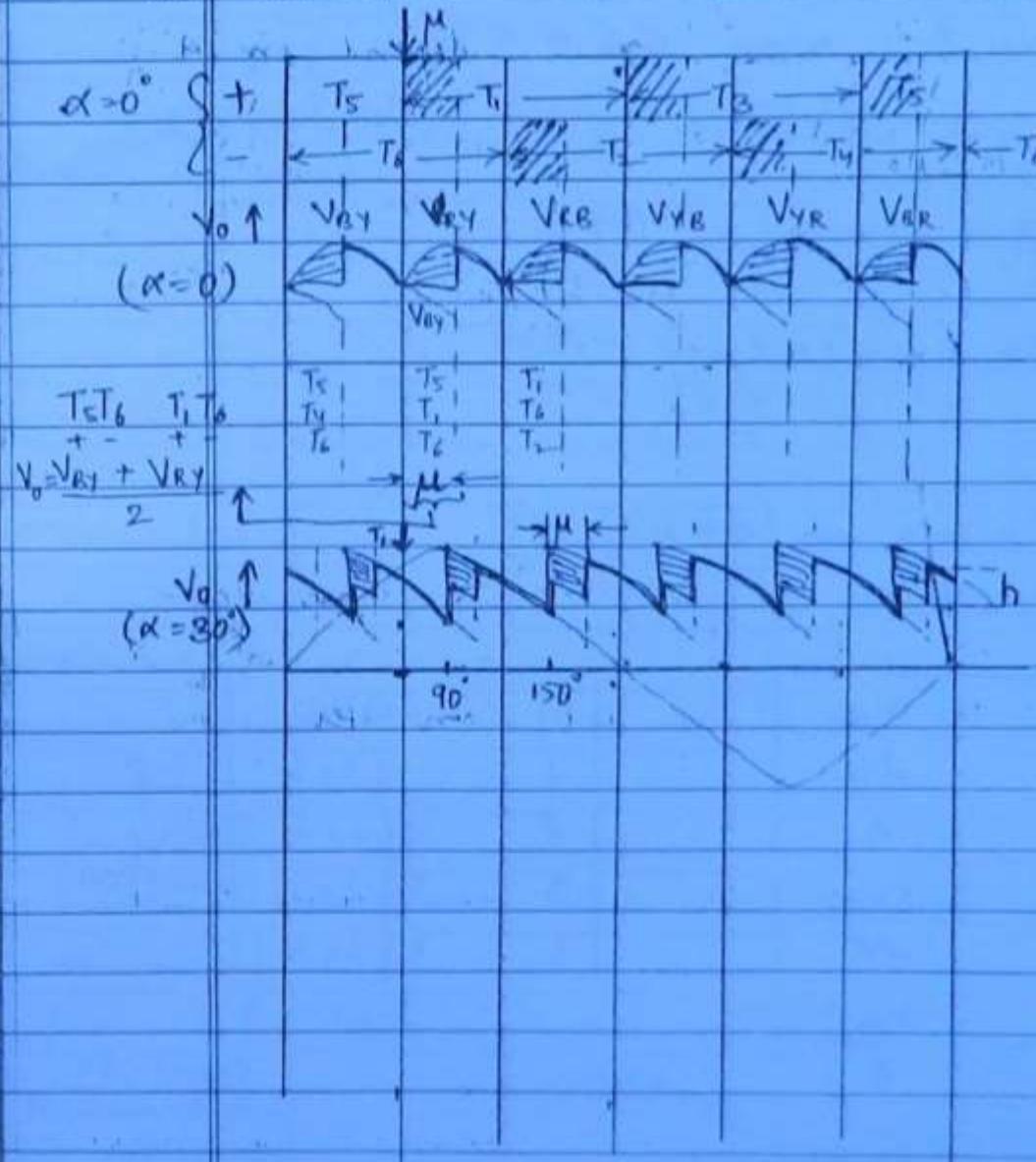

$\alpha \uparrow$ ripple \uparrow $h \uparrow$
 $\therefore \mu \downarrow$ to
 maintain same area
 [max ripple \rightarrow at 90°]
 [min μ]

$$\Delta V_{do} = \frac{V_{do}}{2} (\cos \alpha - \cos(\alpha + \mu)) = 6 f_s L_s I_o \quad \text{--- (1)}$$

(T36)

* We get minimum μ at $\alpha = 90^\circ$ cuz we get maximum ripple.

* We get maximum μ at $\alpha = 0^\circ$ cuz ripple is minimum

\Rightarrow When other parameters are held constant

$\mu \downarrow$ ripple \uparrow when $0^\circ < \alpha < 90^\circ$

* for $\alpha > 90^\circ$, $\alpha \uparrow \mu \uparrow$

$$V_o = V_{do} \cos \alpha - 6 f_s L_s I_o \quad \text{--- (2)}$$

$$V_o = V_{do} \left[\cos \alpha + \cos(\alpha + \mu) \right] \quad \text{--- (3)}$$

$$I_o = V_{ML} \left[\cos \alpha - \cos(\alpha + \mu) \right] \quad \text{--- (4)}$$

m	V_{do}
α	αV_m
1	π
3	$3V_{ML}$ $\alpha\pi$
6	$\frac{3V_{ML}}{\pi}$

m	ΔV_{do}
1	$f_s L_s I_o$
2	$4f_s L_s I_o$
3	$3f_s L_s I_o$
6	$6f_s L_s I_o$


INVERTERS

Fixed DC \rightarrow Variable AC
 $(V_o \propto f_o)$

- Classification of Inverters -
- \rightarrow Voltage Source Inverters (VSI) \rightarrow output waveform is independent of load
 - \rightarrow Current Source Inverters (CSI) \rightarrow app. of VSI

VSI

a) 1φ Half Bridge Inverter -

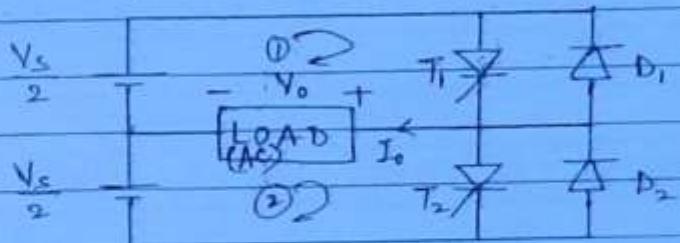

$T_1 \rightarrow ON$

$$V_o = \frac{V_s}{2}$$

$T_2 \rightarrow ON$

$$V_o = -\frac{V_s}{2}$$

$I_g \uparrow$

$I_g \uparrow$

$V_o \uparrow$

(Any Load)

$V_s/2$

$V_s/2$

$I_o \uparrow$

$V_s/2 R$

$V_s/2 R$

\rightarrow forced commutation
is required

(R Load)
Feedback diodes
will not conduct

$-V_s/2 R$

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{4}{n\pi} \left(\frac{V_s}{2} \right) \sin n\omega t$$

$$\Rightarrow V_o = \sum_{n=1,3,5}^{\infty} \alpha V_s \sin n\omega t$$

$$\Rightarrow V_{on} = \frac{2V_s \sin n\omega t}{n\pi}$$


$$(V_{o1})_{rms} = \frac{\sqrt{2} V_s}{n\pi}$$

$$(V_{o3})_{rms} = \frac{\sqrt{2} V_s}{\pi}$$

$$g = \frac{(V_{o1})_{rms}}{V_{on}} = \frac{\frac{\sqrt{2} V_s}{n\pi}}{\frac{V_s}{2}} = \frac{2\sqrt{2}}{\pi}$$

$$THD = 48.34\%$$

b) 1/4 Full Bridge Inverter

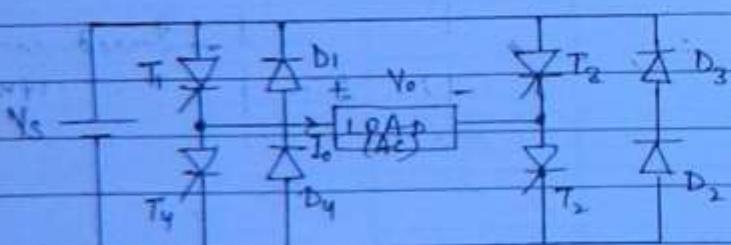

$T_1, T_2 \rightarrow ON$


$$V_o = V_s$$

$T_3, T_4 \rightarrow ON$

$$V_o = -V_s$$

$I_g, I_g \uparrow$

$I_g, I_g \uparrow$

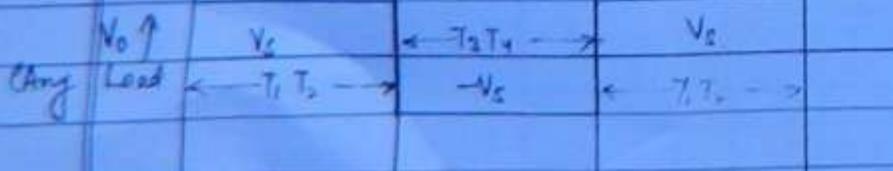

$$V_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin nwt$$

139

$$V_{dn} = \frac{4V_s}{n\pi} \sin nwt$$


$$(V_{dn})_{rms} = \frac{2\sqrt{2}}{n\pi} V_s$$

$$(V_{o1})_{rms} = \frac{2\sqrt{2}}{\pi} V_s$$

$$g = \frac{(V_{o1})_{rms}}{V_{dn}} = \frac{2\sqrt{2}}{\pi} \frac{V_s}{V_s} = \frac{2\sqrt{2}}{\pi}$$

$$THD = 48.34\%$$

1 φ Half Bridge Inverter (Various Loads)

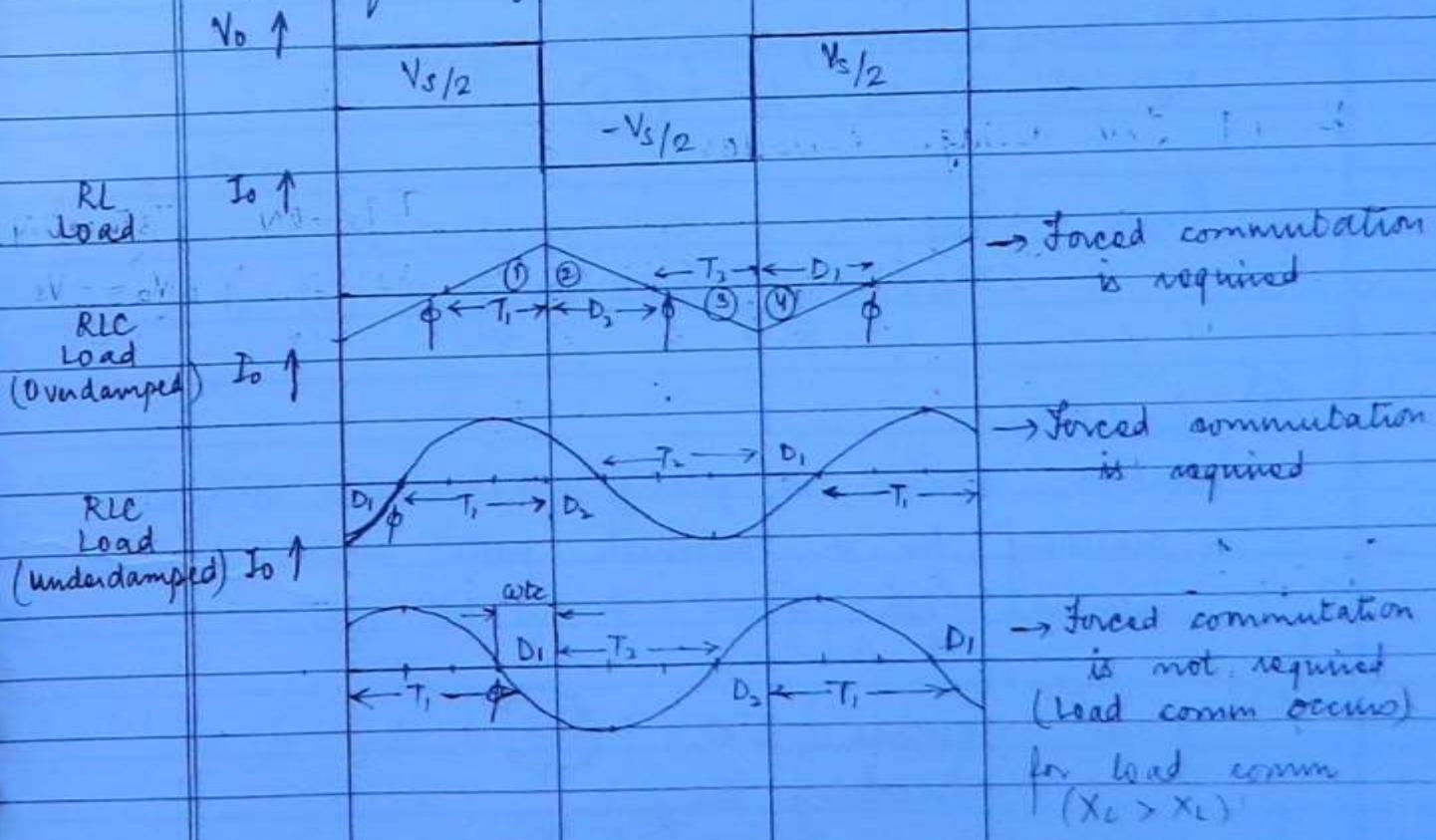

Logics for
I mark
ques



- | | | |
|---|-----------------------------|----------|
| ① | $T \rightarrow ON$ | $P(+)$ |
| ② | $D \rightarrow ON$ | $P(-)$ |
| ③ | $(T, D) \rightarrow ON$ | $V_o(+)$ |
| ④ | $(T_2, D_2) \rightarrow ON$ | $V_o(-)$ |

classmate

Date _____
Page _____

I RL Load -

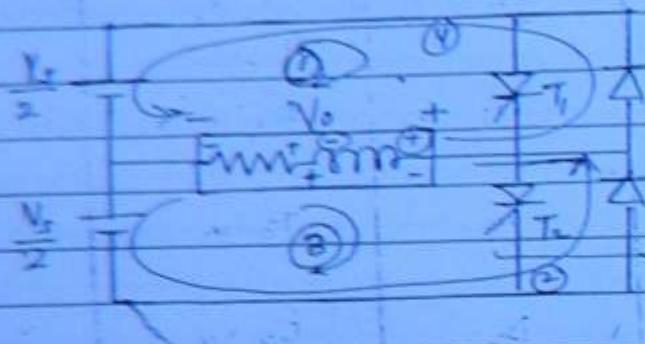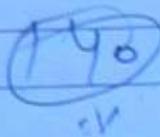After reaching steady state
to logic V_o by $\frac{V_s}{R} = I \tan^2 \omega L$



- ① $T_1 \rightarrow ON$

$$D_1: V_o = V_s, \text{ ie } V_o = I_o + \frac{V_s}{R}$$

(P+)

Source \rightarrow Load

$$\left(\frac{I^2 R}{2} + \frac{1}{2} L I^2 \right)$$

Stores energy.

- ② $D_2 \rightarrow ON$ (P-)

$$\frac{1}{2} L I^2 \rightarrow \text{source} + I^2 R$$

$T_2 \rightarrow ON$ (Releasing Energy)

of antiparallel devices

cannot be ON at the same time.

e.g. D_2 when ON provides RB to T_2 so T_2 is OFF

- ③ $T_2 \rightarrow ON$

(D_2 releases reverse polarity thus T_2 starts conducting)

$$V_o = -V_s, \text{ ie } V_o = I_o - \frac{V_s}{R}$$

(P+)

Source \rightarrow Load

$$\left(\frac{I^2 R}{2} + \frac{1}{2} L I^2 \right) \text{ Stores Energy}$$

- ④ $D_1 \rightarrow ON$

Inductor reduces its polarity to release energy searching for a favourable path which is achieved from D_1 .

$$\frac{1}{2} L I^2 \rightarrow \text{source} + I^2 R$$

(P-)

$\frac{1}{2} L I^2 \rightarrow \text{source} + I^2 R$ (Releasing Energy)

Forced commutation is required for RL load.

* Switching Logic Table

(4)

Device (ON)

V_o	I_o	P	1/2 Bridge	Full Bridge
$T_1 D_1$	$+ T_1 T_2$		T_1	$T_1 T_2$
$T_1 D_1$	$- D_1 D_2$		D_1	$D_1 D_2$
$T_2 D_2$	$- T_1 T_2$		T_2	$T_3 T_4$
$T_2 D_2$	$+ D_1 D_2$		D_2	$D_3 D_4$

for all leading loads it starts with T

for all lagging loads it starts with D

II RLC (Overdamped)

$$X_L > X_C$$

$$I_o \text{ lags } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

III RLC (Underdamped)

$$X_C > X_L$$

$$I_o \text{ lags } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$\text{or } I_o \text{ leads } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

$$\cot \phi$$

$$\phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

\nwarrow if $t_c < t_d$ then load commutation fails
 $(\therefore$ forced commutation is required)

$$V_{on} = \frac{2N_s}{n\pi} \sin(nwt) \quad (\text{Any Load})$$

142

Consider an RLC load

$$I_{on} = \frac{V_{on}}{Z_n}$$

$$Z_n = R + j(X_{ln} - X_{cn})$$

$$X_{ln} = nWL \quad X_{cn} = j$$

\downarrow
 n^{th} harmonic
inductive impedance \downarrow
 n^{th} harmonic
capacitive impedance

$$Z_n = |Z_n| / \phi_n$$

$$|Z_n| = \sqrt{(R)^2 + (X_{ln} - X_{cn})^2}$$

$$\phi_n = \tan^{-1} \left(\frac{X_{ln} - X_{cn}}{R} \right)$$

\downarrow
 n^{th} harmonic
impedance angle

(or) displacement angle.

$$I_{on} = \frac{V_{on}}{Z_n} = \frac{V_{on}}{|Z_n| / \phi_n} = V_{on} / |Z_n| \angle -\phi_n$$

\rightarrow 4 for full bridge

$$I_{on} = \frac{2N_s}{n\pi} \sin(nwt - \phi_n) \quad \rightarrow \text{for RLC load.}$$




$\underline{\omega}$ for pure inductive load

$$|Z_n| = nWL$$


$$\phi_n = 90^\circ$$

$$I_{on} = \frac{2V_s}{n\pi} \sin(nwt - 90^\circ) \Rightarrow I_{on} \propto 1$$

If n^{th} harmonic is
inv. prop. to n^2 shape

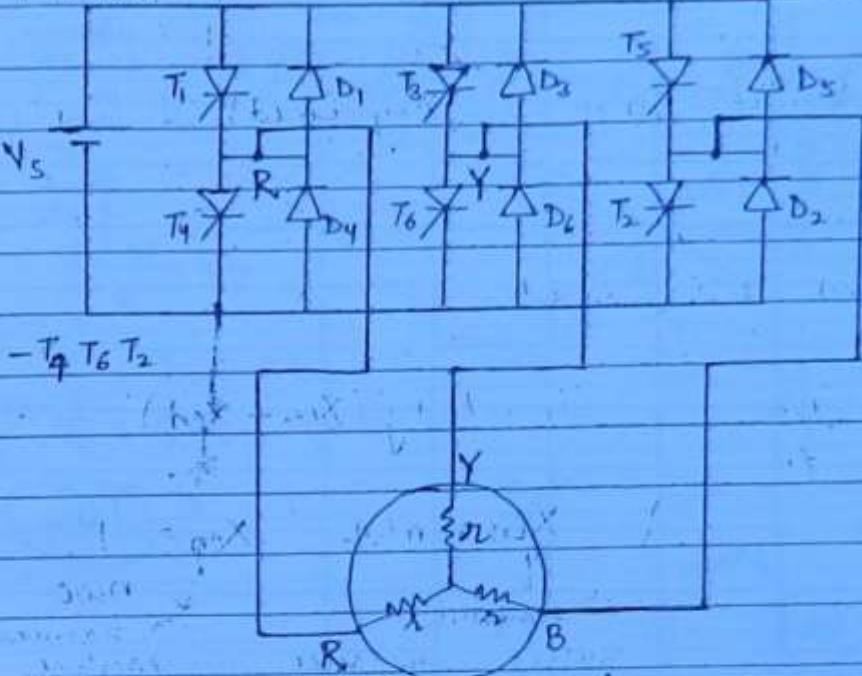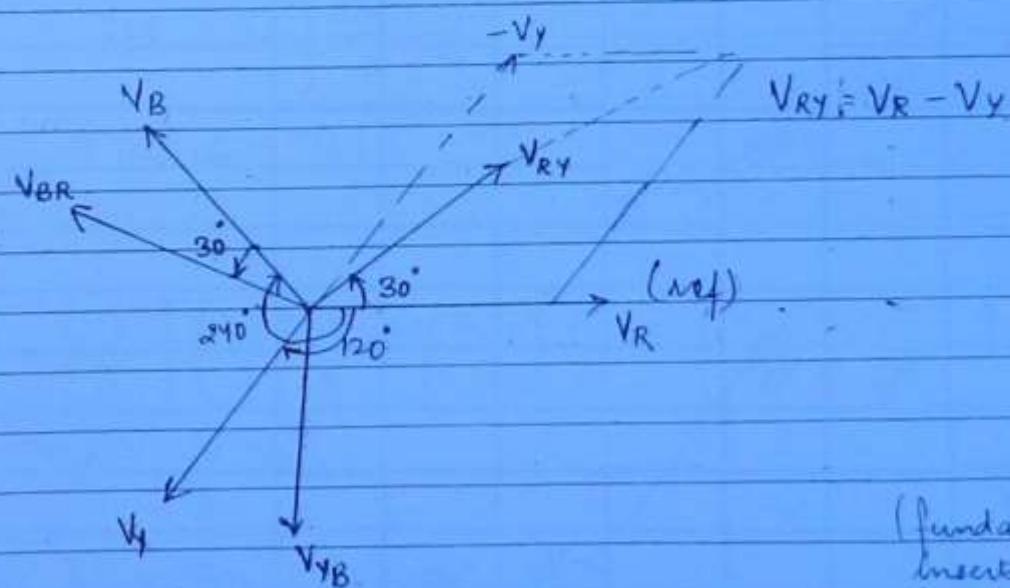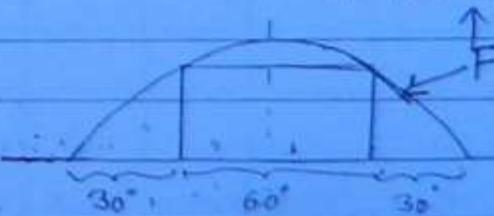3φ VSIa) 180°
MODE3φ Y connected R Load(fundamental
insert the pulse
in the centre)

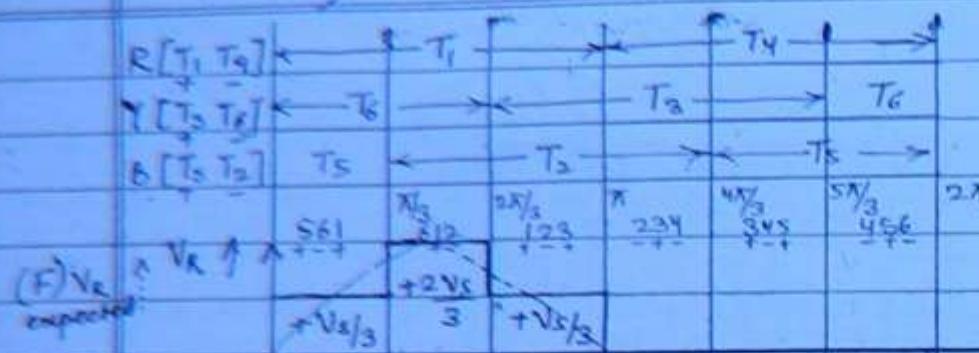Switching pattern
is same in direct & inverse



S61

+ - +

thin -ve share
current of 2 +ve
phases


do its double
ie $Y \neq V$ if I
are double of
 $R \neq B$
since its -ve
its polarity is -ve

so $5 \rightarrow 6 \rightarrow +\frac{V_s}{3}$

$6 \rightarrow Y \rightarrow -\frac{2V_s}{3}$

$1 \rightarrow R \rightarrow +\frac{V_s}{3}$

(144)

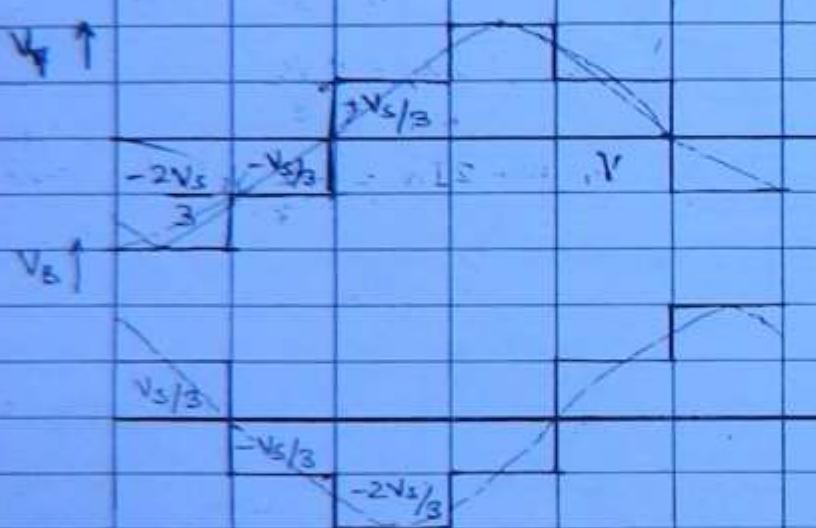


$$V_R - V_Y = V_{RY} \uparrow$$

N_s N_s


N_C

$-V_s$ $-V_s$

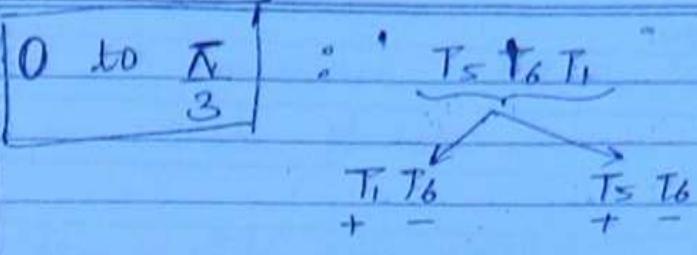The waveforms are same for any load. Δ connected or
connected to DC motor, induction motor, etc.
an in VS1 the waveform is independent of load.



(145)

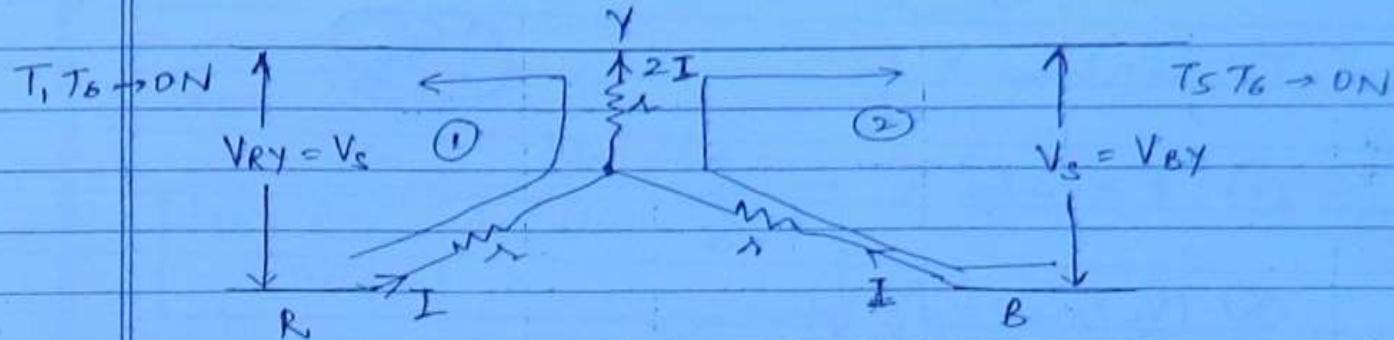

$$V_S = I_n + 2I_n$$

$$V_S = 3I_n$$

$$I_n = \frac{V_S}{3}$$

$$V_R = +I_n = \pm \frac{V_S}{3}$$

$$V_Y = -2I_n = -\frac{2}{3}V_S$$

$$V_B = +I_n = +\frac{V_S}{3}$$

$$V_{RY} = V_S \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$(V_L)_{\text{rms}} = V_S \sqrt{\frac{2}{3}}$$

$$V_R = \left\{ \frac{1}{\pi} \left[\left(\frac{V_S}{3} \right)^2 \frac{\pi}{3} + \left(\frac{2V_S}{3} \right)^2 \frac{\pi}{3} + \left(\frac{V_S}{3} \right)^2 \frac{\pi}{3} \right] \right\}$$

$$V_{ph} = \frac{\sqrt{2}}{3} V_S$$

$$I_L = I_{ph} = \frac{V_{ph}}{Z} = \frac{\sqrt{2}}{3} \frac{V_S}{Z}$$

$$(I_T)_{\text{rms}} = \frac{I_{ph}}{\sqrt{2}}$$

$$V_L = \sqrt{3} V_{ph}$$

$$① V_{ph} = \frac{\sqrt{2}}{3} V_s$$

$$② I_{ph} = \frac{V_{ph}}{r}$$

$$③ (I_T)_{rms} = \frac{I_{ph}}{\sqrt{2}}$$

(14.6)

$$④ P = 3 I_{ph}^2 r = \frac{3 V_{ph}^2}{r}$$

$$⑤ (V_L)_{rms} = \sqrt{3} V_{ph}$$

fourier series form & phase vlg waveform.

$$V_R = \sum_{n=6k+1}^{\infty} \frac{a_n V_s}{n\pi} \sin n\omega t$$

NOTE : Even & triple harmonics are absent

$$V_{Rn} = \frac{a_n V_s}{n\pi} \sin n\omega t$$

$$(V_{Rn})_{rms} = \frac{\sqrt{2} V_s}{n\pi} \quad (V_{R1})_{rms} = \frac{\sqrt{2} V_s}{\pi}$$

$$g = \frac{V_{R1}}{V_R} = \frac{\sqrt{2} V_s}{\pi} / \frac{\sqrt{2} V_s}{3} = \frac{3}{\pi}$$

$$g = \frac{3}{\pi}$$

$$THD = 31\%$$

Let us consider, RLC load
in each phase.

$$V_{Rn} = \frac{2}{n\pi} V_s \sin nwt$$

(147)

$$I_{Rn} = \frac{V_{Rn}}{Z_n} = \frac{V_{Rn}}{|Z_n|/\phi_n}$$

$$I_{Rn} = \frac{2}{n\pi} \frac{V_s \sin(nwt - \phi_n)}{|Z_n|}$$

e.g. I.M $|Z_{\text{eq}}| \text{ per phase} = \sqrt{R_i^2 + (n\omega L_i)^2}$

$$\phi_n = \tan^{-1} \frac{X_{L_n}}{R_i}$$

for $n=1$ (F)

Diode conducts for $\phi = \tan^{-1} \frac{X_L}{R}$ for RL load

if $\phi = \tan^{-1} \frac{X_C - X_L}{R}$ for RLC load

————— X —————

Line vfg.

$$V_{RY} = \sum_{\substack{n=1,3,5 \\ n=6k+1}}^{\infty} \frac{4}{n\pi} V_s \sin \frac{n\pi}{3} \sin n \left(wt + \frac{\pi}{6} \right)$$


•

$$g = \frac{3}{\pi} \quad \text{THD} = 31\%$$

Disadvantage of 180° mode VSI

There's a possibility of S.C across the supply when incoming thyristor start conducting before the outgoing thyristor belonging to the same phase stop conducting

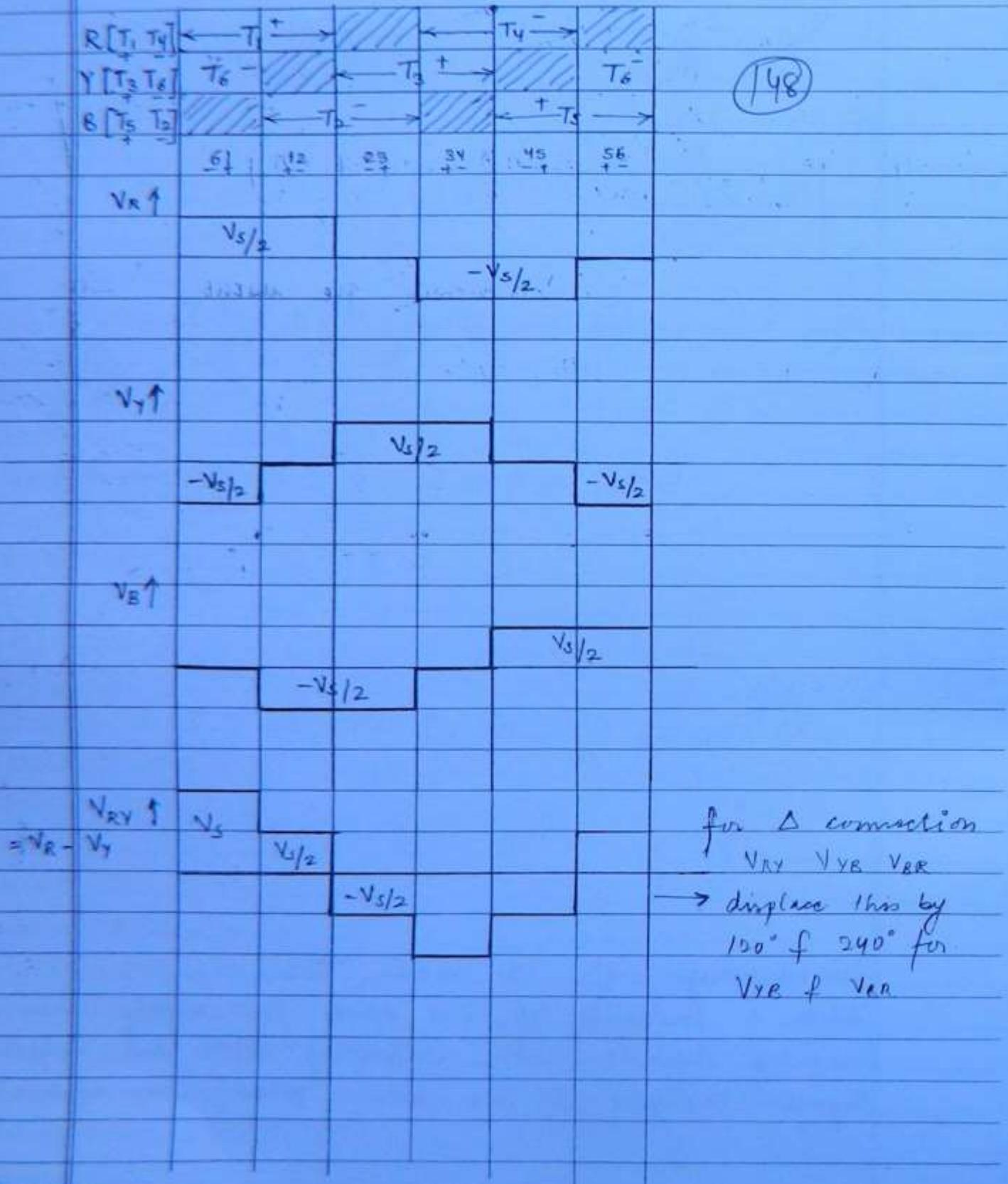b) 120° mode \rightarrow In 120° mode VSI we are allotting a conduction angle of 120° for each thyristor if the last 60° is allotted for commutation



$$(V_R)_{\text{rms}} = \frac{V_s}{2} \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$= \frac{V_s}{2} \sqrt{\frac{2}{3}}$$

(149)

$$(V_R)_{\text{rms}} = \boxed{\frac{V_s}{\sqrt{6}} = V_{\text{ph}}}$$

phase vfg. $V_R = \sum_{\substack{n=6K+1 \\ n=1, 3, 5, \dots}}^{\infty} \frac{2V_s}{n\pi} \sin n \frac{\pi}{3} \sin n \left(\omega t + \frac{\pi}{6} \right)$

NOTE : Even & triple harmonics are absent

$$g = \frac{3}{\pi} \quad \text{THD} = 31\%$$

line vfg. $V_R = \sum_{n=6K+1}^{\infty} \frac{3V_s}{n\pi} \sin n \left(\omega t + \frac{\pi}{3} \right)$



NOTE : Even & triple harmonics are absent

$$g = \frac{3}{\pi} \quad \text{THD} = 31\%$$

for 120° & 180° mode

phase or line vfg
g & THD are same.

CSI

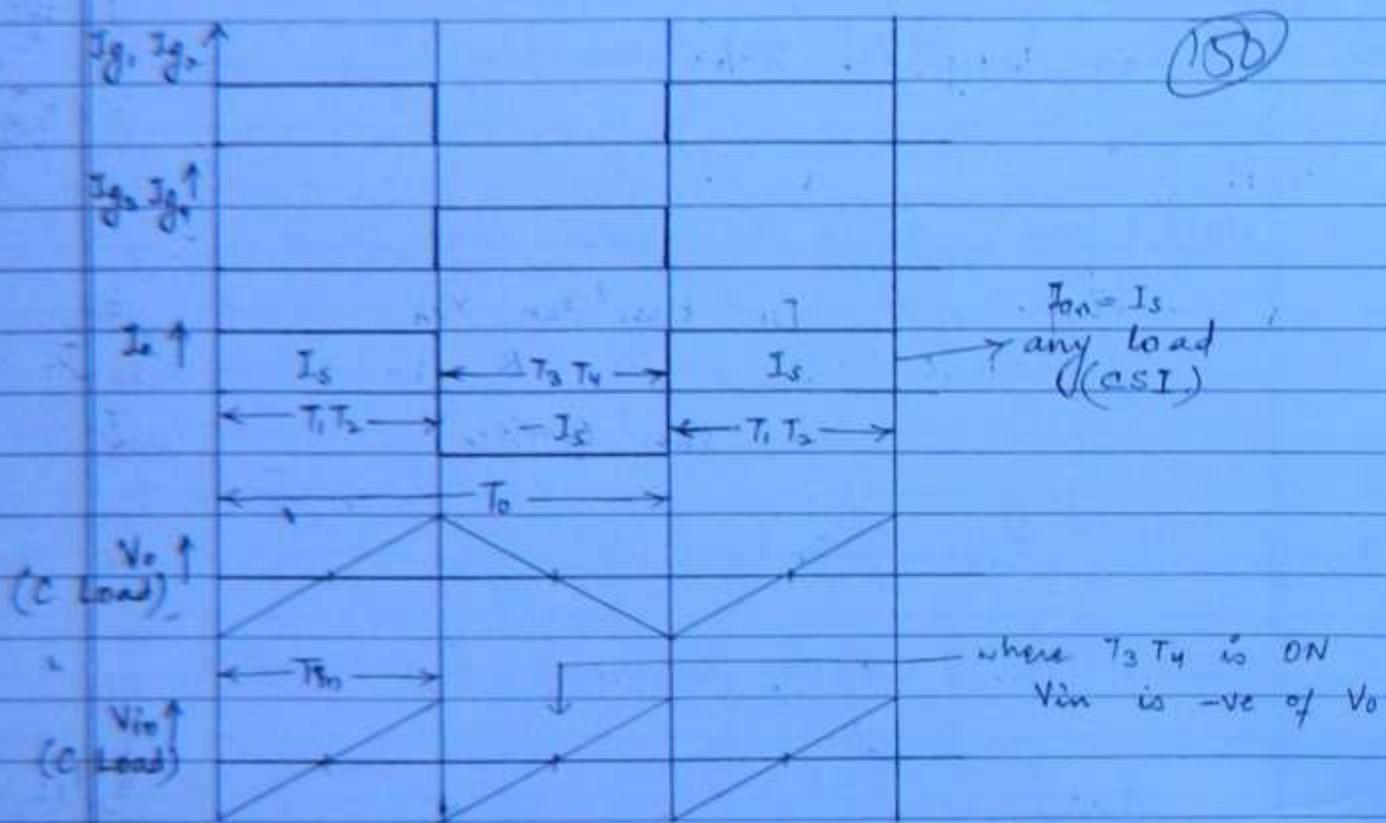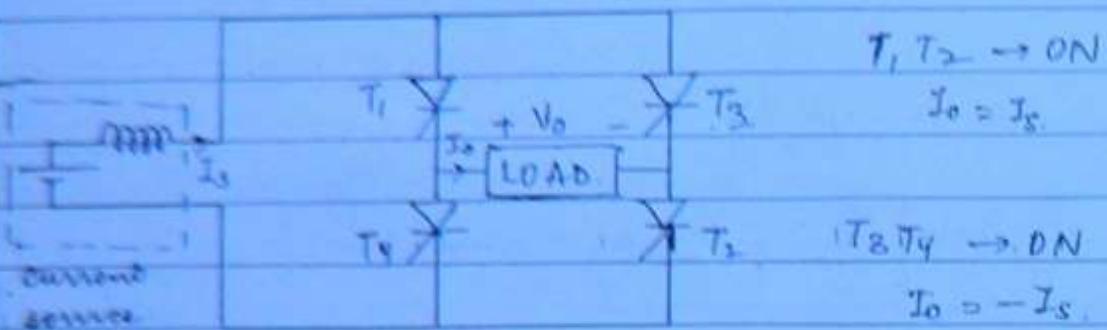

$$I_a = \sum_{n=1,3,5,..}^{\infty} \frac{4 I_s \sin n\omega t}{n\pi}$$

$$g = \frac{2\sqrt{2}}{\pi} \quad THD = 48.34\%$$

$$I_{an} = 4 I_s \sin n\omega t \quad [\text{for any load}]$$

Let us consider an RLC load -

$$V_{on} = I_{on} \cdot Z_n$$

$$= I_{on} |Z_n| / \phi_n$$

(15)

$$V_{on} = \frac{4I_s}{n\pi} |Z_n| \sin(nwt + \phi_n)$$

$$Z_n = R + j(X_{L_n} - X_{C_n})$$

For 'C' load

$$|Z_n| = \frac{1}{n\omega C}$$

$$\phi_n = \tan^{-1} \frac{X_{L_n} - X_{C_n}}{R}$$

$$= \tan^{-1} \frac{0 - X_{C_n}}{0}$$

$$\phi_n = -90^\circ$$

$$V_{on} = \frac{4I_s}{n\pi} \left(\frac{1}{n\omega C} \right) \sin(nwt - 90^\circ)$$

$$V_{on} \propto \frac{1}{n^2}$$

$$T_0 = 2T_{in}$$

$$\therefore \boxed{f_{in} = 2f_0}$$

↓ ↓
DC AC


Advantages of CSI -

1. Feedback diodes are not required in CSI.
2. Commutation is simple.
3. For C loads there's a possibility of load commutation.
4. Inherently there's a short circuit protection for the source when the incoming thyristors are switched on before the outgoing thyristor becomes off due to the presence of high inductance.

(182)

Disadvantages of CSI -

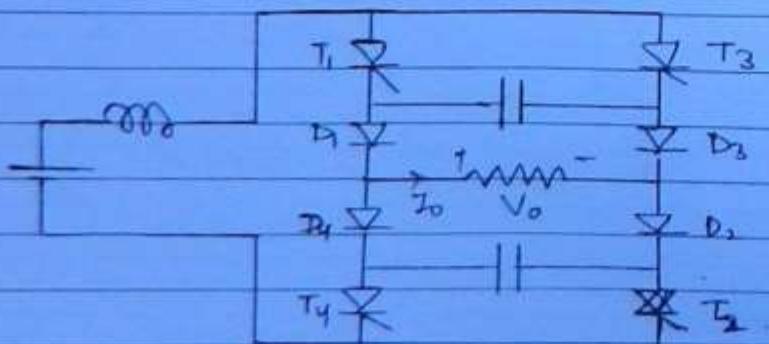1. The commutating element (along with the load) applies high reverse voltage across the power device used in CSI. i.e. the devices having low reverse voltage blocking capability such as GTO, IGBT if other transistors are not generally preferred in CSI. Here we prefer SCR because it has high reverse voltage blocking capability.
2. If commutating capacitor is directly connected across the load, then it will be continuously discharging through the load. To avoid it we must connect the diode as shown in figure.




CWB chapter 2.

(TS3)

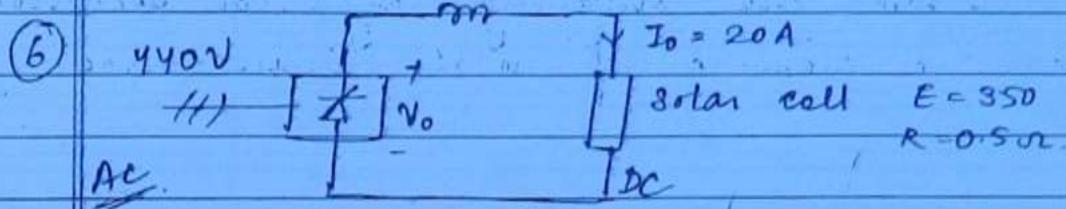(5) $\alpha = 60^\circ$ FDF = $\cos \alpha$ = $\cos 60^\circ = 0.5$
 (IDF)

$$PF = g(FDF)$$

$$= \frac{3}{\pi} (\cos \alpha) = \frac{3}{\pi} \cos 60^\circ = 0.476 \text{ (c)}$$



$$P_{AC} \leftarrow \frac{INV}{(\alpha > 90^\circ)} P_{DC}$$

$$V_o = -E + I_o R$$

$$-350 + 10 = -340$$

$$\frac{3}{\pi} V_{ML} \cos \alpha = -E + I_o R$$

$$3 \cdot \frac{440\sqrt{2}}{\pi} \cos \alpha = -340$$

$$\alpha = 125^\circ$$

$$\text{for } \alpha \geq 60^\circ \quad \omega_{tc} = \pi - \alpha = 180 - 125^\circ$$

$$= 55^\circ \text{ (d)}$$

054

(155)

5


$$\alpha = 60^\circ, \quad FDF = \cos \alpha$$

$$= \cos 60^\circ = 0.5$$

$$PF = g(EDE) = \frac{3 \times 0.5}{\lambda}$$

$$= 0.478$$

6

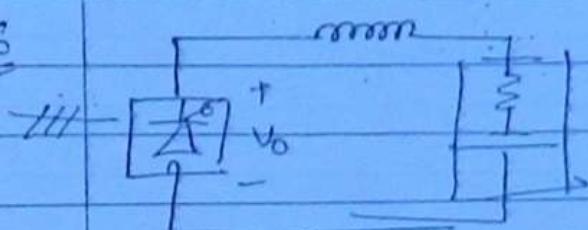

$P_{AC} < P_D$
inversion
 $\alpha > 90^\circ$

$$V_0 = -E + I_R R$$

$$\frac{\cos \alpha \cdot 3V_{ML}}{\pi \cos \alpha} = -350 + (20 \times 0.5)$$

$$\frac{3 \times 40\sqrt{2} \cos \alpha}{\cos \pi} = -350 + 10$$

$$\cos \alpha \Rightarrow \alpha = 125^\circ$$

$$\text{I } \alpha < 60^\circ, \quad \omega t_c = 4\pi/3 - \alpha$$

$$\text{II } \alpha > 60^\circ, \quad \omega t_c = \pi - \alpha/2$$

$$= 180^\circ - 125^\circ$$


$$= 55^\circ$$

VOLTAGE Control of Inverter


15d

I - External control

a)

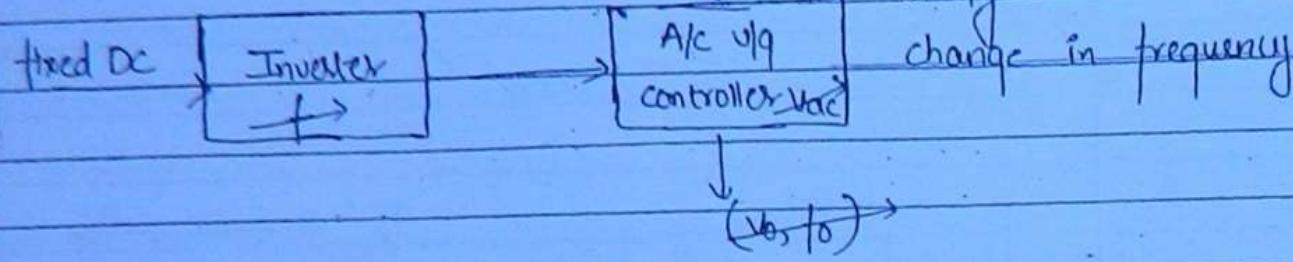

b)

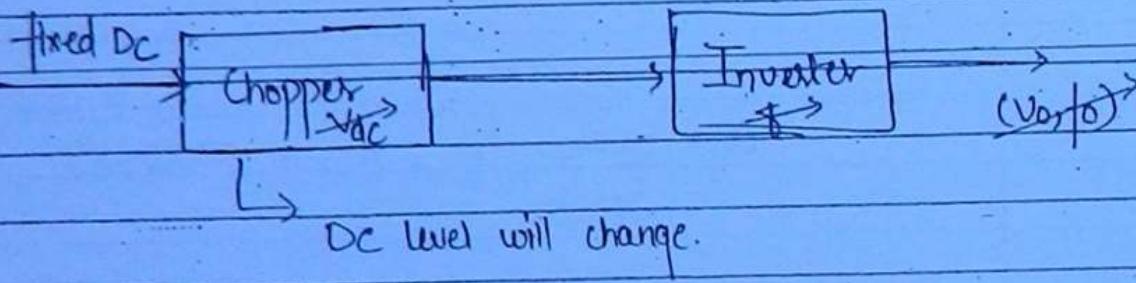

(157)


Advantages of PWM technique:-


1. We can get variable v/f within the inverter without increasing no. of stages.
2. We can eliminate some of the lower order harmonics (higher order harmonics can be easily filtered).

Types of PWM techniques:-

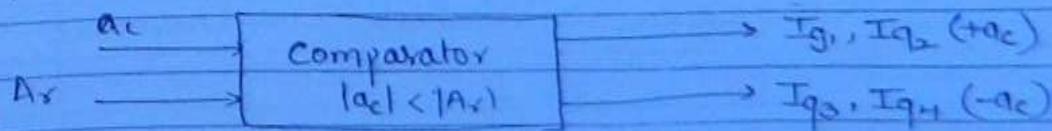1. Single PWM technique :-

Let us realise this modulation technique using full bridge inverter.



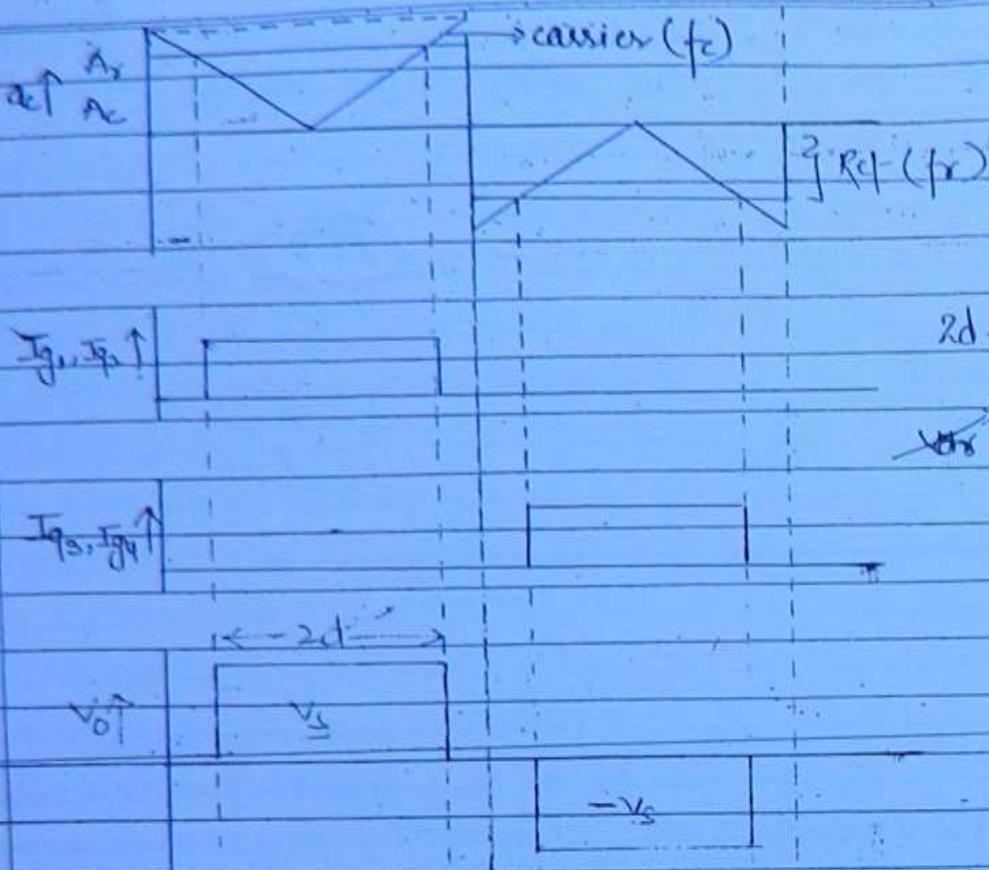

$2d \rightarrow$ Total pulse width

$$V_{ot} = V_s \left(\frac{2d}{\lambda} \right)^{1/2}$$

(158)

Fourier series for o/p v/q waveform:-

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t \cdot \sin \frac{n\pi}{2} \sin nd$$

$$V_{on} = \frac{4V_s}{n\pi} \cdot \sin \frac{n\pi}{2} \cdot \sin nd \cdot \sin n\omega t$$

$$V_{on} = 0 \text{ if } nd = \pi, 2\pi, 3\pi, \dots$$

$$d = \frac{\pi}{n}, \frac{2\pi}{nd}, \frac{3\pi}{n}, \dots$$

$$2d < 2\pi, \frac{4\pi}{n}, \frac{6\pi}{n} \rightarrow \text{valid only if } 2d < \pi$$

Condition to eliminate nth harmonic

To eliminate 3rd harmonic

$$2d = \frac{2\pi}{3}, \frac{4\pi}{3}, \frac{6\pi}{3}, \dots$$

Since it is less than π .

$$2d = \frac{2\pi}{3} = 120^\circ$$

(159)

To eliminate 5th harmonic

$$2d = \frac{2\pi}{5}, \frac{4\pi}{5}, \frac{6\pi}{5}, \dots$$

both less than π

$$2d = 72^\circ, 144^\circ$$

$$V_{on} = \frac{4Vs}{n\pi} \left| \sin\left(\frac{n\pi}{2}\right) \right| \sin n\theta - \sin(n+1)\theta$$

for $n=1, 3, 5 \dots$ it is ± 1 , for
rms value calculation it is always \pm

$$(V_{on})_{rms} = \frac{4Vs}{n\pi} \frac{\sin n\theta}{\sqrt{2}} = \frac{2\sqrt{2}Vs}{n\pi} \sin n\theta$$

$$(V_{o1})_{rms} = \frac{2\sqrt{2}Vs}{\pi} \sin \theta$$

$$g = \frac{(V_{o1})_{rms}}{V_{o1}} = \frac{2\sqrt{2}Vs}{\pi} \frac{\sin \theta}{Vs \left(\frac{2d}{\pi} \right)^{1/2}}$$

$$g = \frac{2\sqrt{2} \cdot Vs \sin \theta}{\sqrt{(2d) \cdot \pi}}$$

$$THD = \left(\frac{1}{g^2} - 1 \right)^{1/2}$$

Page 89

$$2d = \alpha = 120^\circ$$

$$V_s = 1V$$

$$(V_{01})_{rms} = \frac{2\sqrt{2} V_s}{\pi} \sin d$$

$$= \frac{2\sqrt{2}}{\pi} \sin 60^\circ$$

$$= 0.78$$

(166)

2.

$$2d = 72^\circ \text{ or } 144^\circ$$

3

$$2d = 144^\circ$$

$$(V_{03})_{rms} = \frac{2\sqrt{2} V_s}{3\pi} \sin 3d$$

$$(V_{03max}) = \frac{2\sqrt{2} V_s}{\pi}$$

$$\frac{(V_{03})_{rms}}{(V_{03})_{max}} = \frac{\sin 3d}{3}$$

$$= 19.6\%$$

5

$$2d = 150^\circ$$

$$(V_{01})_r = \frac{2\sqrt{2} V_s}{\pi} \sin d$$

$$g = \frac{2\sqrt{2} \cdot \sin d}{\sqrt{(2d) \cdot \pi}}$$


$$= 0.95$$

$$THD = 0.32$$

$$= 31.63\%$$

Multiple pulse PWM technique :-

(T6)

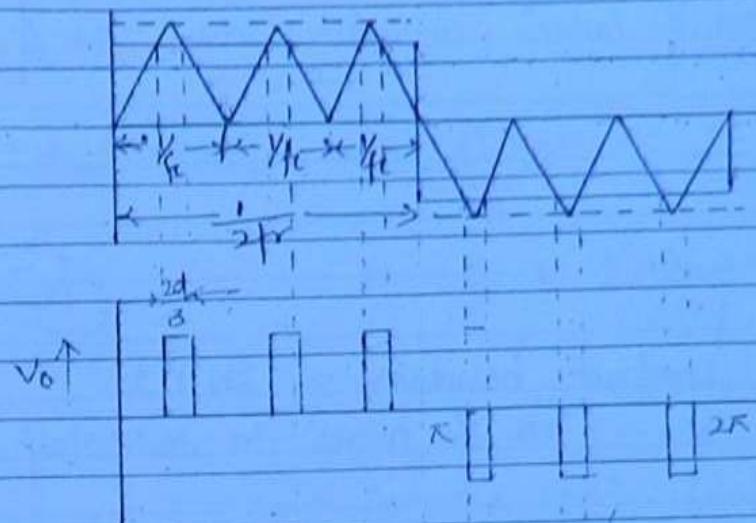

$$\frac{3}{f_c} = \frac{1}{2f_r}$$

$$3 = \frac{f_c}{2f_r}$$

2d → Total PWM

each $\frac{1}{2}$ cycles

$$V_{or} = V_s \left(\frac{2d}{\pi} \right)^{1/2}$$

$$n = \frac{f_c}{2f_r}$$

$$\text{Pulse width} = \frac{2d}{N} = \left(\frac{1-V_r}{V_c} \right) \frac{\pi}{N}$$

(Pulse length)

→ Height of pulse is decided by supply, Only by changing supply, height of the pulse can be varied.

Sinusoidal PWM technique

In sinusoidal PWM technique, the reference signal is taken as sine waveform.

There we've two cases :-

I Case:- Peak value of carrier coincident with zero of Ref. signal.

II Case:- Zero of carrier coincident with zero of reference.

$$\text{Case-1 :- } N = \frac{f_c}{2f_r}, \quad \text{Case-2 :- } N = \frac{f_c}{2f_r} - 1$$

(162)

NOTE:-

Dominant harmonics = $2N \pm 1$.


$N \rightarrow$ No. of pulses in each half cycle

for $N=3$, Dominant harmonic = $6 \pm 1 = 5, 7$ -th.

for $N=9$, " " " = $18 \pm 1 = 17, 19$ -th.

- If Domination is shown by lower order, it is difficult to filter them, we require big size filter to remove lower order harmonics.
- If Domination is shown by higher order, we can easily filter them.

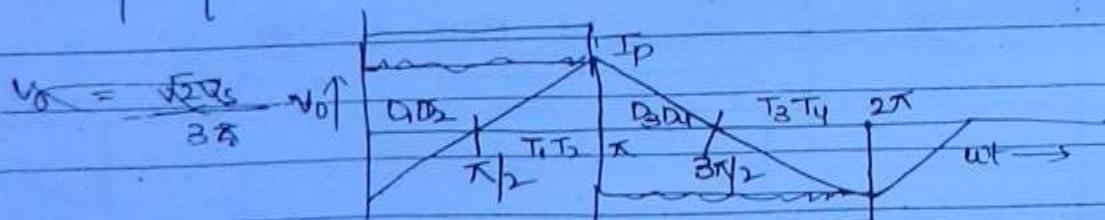In commensurable PWM tech., we ↑ the No. of pulses in each half cycle & ↑ the order of dominant harmonics so that they can be easily filtered.



$$\frac{\pi}{2} \rightarrow \pi \rightarrow V_0 = V_s = \frac{L dI}{dt} = V_s$$

$$\omega di = \frac{V_s}{L} dt \quad \Rightarrow \quad \omega di = \frac{V_s}{L} d(\omega t)$$

$$\int_0^{\frac{\pi}{2}} di = \frac{V_s}{\omega L} \int_{\pi/2}^0 d(\omega t)$$

$$I_p = \frac{200}{100\pi \times 60} \times \frac{\pi}{2} = 10A$$

(163)

13 Since, Inductor $\rightarrow \phi = 90^\circ$

$$\omega t_c = \phi$$

$$t_c = \frac{\phi}{\omega} = \frac{90^\circ / 180^\circ \times \pi}{2\pi f} = 5ms.$$

12 3Φ VSI

→ pure inductive load, $|Z_n| = n\omega L$

$$V_{0n} = \alpha V_{01} \quad (\alpha_n < 1)$$

$$I_{0n} = \frac{\alpha V_{01}}{|Z_n|} = \frac{\alpha_n}{n} \frac{V_{01}}{\omega L}$$

$$0.5 \times \pi$$

$$2\pi f \times 50$$

$$= \frac{\alpha_n}{n} I_{01}$$

$$1. R = 3\Omega, X_L = 12\Omega, X_C = ?$$

$$f = \frac{10^3}{0.02} = \frac{10^3 \times 10}{2} = 5000 \text{ Hz}$$

$$t_q = 12 \times 10^{-6} \text{ s}, SF = 2$$

$$t_c = 12 \times 2 \times 10^{-6}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$12 \times 10^{-6} \times \frac{2 \times \pi \times 5000 \times 180^\circ}{\pi} \tan^{-1} \left(\frac{12 - X_C}{3} \right)$$

$$X_C = X_C = 19.182 \quad \frac{1}{2\pi f C} = X_C$$


$$C = 2.15 \mu F$$

CHOPPER


(164)

fixed DC \longrightarrow variable DC

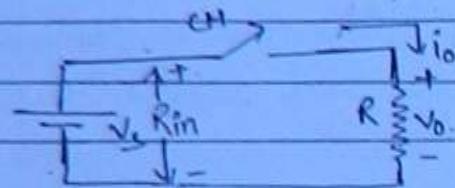1. Step-down chopper : $(V_o < V_s)$ \rightarrow without filter



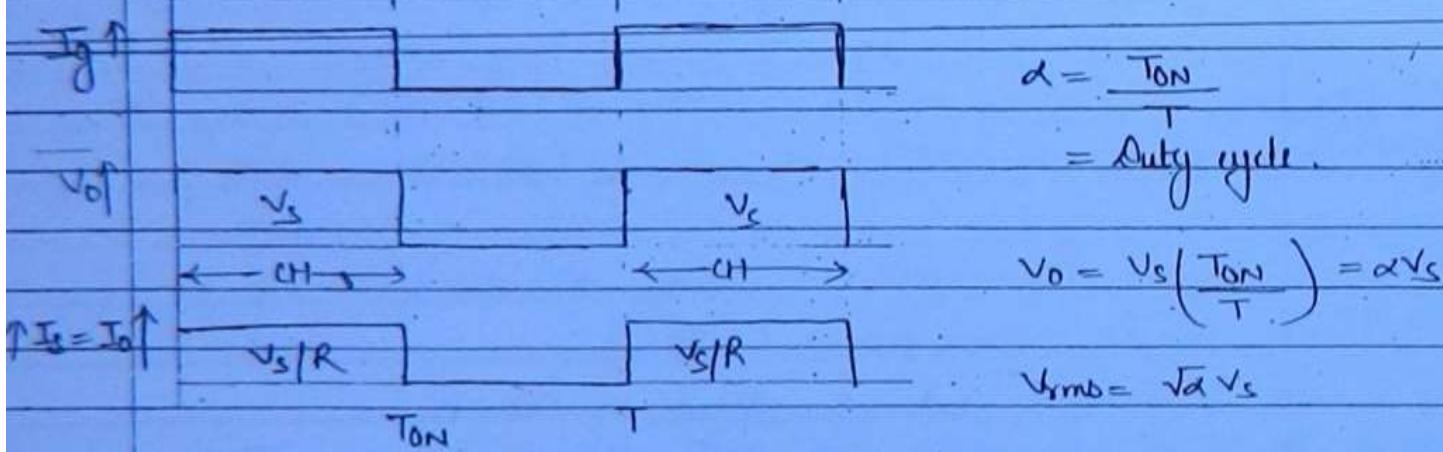Switch can be replaced by GTO or any power device for low power appl' but for high-power, it should be SCR with forced commutation.



$$I_o = \frac{V_o}{R} = \frac{\alpha V_s}{R} = I_{so}$$

$$R_{in} = \frac{V_s}{I_s} = \frac{V_s}{\alpha \frac{V_s}{R}} = \frac{R}{\alpha}$$

$$\boxed{R_{in} = \frac{R}{\alpha}}$$

$$V_o = \alpha V_s + \sum_{n=1}^{\infty} \frac{2V_s}{n\pi} \sin(n\omega t + \phi_n) \sin n\pi\alpha$$

$$\text{where } \phi_n = \tan^{-1} \left[\frac{\cos n\pi}{\sin n\pi} \right]$$

(65)

$$v_{bn} = \frac{\alpha V_s + 2V_c \sin n\pi d \cdot \sin(n\omega t + \phi_n)}{n\pi}$$

$v_{bn} = 0$ if $n\alpha = 1$


$$\alpha = \frac{1}{n} \rightarrow \text{cond}^n \text{ to eliminate } n^{\text{th}} \text{ harmonic}$$

$$FF = \frac{V_{or}}{V_o} = \frac{\sqrt{\alpha} V_s}{\alpha V_s} = \frac{1}{\sqrt{\alpha}}$$

$$\downarrow VRF = \sqrt{FF^2 - 1} = \sqrt{\frac{1}{\alpha} - 1}$$

For High values of Duty cycle, harmonics are lesser.

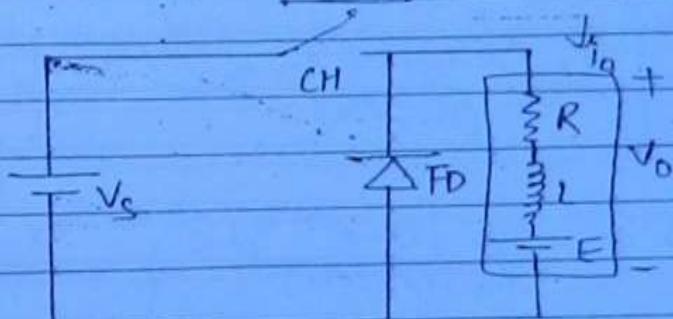
③ RLE load \rightarrow Cont. Conduction (waveform analysis for $RL \neq RLE$)




$$V_o = \alpha V_s$$

$$V_{or} = \sqrt{\alpha} V_s$$

$$I_o = \alpha V_s - \frac{E_b}{R}$$

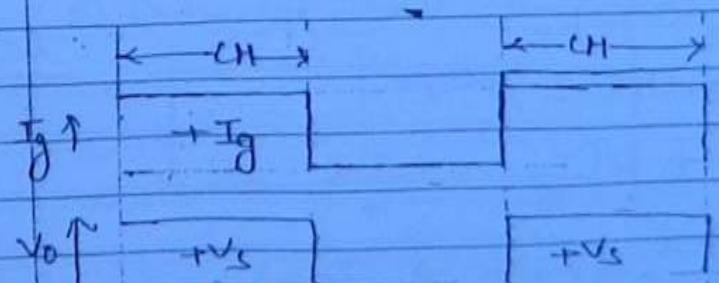

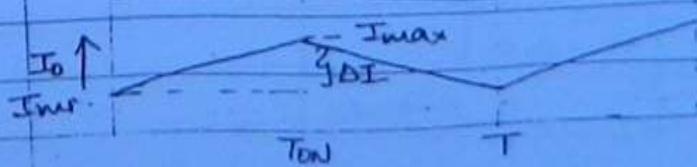Ap. v/q will not depend on value of L but ripple will depend.



$$I_{max} = \frac{V_s}{R_a} \left(\frac{1 - e^{-T_{on}/T_a}}{e^{T/T_a} - 1} \right) - \frac{E_b}{R_a} \quad (1)$$

where $T_a = \frac{L_a}{R_a} \rightarrow$ in/c time constP

(165)

$$-I_{min} = \frac{V_s}{R_a} \left[\frac{\frac{T_{on}/T_a}{e^{T/T_a} - 1}}{\frac{e^{T/T_a} - 1}{e^{T/T_a} - 1}} \right] - \frac{E_b}{R_a} \quad (2)$$

$$\begin{aligned} \text{Ripple current} &= \Delta I_0 = I_{max} - I_{min} \\ &= \frac{V_s}{R_a} \left\{ \left(\frac{e^{T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right) \left(\frac{e^{T/T_a}}{e^{T_{on}/T_a}} \right) - \left(\frac{e^{T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right) \right\} \\ &= \frac{V_s}{R_a} \left\{ \left(\frac{e^{T/T_a} - 1}{e^{T_{on}/T_a} - 1} \right) \left(\frac{e^{-T_{on}/T_a} - 1}{e^{-T/T_a} - 1} \right) \right\} \\ &= \frac{V_s}{R_a} \left[\frac{(1 - e^{-T_{on}/T_a})(1 - e^{-T_{off}/T_a})}{(1 - e^{-T/T_a})} \right] \end{aligned}$$

as α varies, ΔI_0 varies.

$$T_{on} = \alpha T, \quad T_{off} = (1-\alpha)T$$

$$\Delta I_0 = \frac{V_s}{R_a} \left[\frac{(1 - e^{-\alpha T/T_a})(1 - e^{-(1-\alpha)T/T_a})}{(1 - e^{-T/T_a})} \right]$$

$$\frac{d\Delta I_0}{d\alpha} = 0 \Rightarrow V_s \left[\frac{(1 - e^{-\alpha T/T_a})}{R_a} e^{-(1-\alpha)T/T_a} \times \frac{T}{T_a} + (1 - e^{-\alpha T/T_a}) \frac{\alpha T}{T_a} e^{-\alpha T/T_a} \right]$$

$$\begin{aligned} &= (1 - e^{-\alpha T/T_a}) e^{-(1-\alpha)T/T_a} - (1 - e^{-\alpha T/T_a}) e^{-\alpha T/T_a} = 0 \\ &= e^{-(1-\alpha)T/T_a} - e^{-\alpha T/T_a} \end{aligned}$$

$$\frac{(1-\alpha)T}{T_a} = \frac{\alpha T}{T_a}$$

$$\alpha = 1 - \alpha \Rightarrow 2\alpha = 1$$

$\alpha = 0.5$	ΔI_{0max}
----------------	-------------------

$$\Delta I_{0\max} = \frac{V_s}{R_a} \cdot \frac{(1 - e^{-\alpha ST/T_a})^2}{(1 - e^{T/T_a})}$$

$$= \frac{V_s}{R_a} \tan \alpha \left(\frac{T}{4T_a} \right) \quad (167)$$

$$\Delta I_{0\max} \approx \frac{V_s \times T}{R_a \cdot 4T_a} = \frac{V_s \times 1}{R_a \cdot f \times 4 \times L_a}$$

$$\boxed{\Delta I_{0\max} \approx \frac{V_s}{4L_a}} \rightarrow \text{at } \alpha = 0.5$$

from this Eqn. Ripple current $\propto \frac{1}{fL_a}$

for $L_a = \infty \Rightarrow \Delta I_{0\max} = 0$.

i.e. for Highly inductive load \rightarrow const. current.

for High frequency \rightarrow Ripple will \downarrow \therefore chopper is being operated at very high frequency i.e. in range of KHz.

\Rightarrow At very high switching frequency we can reduce the ripple in the output without increasing the size of filter. UPS operates on the same chopper principle.

Reasons for Discont. conduction

Rectifier


- $\uparrow \alpha \rightarrow$ firing angle.
- $\downarrow L$
- $\downarrow I_o$

Chopper

- $\downarrow d \rightarrow$ Duty cycle
- $\downarrow L$
- $\downarrow I_o$

RLE load \rightarrow Discontinuous conduction

(168)

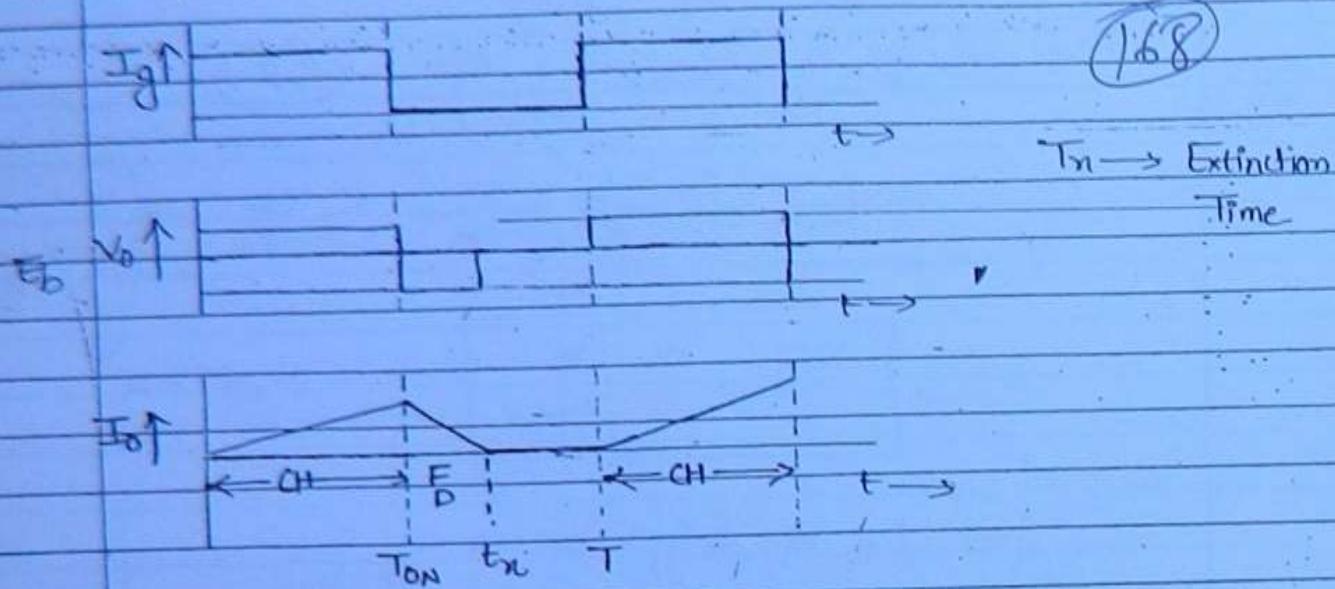


$$V_o = V_s \left(\frac{T_{ON}}{T} \right) + E_b \left(\frac{T-t_n}{T} \right)$$

$$I_{to} = \alpha V_s + E_b \left(1 - \frac{t_n}{T} \right)$$

Duty cycle limit for continuous conduction :-

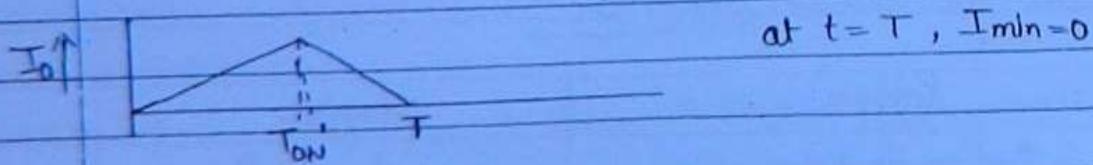Let α' be the duty cycle at the boundary b/w continuous & discontinuous conduction.



at $t = T$, $I_{min} = 0$

$$I_{min} = \frac{V_s}{R} \left(\frac{e^{T_{ON}/T_a} - 1}{e^{T/T_a} - 1} \right) - \frac{E_b}{R_a} = 0$$

$$\frac{e^{T_{ON}/T_a} - 1}{e^{T/T_a} - 1} = \frac{E_b}{V_s}$$

$$\text{at boundary, } e^{T_{ON}/T_a} - 1 = \frac{E_b}{V_s} (e^{T/T_a} - 1)$$

$$e^{T_{ON}'/T_a} = \frac{E_b}{V_s} (e^{T/T_a} - 1) + 1 \quad (TG9)$$

$$T_{ON}' = T_a \ln \left[\frac{E_b}{V_s} (e^{T/T_a} - 1) + 1 \right]$$

$$\alpha' = \frac{T_{ON}'}{T} = \frac{T_a}{T} \ln \left[\frac{E_b}{V_s} (e^{T/T_a} - 1) + 1 \right]$$


$\alpha < \alpha'$ \rightarrow Discontinuous conduction.

$\alpha > \alpha'$ \rightarrow Continuous conduction.

Step-down chopper \rightarrow with filter

Buck Regulator

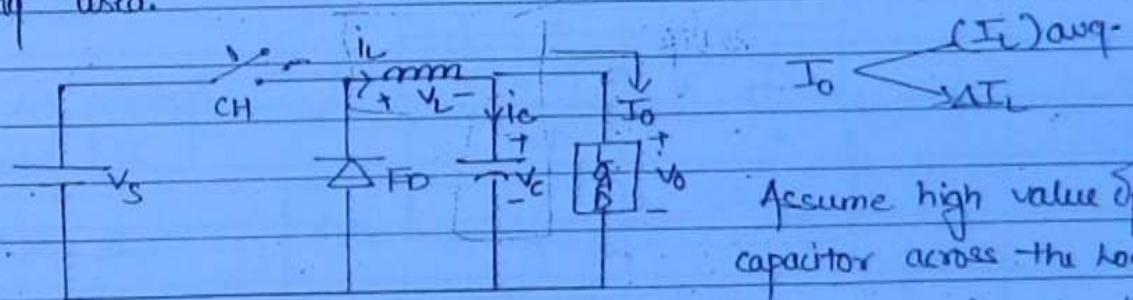In the step-down chopper, we could \downarrow the ripple in current by $\uparrow L_m$ but Ripple in v_{lg} was unaffected. \therefore to reduce Ripple in v_{lg} , step-down chopper with filter is being used.




Assume high value of capacitor across the load

which maintains almost const. v_{lg} across the load.

$(I_L)_{avg} \rightarrow$ DC component = I_o

$$\Delta I_L = \Delta I_c$$

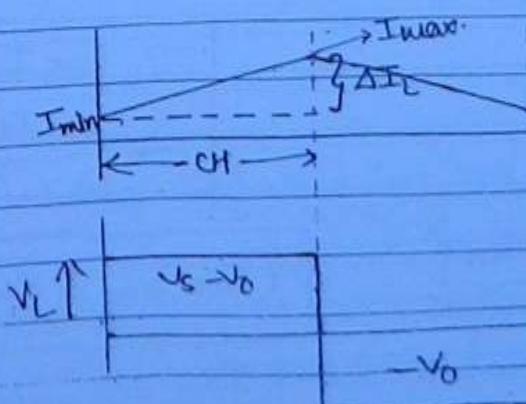

$0 < t < T_{ON}$ $CH \rightarrow ON$

$$-V_S + V_L + V_0 = 0$$

$$V_L = V_S - V_0$$

$$\frac{dI_L}{dt} = V_S - V_0$$

$$dI_L = \frac{V_S - V_0}{L} dt$$

$$I_{max} = \int_{T_{min}}^{T_{ON}} dI_L = \frac{V_S - V_0}{L} \int_0^{T_{ON}} dt$$

$$(I_{max} - I_{min}) = \frac{(V_S - V_0) T_{ON}}{L}$$

$$\Delta I_L = \left(\frac{V_S - V_0}{L} \right) T_{ON}$$

$$= \frac{V_S (1-\alpha)}{L} T_{ON}$$

$$\boxed{\Delta I_L = \frac{V_S (1-\alpha)}{fL}}$$

$$\Delta I_L \propto \frac{1}{fL}$$

$$\frac{d\Delta I_L}{d\alpha} = \frac{T_S}{fL} (1-2\alpha) = 0$$

$$\alpha = 0.5 \text{ for } \Delta I_L \Big|_{max.}$$

$$\boxed{\Delta I_{Lmax} \Big|_{\alpha=0.5} = \frac{V_S}{4fL}}$$

$$\boxed{I_S = I_{CH}}$$

 $T_{ON} < t < T$ $CH \rightarrow OFF, FD \rightarrow ON$

$$+V_L + V_0 = 0$$

$$\therefore V_L = -V_0$$

$$(V_L)_{avg} = 0$$

Ave. of true asymp = Ave. of -
true spike

$$(V_S - V_0) T_{ON} = V_0 T_{OFF}$$

$$V_0 (T_{OFF} + T_{ON}) = V_S T_{ON}$$

$$V_0 T = V_S T_{ON}$$

$$V_0 = \frac{V_S T_{ON}}{T}$$

$$\boxed{V_0 = \alpha V_S}$$

Assuming no loss in chopper
I/p power = o/p power

$$V_0 I_0 = V_S I_S$$

$$\frac{V_0}{V_S} = \frac{I_S}{I_0} = \alpha$$

CHOPPER works as DC
transformer.


$$\boxed{T_S = \alpha I_0}$$

$$\boxed{I_0 = \frac{I_S}{\alpha}}$$

$$\boxed{(I_{FD})_{avg} = (1-\alpha) I_0}$$

Ripple in capacitor voltage ($\Delta V_C = \Delta V_0$)

(171)

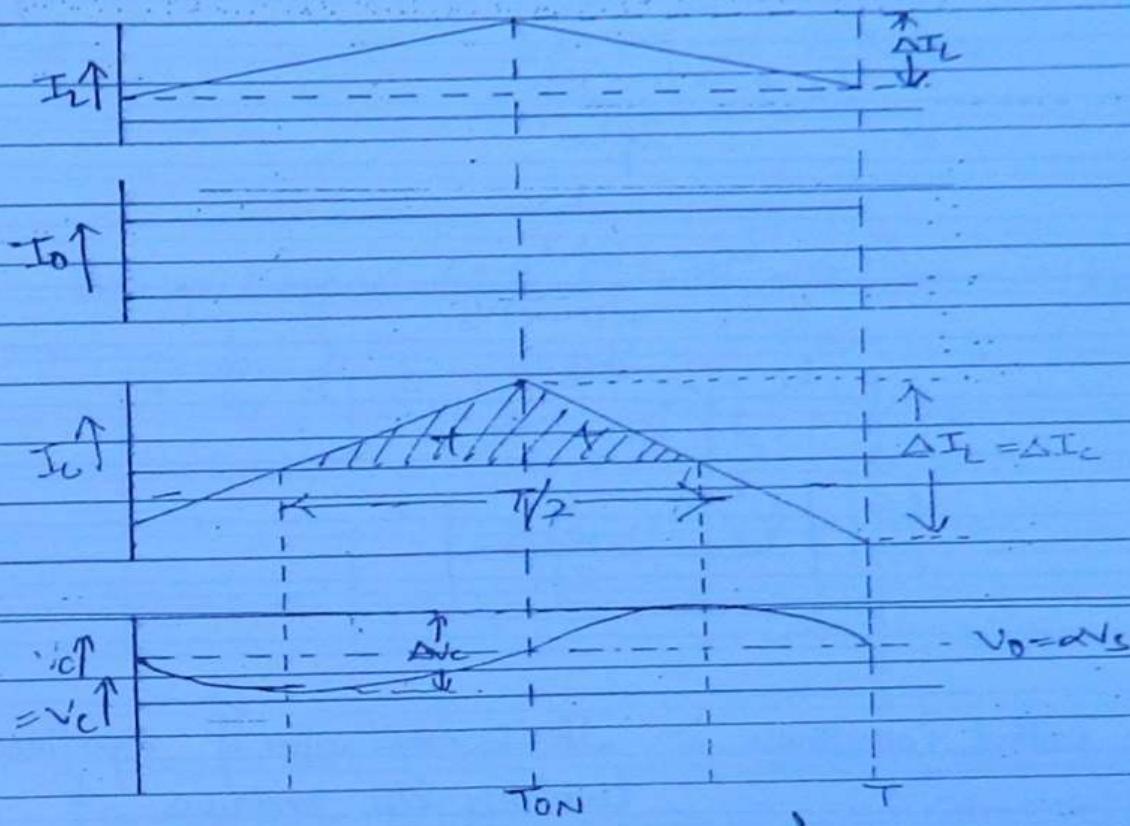

$$\Delta Q = C \Delta V_C \Rightarrow \Delta Q = \frac{\Delta I_L}{2} \times \frac{1}{2} \times \frac{T}{2} = \frac{\Delta I_L T}{8}$$

$$\boxed{\Delta V_C = \frac{\Delta I_L}{8fC}}$$

$$\Delta V_C \propto \frac{1}{fC}$$

$$\Delta V_C = \frac{\alpha(1-\alpha)V_0}{8f^2LC}$$

$$\Delta V_C|_{\text{max}} \text{ at } \alpha=0.5 = \frac{V_0}{32f^2LC}$$

Critical Inductance :- It is the value of inductance at which the inductor current waveform is just discontinuous.

Symbol $\rightarrow L_c$

At -the boundary b/w continuous & discontinuous cond'n of i

$$I_0 = \frac{\Delta I_i}{2} = (I_i)_{avg}$$

(172)

$$I_0 = \alpha(1-\alpha)V_s$$

$$2fL_c$$

1

$$L_c = 2f I_0$$

$$\alpha(1-\alpha)V_s$$

$$L_c = \frac{2f \alpha V_s R}{\alpha(1-\alpha)V_s} =$$

$$L_c = \frac{(1-\alpha)R}{2f}$$

Critical Capacitance :- It is the value of Capacitance at -the boundary b/w continuous & discontinuous conduction for -the capacitance v/q waveform.

At -the boundary :- $V_0 = \frac{\Delta V_c}{2} = (V_c)_{avg}$

$$V_0 = \alpha(1-\alpha)V_s \times \frac{1}{2}$$

$$\alpha V_s = \alpha(1-\alpha)V_s \times \frac{1}{2}$$

$$C_c = \frac{(1-\alpha)}{16f^2 L_c}$$

$\alpha = 0.5, \Delta I_c = 1.6, I_0 = 5A$


$$(I_L)_{\text{min}} = (I_L)_{\text{max}}$$

(T73)

$$(I_L)_{\text{max}} = I_0 + \frac{\Delta I_L}{2}$$

$$= \frac{1.6 \times 5}{2} = 5.8 \text{ Amp}$$

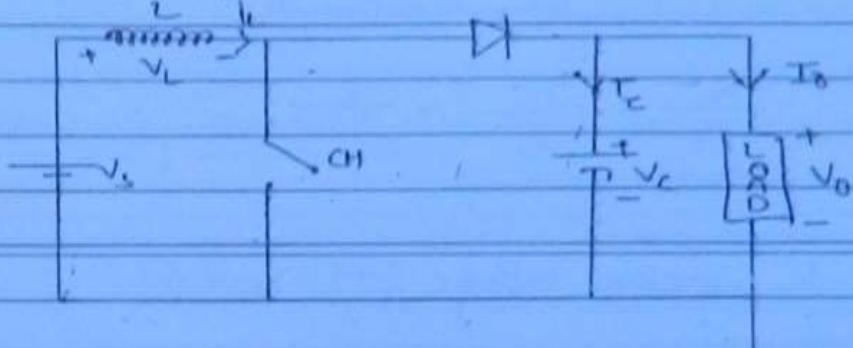3. Step-up chopper ($v_o > v_s$) (with filter) \rightarrow Boost Regulator



$$(I) \quad 0 \leq t \leq T_{ON} \rightarrow I_C = -I_0$$

CH \rightarrow ON, D \rightarrow OFF


$$V_L = V_s$$

$$L \frac{dI_L}{dt} = V_s$$

$$\int_{T_{\text{min}}}^{T_{\text{max}}} dt = \frac{V_s}{L} \int_0^{T_{ON}}$$

$$(II) \quad T_{ON} \leq t \leq T$$

CH \rightarrow OFF, D \rightarrow ON

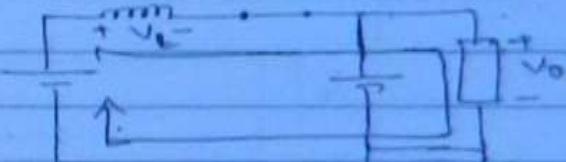

$$V_s = V_L + V_o$$

$$\Delta I_L = \frac{V_s}{L} T_{ON}$$


$$\boxed{\Delta I_L = \frac{\alpha V_s}{f L}}$$

$$V_L = V_s - V_o = -(V_o - V_s)$$

\downarrow Since it is step-up chopper,

$$V_o > V_s \Rightarrow V_L < 0$$


L is releasing energy

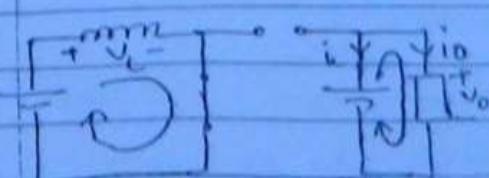

$$I_C = -I_0$$

$$I_L = I_C + I_0$$

$$I_C = I_L - I_0$$

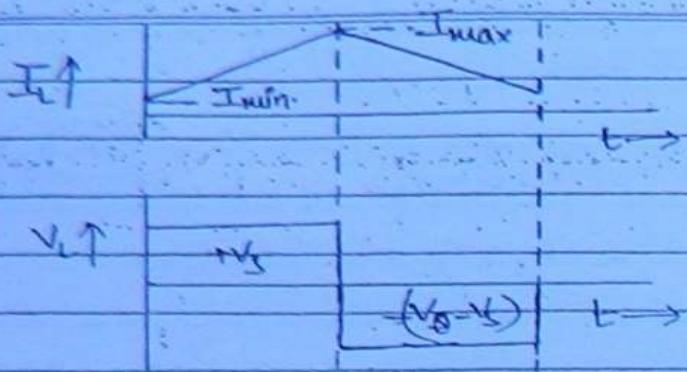

$$(V_L)_{avg} = 0$$

$$V_s T_{ON} - (V_0 - V_s) T_{OFF} = 0$$

$$V_s (T_{ON} + T_{OFF}) = T_{OFF} V_0$$


$$V_s T = V_0 T_{OFF}$$

$$V_s T = (1-\alpha) V_0 T_{OFF}$$

$$V_0 = \frac{V_s}{1-\alpha}$$

$$\frac{V_0}{V_s} = \frac{I_s}{I_0} = \frac{1}{1-\alpha}$$


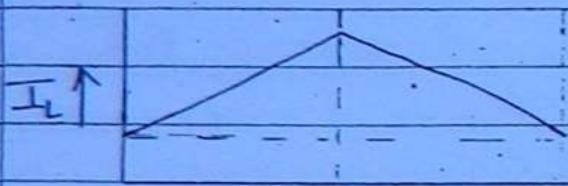
Ripple in Capacitor voltage :- ($\Delta V_C = \Delta V_0$)



$$\Delta V_C = \frac{\Delta Q}{C}$$

$$\Delta V_C = \frac{I_0 T_{ON}}{C}$$

$$\Delta V_C = \frac{\alpha I_0}{f_C}$$

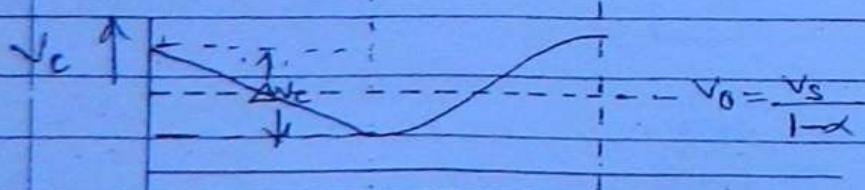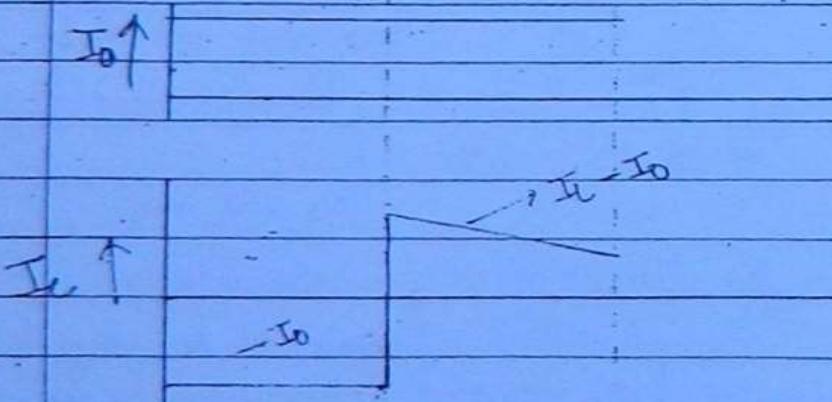

$$V_0 = \frac{V_s}{1-\alpha}$$

Critical Inductance (I_c):-

At the boundary cond's of I_L

$$I_0 = \frac{\Delta I_L}{2} = (I_L)_{av.}$$

(125)

$$\frac{V_s}{R(1-\alpha)} = \frac{\alpha V_s}{2 + L_c}$$

$$L_c = \frac{R(1-\alpha)\alpha}{2 + }$$

Critical Capacitance (C_c):-


At the boundary cond'n of V_C waveform

$$V_b = \frac{\Delta V_C}{2} = (V_C)_{av.}$$

$$\frac{I_0 R}{2 + C_c}$$

$$C_c = \frac{\alpha}{2 + R}$$

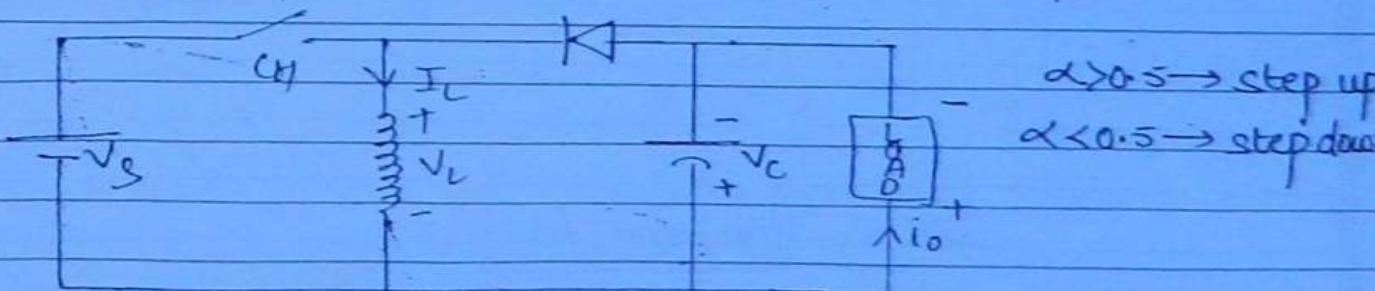
Buck-Boost Regulator (Step up / Step down chopper)



Mode-I

$0 < t < T_{on}$

Same as step-up chopper

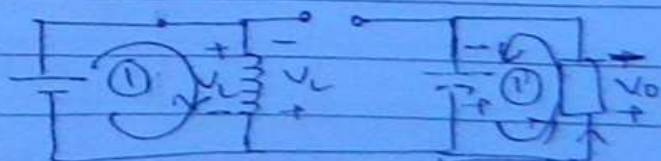

$$V_S = V_L$$

Mode-2 CH → OFF, D → ON $T_{ON} \leq t \leq T$

$$\frac{di}{dt} = \frac{V_S}{L}$$

T_{ON}


$$\int di = \frac{V_S}{L} \int dt$$

T_{ON}

$$\Delta I_L = \frac{V_S}{L} T_{ON}$$

$$\boxed{\Delta I_L = \frac{\alpha V_S}{L}}$$

$$\boxed{I_C = -I_0}$$

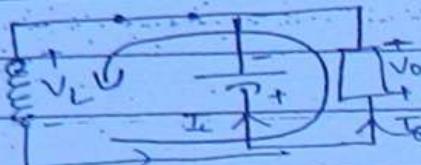


(17G)

$$\rightarrow V_L + V_0 = 0$$

$$\therefore V_L = -V_0$$

$$I_L = I_C + I_0$$

$$\boxed{I_C = I_L - I_0}$$

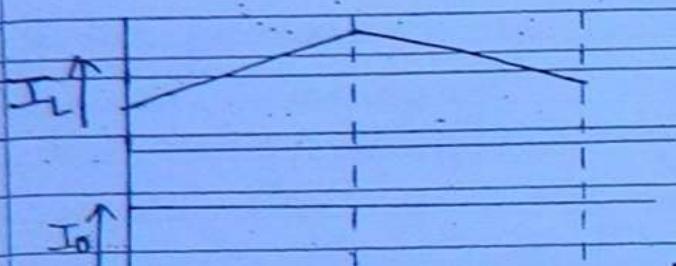


$$(I_L)_{avg} = 0$$

$$V_S T_{ON} - V_0 T_{OFF} = 0$$

$$V_S T_{ON} = V_0 T_{OFF}$$

$$V_S \alpha T = V_0 (1-\alpha) T$$

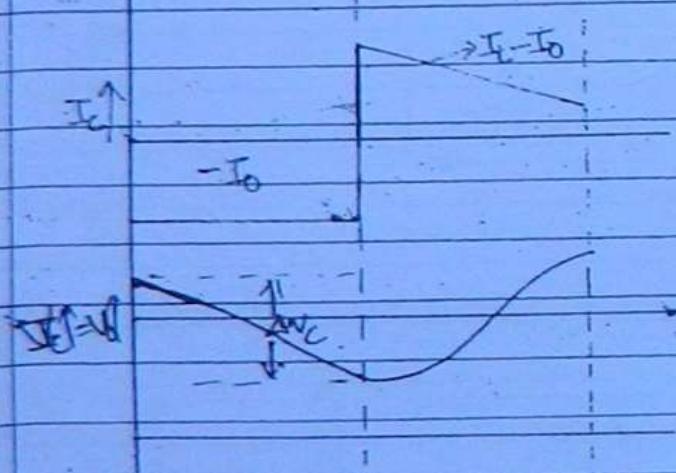

$$\boxed{V_0 = \frac{V_S \alpha}{1-\alpha}}$$

$$\frac{V_0}{V_S} = \frac{I_C}{I_0} = \frac{\alpha}{1-\alpha}$$

$$\rightarrow V_0 = \frac{\alpha V_S}{1-\alpha}$$

$$\Delta V_C = \frac{\Delta Q}{C}$$

$$= \frac{I_0 T_{ON}}{C} = \frac{\alpha I_0}{C}$$

Critical Inductance (L_c) :-

$$I_0 = \frac{\Delta I_L}{2}$$

$$\frac{\alpha V_S}{(1-\alpha)R} = \frac{\alpha V_S}{2 + L_c} \Rightarrow$$

$$\boxed{L_c = \frac{(1-\alpha)R}{2f}}$$

Critical Capacitance :-

$$V_0 = \frac{\Delta V_C}{2}$$


(177)

$$\frac{dV_S}{1-\alpha} = \alpha I_0 = I_0 R$$

$$C_C = \frac{\alpha}{2+R}$$

Classification of chopper based on quadrant operation

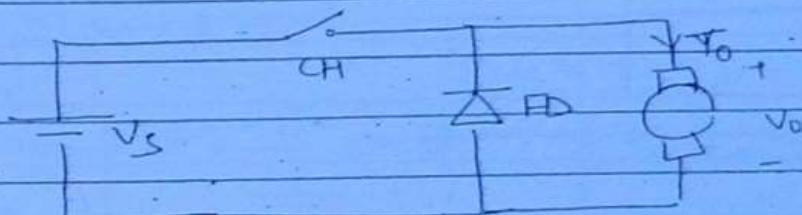I First quadrant chopper (Type A) - (Stepdown chopper)




(I) CH → ON, V_0 = V_S

∴ V_0(+ve), E_B(t) negt

II (CH → OFF) D → ON FWD [I_0(+ve)]
∴ I_0 → E_B → T + T_A + C
V_0(+ve) | V_S = E_B + I_0 R | P(+ve), Q(+ve)
I_0(+ve)

II Second quadrant operation (Type B chopper)


Regenerating Braking of DC Motor :-

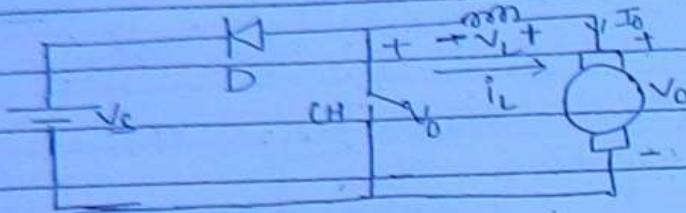

Assume that w/c is operating at rated speed b/T
T = 0 seconds.

$$\text{Mech Energy} = \frac{1}{2} J_0^2 \rightarrow \text{Brake Energy}$$

$$J_0 = \frac{V_0 - E_b}{R_a}$$

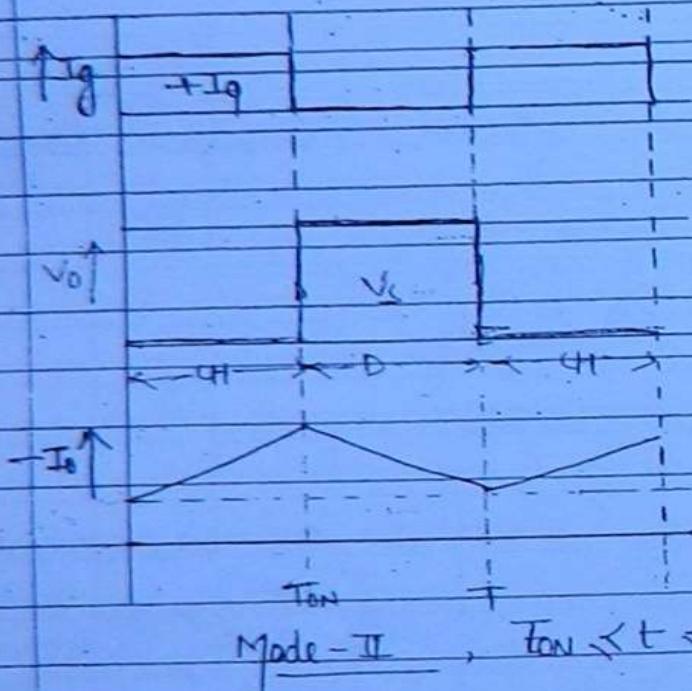


Mode-I

CH → ON, D → off


0 < t < TON
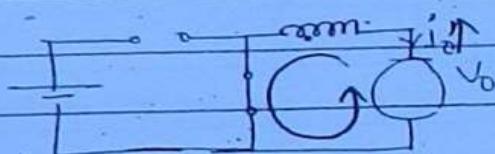
$$\therefore I_0 \leftarrow \text{ve}, \therefore T_a \rightarrow \phi I_0 \\ t \text{ ve}$$



$$\frac{1}{2} J_0^2 \rightarrow \frac{1}{2} L_i^2$$

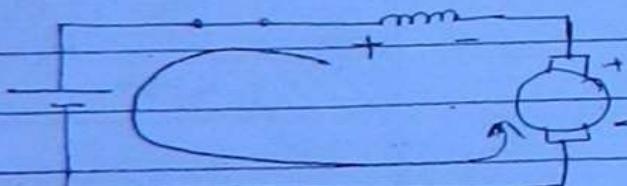
Mode-II, $T_{ON} < t < T$, CH → OFF, D → ON



$$V_0 = V_s$$

$$\frac{1}{2} L_i^2 \rightarrow \text{Source}$$

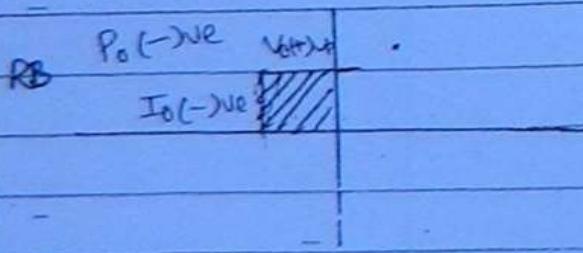
Brake Energy to source
Regenerative Braking




$$V_0 = V_s (T_{off}/T) = (1-\alpha) V_s$$

$$\begin{aligned} \text{Regenerated power} &= V_0 I_0 \\ &= V_s (1-\alpha) \cdot I_0 \end{aligned}$$

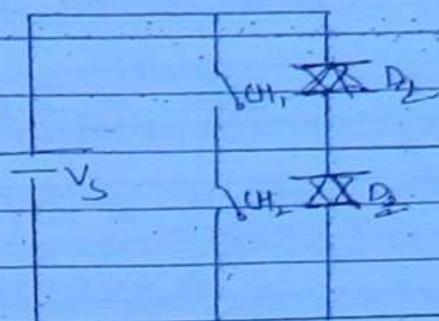III → Two quadrant operation (Type-C Choppers)



(179)

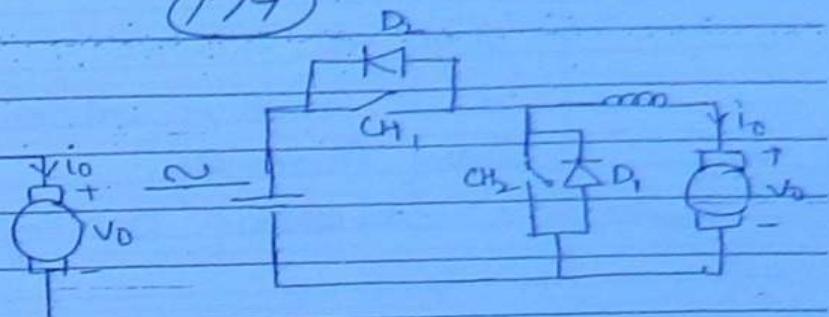

I $CH_2 \rightarrow ON$
 $I_0 \rightarrow (-)ve, T_a \leftarrow (+)ve$
 $\therefore \frac{1}{2} JW^2 \rightarrow \frac{1}{2} Li^2$

II $CH_2 \rightarrow OFF$
 $D_2 \rightarrow ON$
 $B_2 Li^2 \rightarrow SOURCE$

$V_0 \uparrow$


I $\rightarrow CH_1 \rightarrow ON, D_2 \rightarrow OFF$

$I_0 (+)ve, V_0 (+)ve, E_b (+)ve, T_a (+)ve, w(t)ve$


II $CH_1 \rightarrow OFF$

D $\rightarrow ON$ (FWP)

$$\Delta V_s = E_b + I_0 R_q$$

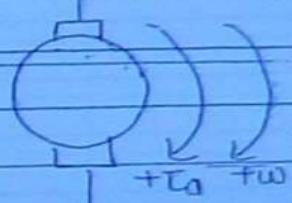


(RB)

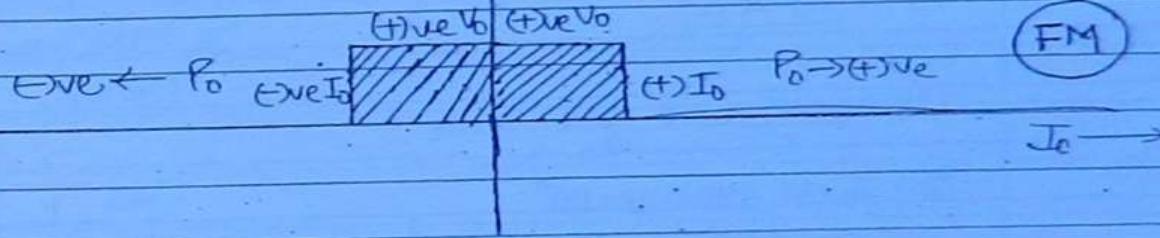

(FM)

$J_0 \rightarrow$

IV → Four quadrant Chopper (Type-D)

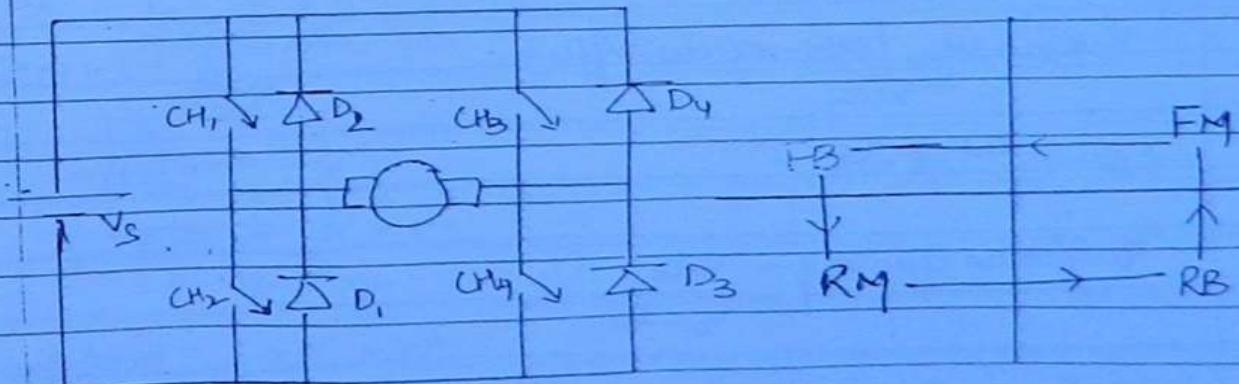

Ques 10

$$S-\phi \text{ asymmetrical}$$

$$T_A \neq 0 \Rightarrow I_A \neq 0$$

$$I_A(\omega t) = 0$$

$$\text{at } \omega t = \beta, I_{A(\omega t)} = 0$$

i.e. it is discontinuous.

During discontinuity,

$$\text{load voltage} = \text{Back Emf}$$

$$R_{\text{load}} = 100 \Omega, FSD \rightarrow 1 \text{ mA}$$

Project → measure AC voltage :

It will measure DC voltage only.

$$V_{d0} = \frac{2V_m}{\pi} = T_f (100 + R_s)$$

$$\frac{2 \times 100 \sqrt{2}}{\pi} = 10^3 (100 + R_s)$$

$$R_s = 89.9 \text{ k}\Omega$$

Ques 11 $\alpha > 90^\circ \rightarrow$ Inversion mode

$$P_{AC} \leftarrow P_{DC}$$

$$V_0 = -E + T_0 \sin \alpha \quad \text{--- (1)}$$

$$\Delta V_{d0} = 4T_0 \sin \alpha$$

$$V_0 = V_{d0} \cos \alpha - 4T_0 \sin \alpha$$

$$V_{d0} = \frac{2V_m}{\pi}$$

\times

$$= \frac{2 \times 120 \sqrt{2}}{\pi}$$

\times

$$V_0 = \frac{240 \sqrt{2} \cos 110^\circ - 4 \times 50 \times 10^{-3} \times T_0}{\pi}$$

$$-80 + T_0 \times F = 240 \sqrt{2} \cos 110^\circ$$

\times

$$T_0 (1+2) = \frac{240 \sqrt{2} \cos 110^\circ + 80}{\pi}$$

$$T_0 = 85.87 \text{ A}$$

$$\Delta V_{d0} = \frac{V_{d0}}{2} [\cos \alpha - \cos (\alpha + 110^\circ) = 4T_0 \sin \alpha$$

$$\alpha = 90^\circ - 25^\circ$$

$$V_0 = \sqrt{V_{d0} (1 + \cos \alpha)}$$

$$\frac{1}{2} \left[\frac{2V_m \sin \alpha}{\pi} \right] = \frac{2V_m \sin \left(90^\circ - 25^\circ \right)}{\pi}$$

$$\sqrt{V_{d0}} = \frac{\sqrt{2} V_m \sin \alpha}{\pi} = \frac{1}{2} = \cos (90^\circ - 30^\circ)$$

$$\alpha = 67.7^\circ$$

$$T_0 = \frac{V_0}{R} = \frac{7.74}{100} \text{ Amp.}$$

$$\text{Rectification Efficiency} = \frac{V_0 T_0}{V_{0F} T_{0F}}$$

$$= 55.05 \%$$

$$T_{0F} = \frac{V_{0F}}{R} = 10.48 \text{ Amp.}$$

$$\alpha_{max} = 180^\circ - (\omega t q + \alpha_0)$$

$\alpha_0 \rightarrow$ overlap angle at $\alpha=0^\circ$

$$V_0 = E_b + I_0 R_a$$

$$V_0 = V_{dc} \cos \alpha - 3fL_s I_0$$

$$E_b + I_0 R_a = V_{dc} \cos \alpha - 3fL_s I_0$$

$$I_0 = \frac{V_{dc} \cos \alpha - E_b}{R_a + 3fL_s}$$

$$V_{dc} = \frac{B \sqrt{mL}}{2\pi} = 202.5 \text{ V}$$

$$I_0 = 14.77 \text{ A}$$

$$\text{at } \alpha=0^\circ = \alpha = 30^\circ$$

(T81)

$$I_0 = (0.8 \alpha - 0.8 \sin(\alpha + \alpha))$$

$$I_0 = 0.134$$

$$\text{at } \alpha=30^\circ$$

$$0.134 = \cos 30^\circ - \cos(30^\circ + \alpha)$$

$$\alpha = 12.94^\circ$$

$$V_{dc} (\cos \alpha - \cos(\alpha + \alpha)) = 3fL_s I_0$$

$$\alpha \Big|_{\alpha=0^\circ} = 17^\circ$$

$$\text{at } \alpha=60^\circ$$

$$0.134 = \cos 60^\circ - \cos(60^\circ + \alpha)$$



$$\alpha = 8.53^\circ$$

$$\omega t q = 2\pi \cdot 250 \times 10^6 \cdot \frac{180}{\pi} \\ = 4.5^\circ$$

$$\alpha_{max} = 180 - 4.5 - 17^\circ \\ = 158.5^\circ$$

Choppers :-


1.

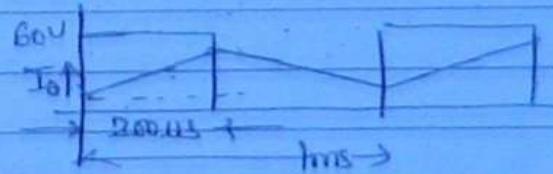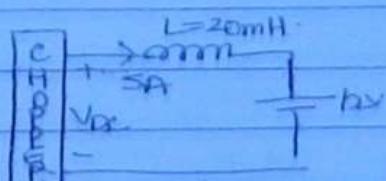

$$CH \rightarrow ON, V_{DC} = 60V$$

$$\Delta I_L = \frac{48}{20 \times 10^{-3}} \times \frac{10}{200 \times 10^{-6}}$$

$$= 480 \times 10^{-3} = 0.48A$$

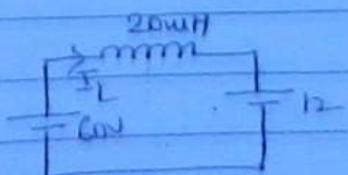

$$60 - 12 = L \frac{di}{dt}$$

$$\Delta I_L = \frac{48}{20 \times 10^{-3}} \times T_{ON}$$

$$V_s = 100V$$

$$\alpha = 0.8$$

$$(I_{FD}) = I_0 \frac{(T_{qH})}{T}$$

$$= I_0 (1-\alpha)$$

$$I_0 = \frac{\alpha V_s}{R}$$

$$= 0.8 \times 100 = 8$$

$$(I_{FD})_{av} = 8(1 - 0.8) \\ = 1.6A$$

3 CLASS-D Commutation \rightarrow v/q commutation

$$V_0 = V_s \left[\frac{T_{qH} + 2t_{cm}}{T} \right]$$

$$(V_0)_{min} = 250 \left[\frac{140 \times 10^{-6} + 2t_{cm}}{10} \right] \times 10^3$$

$$t_{cm} = C V_s = \frac{10^{-6} \times 250}{I_0} \\ = 25 \times 10^{-6}$$

$$(V_0)_{min} = 47.5V$$

$$(I_{TM})_{peak} = I_0 + V_s \sqrt{\frac{1}{L}} = 10 + 200 \sqrt{\frac{10^{-7}}{10^{-3}}} = 10 + 200 \times 10^{-2} = 12A$$

$$(I_{TA})_{peak} = I_0 = 10A$$

Step-down chopper $\rightarrow \alpha = 0.5$

$$I_0 = \frac{\alpha V_s}{R} = \frac{0.5 \times 60}{3} = 10A$$

A_q value will not depend on Inductance.

$$T_{qH}' = T_A \ln \left[1 + \frac{E_b}{V_s} \left(e^{T/T_A} - 1 \right) \right]$$

$$T_A = \frac{L}{R} = \frac{10^{-3}}{0.25} = 4 \times 10^{-3}$$

$$\frac{I}{T_A} = \frac{2.5 \times 10^{-3}}{4 \times 10^{-3}} = 0.625$$

$$T_{qH}' = 332.5 \mu\text{sec}$$

$$\underline{9} \quad d = \frac{1}{3} \Rightarrow VRF = \sqrt{1-d} = \sqrt{5-1} = 2$$

(183)

$$\underline{10} \quad t_{min} = \pi \sqrt{L C}$$

$$t_{max} = \pi \sqrt{L C} + \sqrt{L C} \sin^{-1} \left(\frac{I_0}{I_p} \right)$$

$$I_p = V_s \sqrt{C} = 230 \times \frac{\sqrt{10 \times 10^{-6}}}{\sqrt{25.28 \times 10^{-6}}} \\ = 144.66$$

$$t_{max} \approx 75 \mu s.$$

$$t_{min} = 50 \mu s$$

$$\underline{11} \quad L = 64 \mu H.$$

$$(I_m)_{peak} = I_0 + V_s \sqrt{C} = 70.7 + 200 \sqrt{\frac{64 \times 10^{-6}}{16 \times 10^{-6}}} \\ = 140.7 A$$

$$\underline{12} \quad c) \quad t_{CM} = \frac{CV_s}{I_0} = \frac{50 \times 10^{-6} \times 220}{80} = 137.5 \mu sec.$$


$$t_{CA} = \frac{\pi \sqrt{L C}}{2} = \frac{\pi \sqrt{20 \times 50}}{2} \times 10^{-6} = 49.67 \mu sec.$$

$$a) \quad T_{ON|_{effective}} = T_{ON} + 2t_{CM} \\ = 800 + 2 \times 137.5 = 1075 \mu s$$

$$(I_m)_p = I_0 + V_s \sqrt{C} = 427.85 Amp.$$

$$(I_{TA})_p = I_0 = 8 Amp.$$
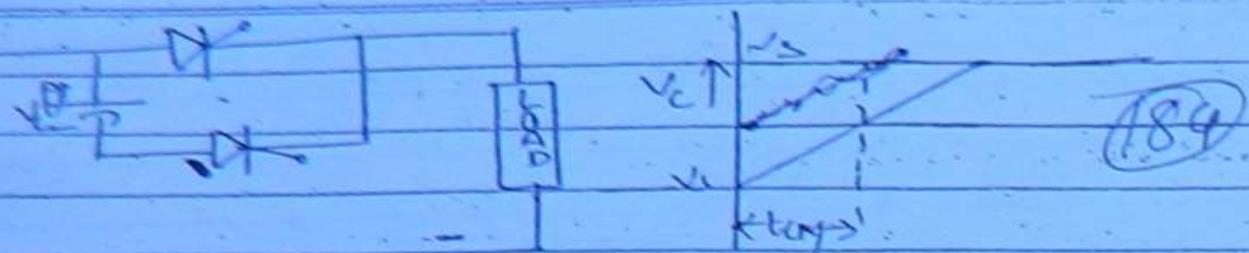
$$\text{Total Commutation interval} = 2t_{CM} \\ = 2 \times 137.5 = 275 \mu s.$$



$$V_C = \frac{V_s}{R} \cdot t \Rightarrow V_C = \frac{220}{15} \cdot 150 - 220$$

$= 20V$



AC VOLTAGE CONTROLLERS

(185)

fixed AC \rightarrow variable AC (V_o, f_o)

I Phase Control Technique -

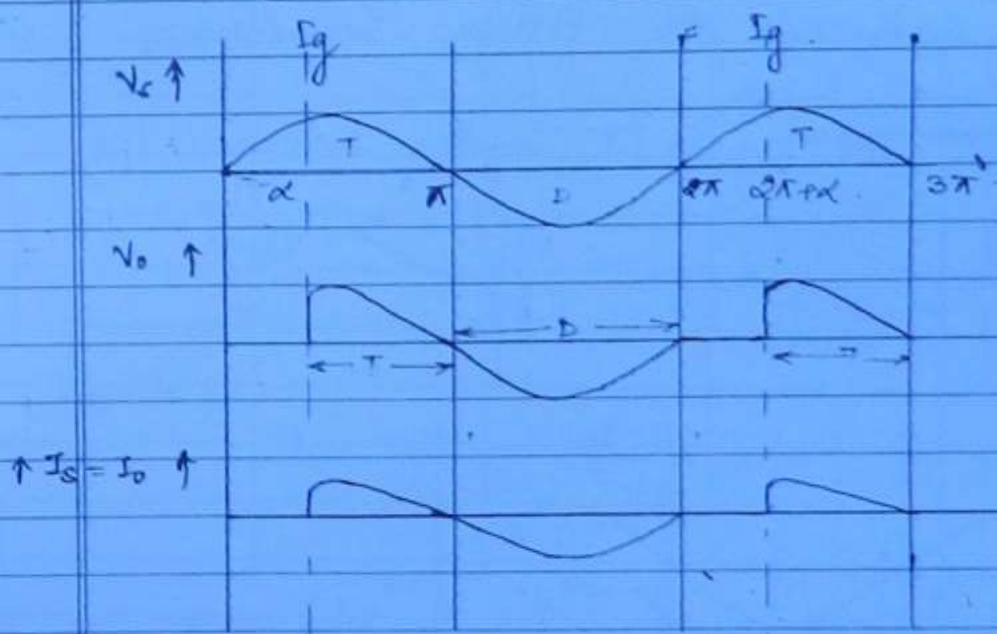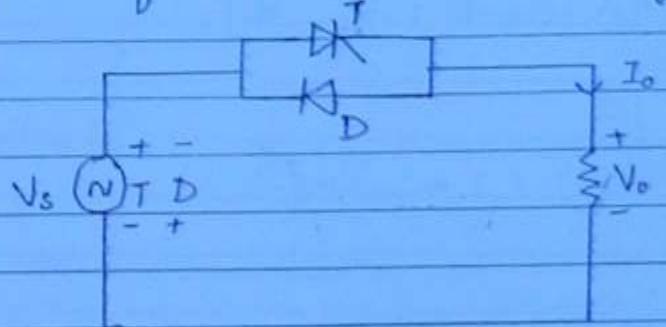a) 1-φ Half Controlled Ac Voltage Controllers -



$$V_o = \frac{1}{\alpha \pi} \int_{\alpha \pi}^{2\pi} V_m \sin \omega t \, d(\omega t) = \frac{V_m}{\alpha \pi} (\cos \alpha - 1)$$

$$(I_s)_{avg} = I_o = \frac{V_m}{\alpha \pi R} (\cos \alpha - 1)$$

DC component

Drawback -

Source current contains DC component & saturates the supply transformer core.

(18)



$$V_{0x} = \frac{1}{\sqrt{2\pi}} \int_{-\infty}^{\infty} V_m \sin^2 \omega t d(\omega t)^{\frac{1}{2}}$$

$$V_{0x} = \frac{V_m}{2\sqrt{\pi}} \left[(\omega T - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$

$$\text{PF} = \frac{V_{0x}}{V_{0x}} = \frac{1}{\sqrt{2\pi}} \left[(\omega T - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$

(b) 1-Φ Full Controlled AC Voltage Controller -

1. R Load

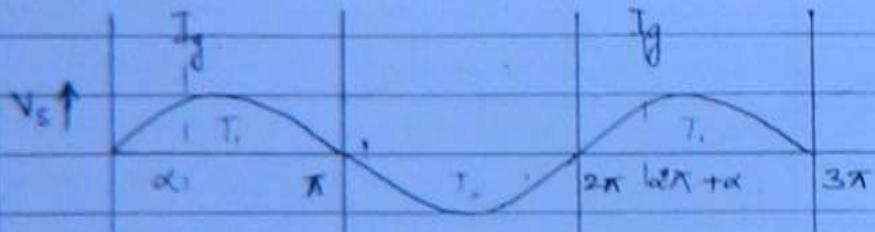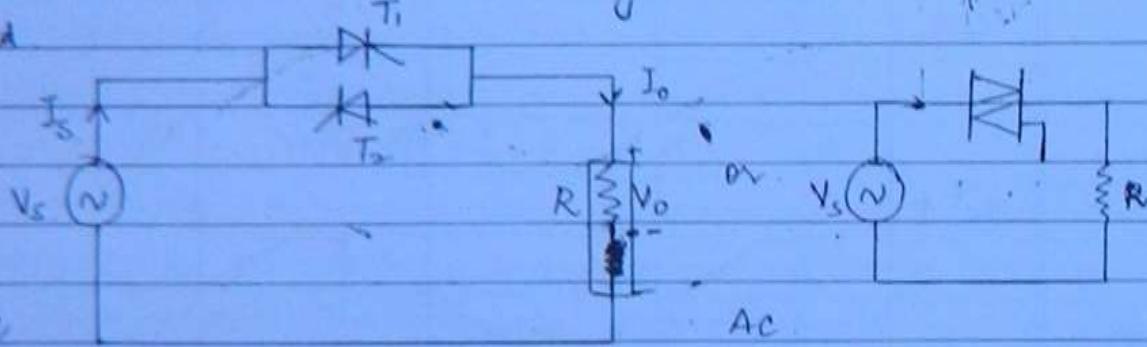

$$I_S = I_o$$



Q. RL load.

After reaching steady state I_o lags V_o by
 $\phi = \tan^{-1} \frac{wl}{R}$.

(I) $\alpha > \phi$, V_o is controlled

(II) $\alpha \leq \phi$, V_o is uncontrollable.

(187)

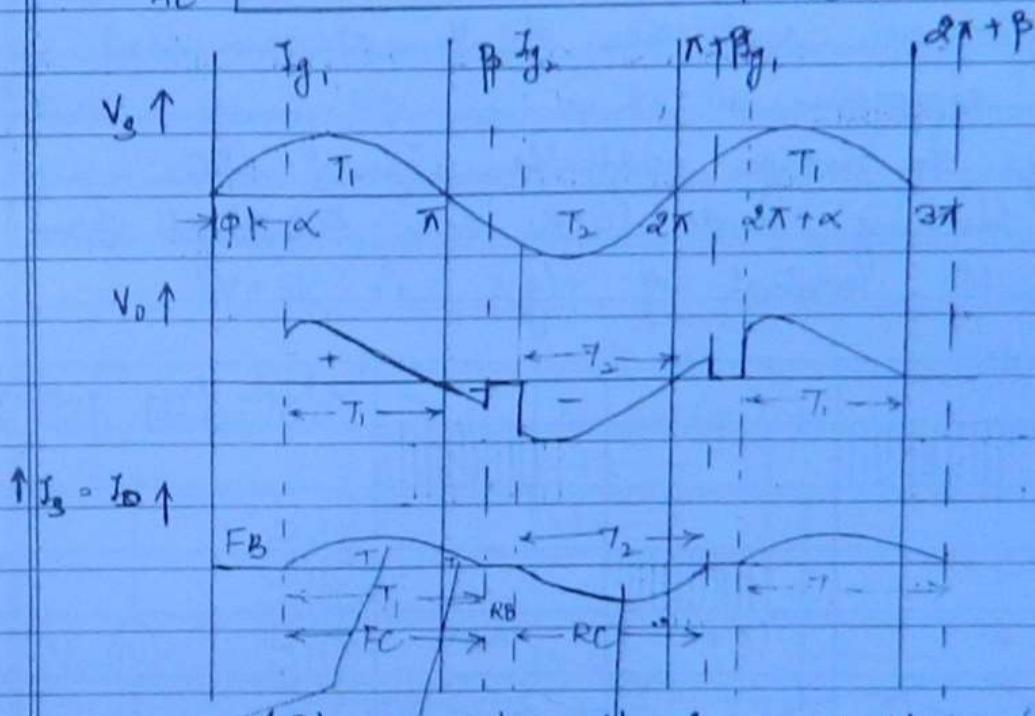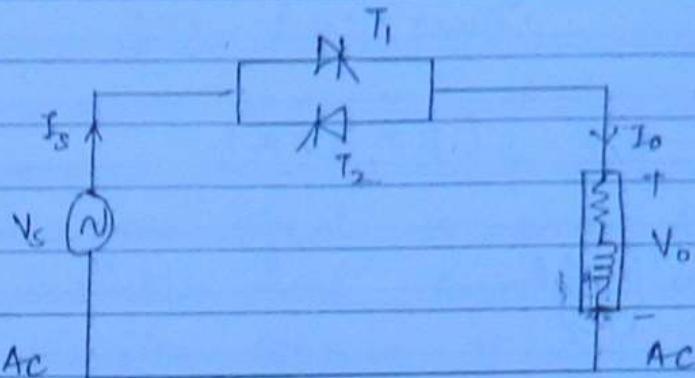

$P(+)$ power flows from source to load
 $P(-)$ power again flows from source to load
 $I_o \rightarrow V_o$ (Inductor changes polarity).

$$V_{o\alpha} = \left\{ \frac{1}{\pi} \int_{-\pi}^{\pi} V_m^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

(188)

$$V_{o\beta} = \frac{1}{2\pi} \int_{-\pi}^{\pi} V_m \left[(\beta - \alpha) + \frac{1}{2} (\sin \alpha - \sin 2\beta) \right]^{1/2}$$

II $\phi > \alpha$

$L \uparrow T \uparrow \beta \uparrow (\beta > \pi + \alpha)$

$$\tan \phi = \frac{\text{tanh}(\omega L)}{R}$$


→ continuous conduction of V_o occurs as

β approaches $\pi + \alpha$

Only 2 modes available FC & RC

No blocking mode (SCRs are short circuited)

∴ No control of vgs. ∴ $V_o = V_d$

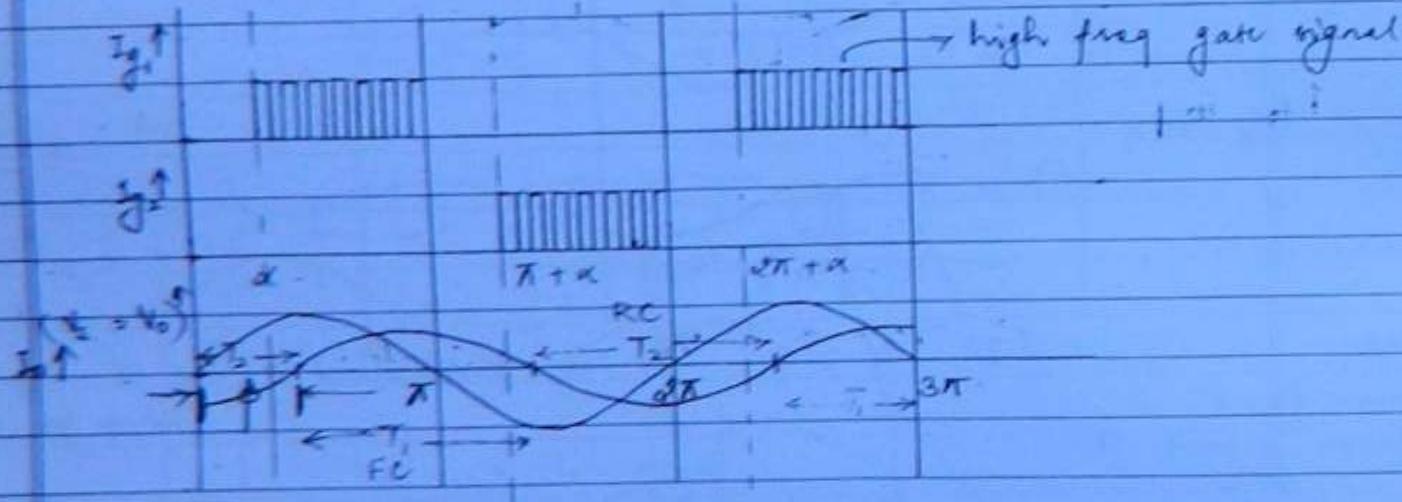

When T_1 stops conducting, but there is no gate signal for T_2 (I_{g2}), T_2 fails to turn-on if it behaves as a rectifier.

To avoid this continuous gate signal is given but that + power loss & also may saturate pulse timer

We get max" output v_o than its uncontrolled

$$(V_o)_{max} = (V_s)_{max} = \frac{V_m}{\sqrt{2}}$$

(189)

$$(I_{ex})_{max} = I_{ex} = (V_o)_{max}$$


|Z|


$$|Z| = \sqrt{R^2 + (WL)^2}$$

NOTE

If pulse gate signal is given to AC v_g controller with inductive load, then it may behave as half wave rectifier because if one of the SCRs fails to turn-on due to the absence of gate signal at that instant. To avoid this problem we can give either continuous gate signal or high frequency gate signal.

c) Two stage AC v_g controller -

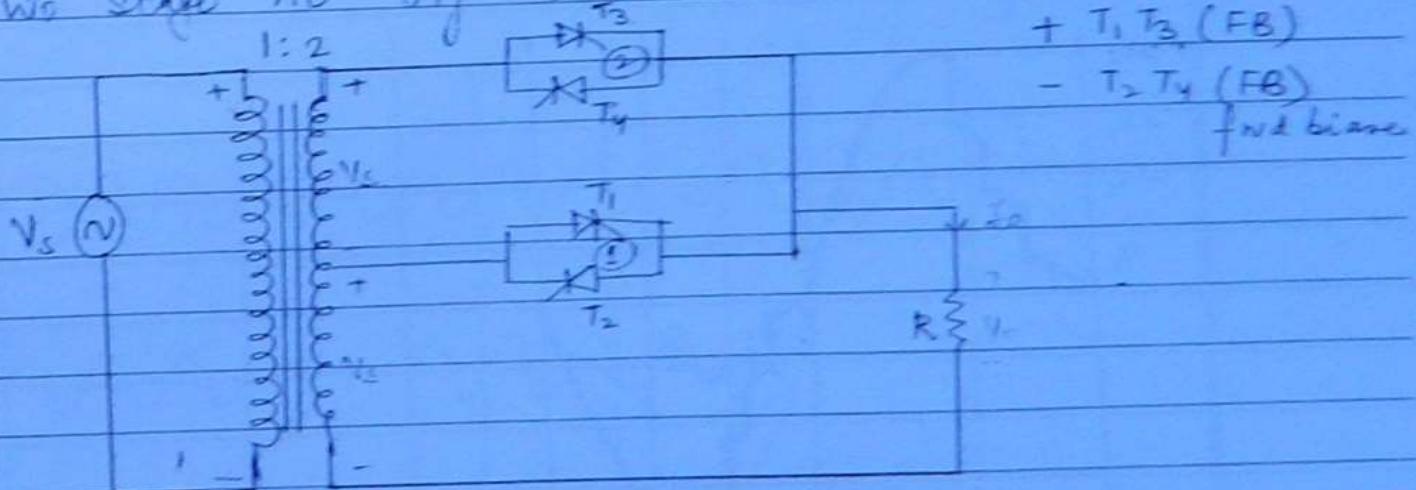

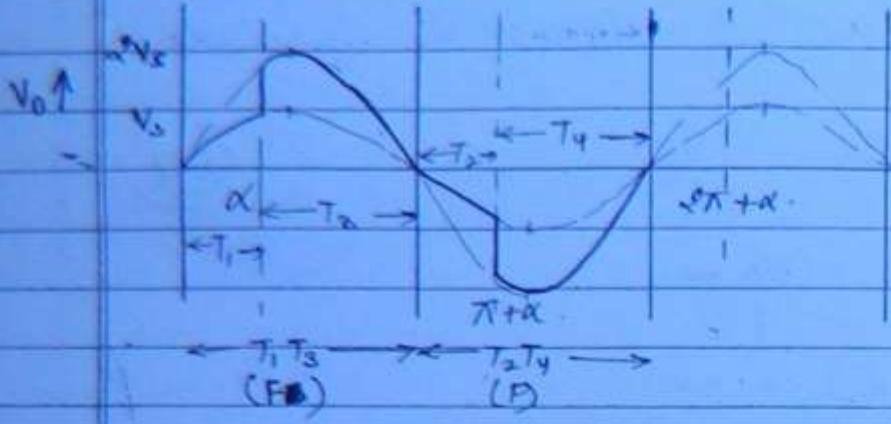


* Since waveform is approaching sine wave,
the smoothness \uparrow with no. of stages
Thus harmonic distortion \downarrow .

$$V_{oN} = \left\{ \frac{1}{2\pi} \left[\int_{-\alpha}^{\alpha} V_m^2 \sin^2 \omega t \, d(\omega t) + \int_{-\alpha}^{\pi} 4V_m^2 \sin^2 \omega t \, d(\omega t) \right] \right\}^{1/2}$$


$$= V_m \left\{ \frac{1}{2} [\alpha - \frac{1}{2} \sin \alpha] + 4 \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right] \right\}^{1/2}$$

d) Multistage Regulation -

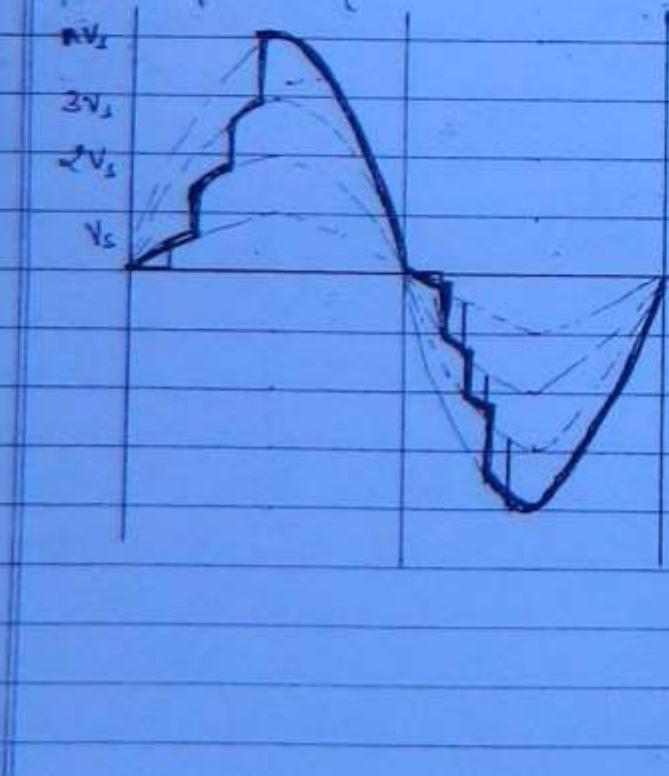

II Integral Cycle Control (ON/OFF)



T91

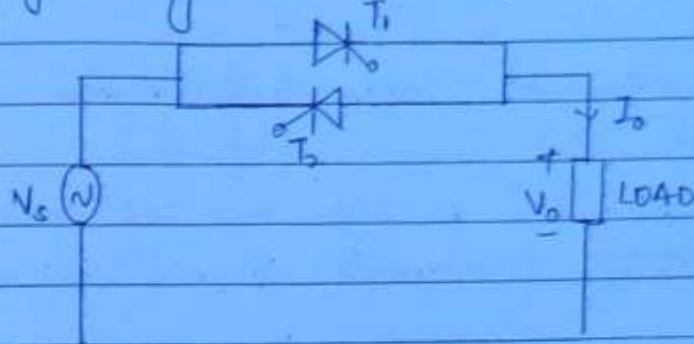

m cycles (ON) [$m = 3$]
n cycles (OFF) [$n = 2$]

$$I_g, (0, 2\pi, 4\pi, \cancel{6\pi}, \cancel{8\pi}, 10\pi, 12\pi, 14\pi, \cancel{16\pi}, \cancel{18\pi}, \dots)$$
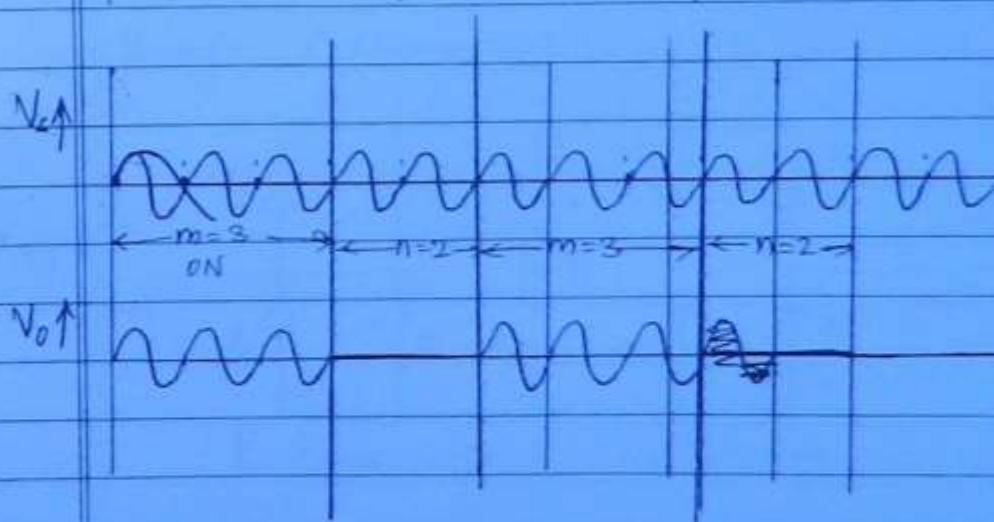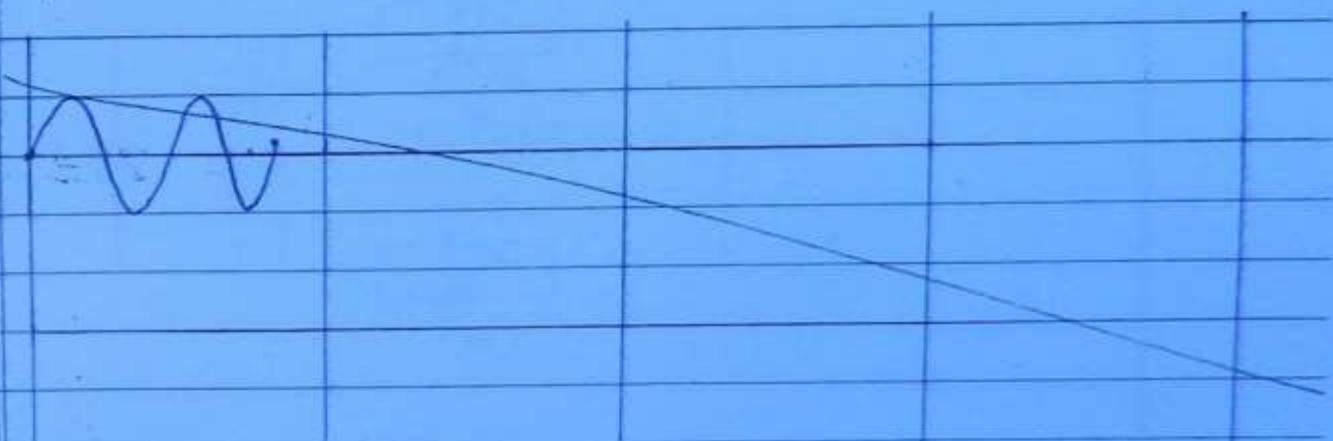
$$I_g, (\pi, 3\pi, 5\pi, \cancel{7\pi}, \cancel{9\pi}, 11\pi, 13\pi, 15\pi, \cancel{17\pi}, \cancel{19\pi}, \dots)$$



$$V_{o_n} = V_{s_n} \left(\frac{m}{m+n} \right)^{\frac{1}{2}}$$

$$V_{o_n} = \sqrt{k} V_{s_n} \quad \text{when } k = \frac{m}{m+n}$$

Applications -

(A92)

It can be used for AC loads with ^{high} ~~large~~ time constant.

e.g. It can be used for a big size of motor with high MOI & mech time constant.

Limitations -

We cannot get wide range of control i.e. control is limited.

CYCLOCONVERTER


(93)

Fixed Ac \rightarrow Variable Ac
 (V_s, f_s) , (V_o, f_o)

$f_o < f_s \Rightarrow$ step down cycloconverter

$f_o > f_s \Rightarrow$ step up cycloconverter


Mid - Point Cycloconverter -

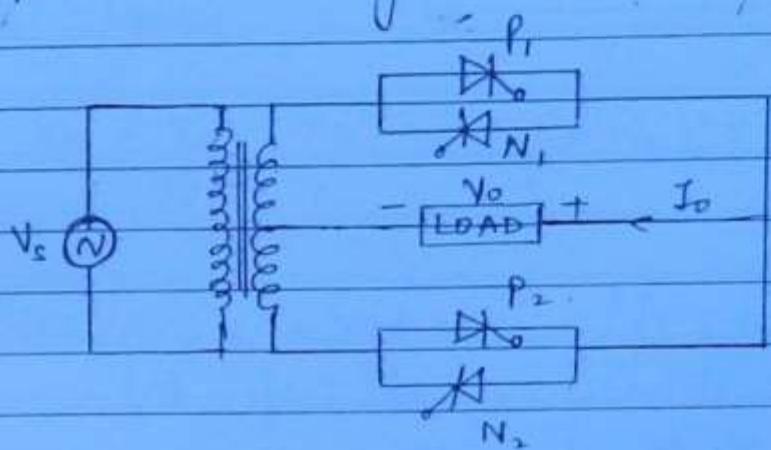

Bridge Cycloconverter

+ $P_1 P_2$ N, N_2 (E)


- $P_3 P_4$ $N_3 N_4$ (F)

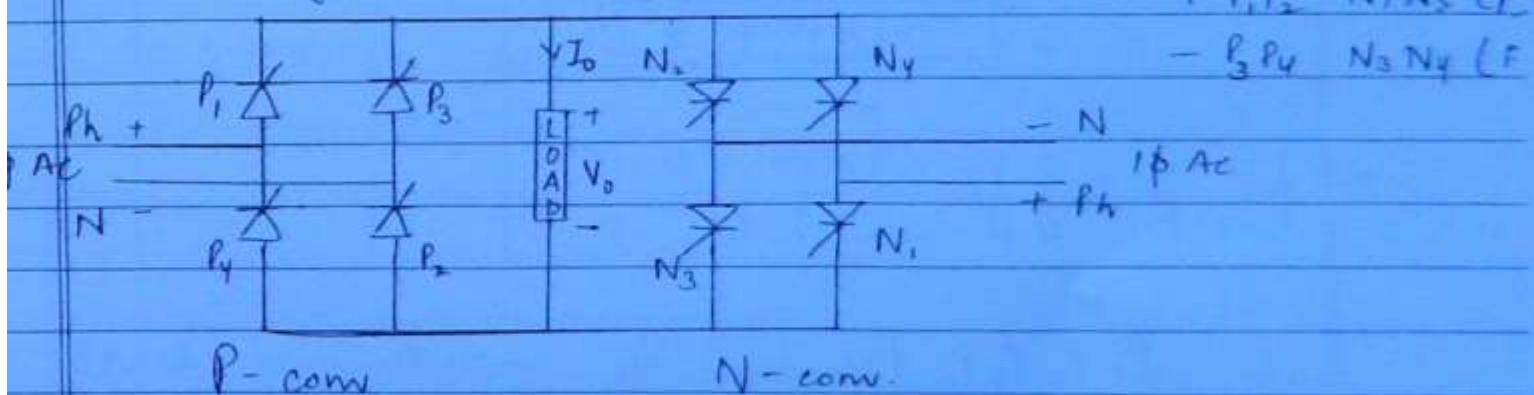

Stepdown cycloconverter ($f_o < f_s$)


$$\text{let } f_o = \frac{1}{3} f_s \quad \therefore \quad T_o = \frac{3}{8} T_s$$

18y

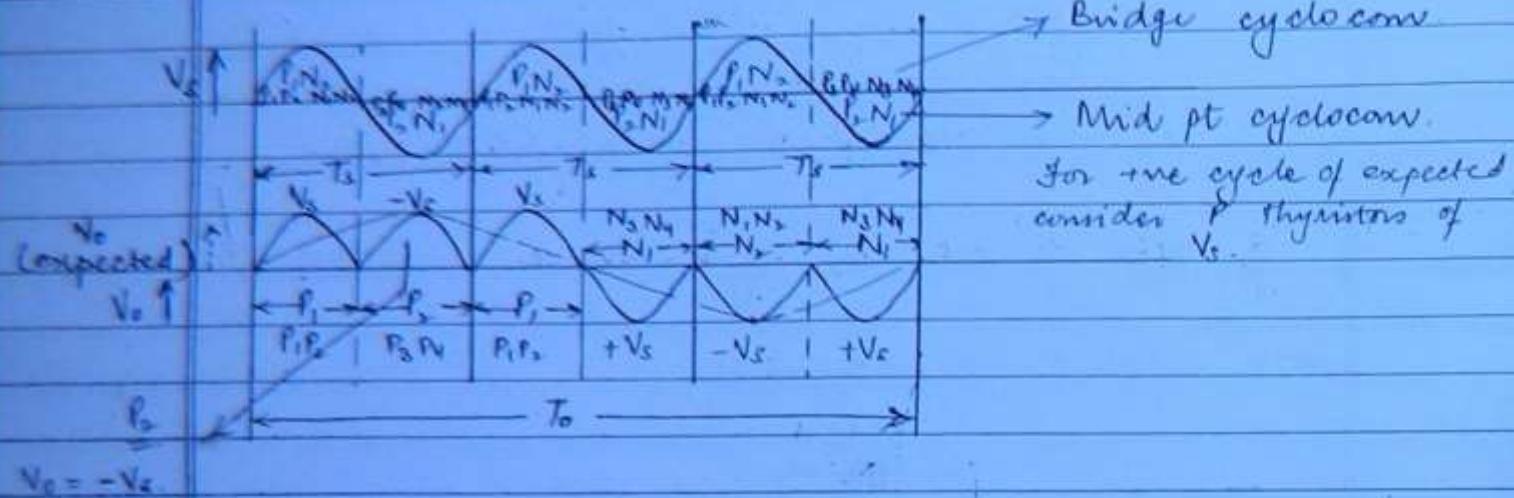


Shortcut →
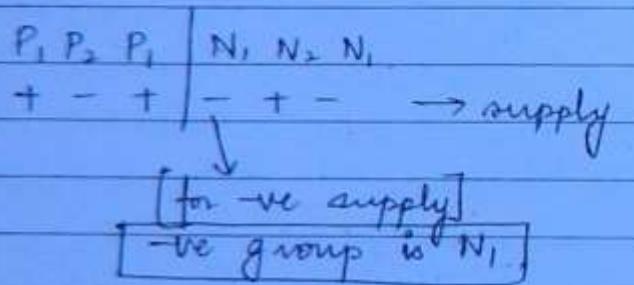
$$\Rightarrow \text{for } f_o = \frac{1}{3} f_s$$


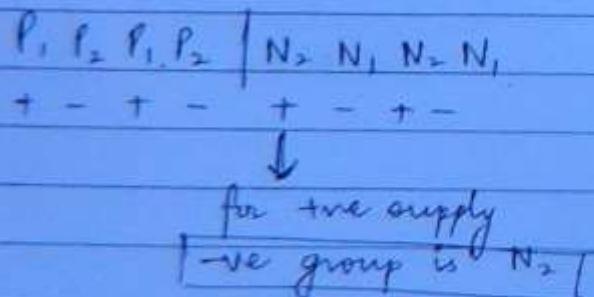
$$\Rightarrow \text{for } f_o = \frac{1}{4} f_s$$



Here only frequency is varied as α is kept 0 but
is maintained in both V_o & f_o is required with
this scheme say N

(P95)

R-load -


$$V_{oR} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin \alpha \right]^{\frac{N}{2}}$$

RL-load -

$$V_{oR} = \frac{V_m}{\sqrt{2\pi}} \left[(\beta - \alpha) + \frac{1}{2} (\sin \alpha - \sin \beta) \right]$$

Step Up Cycloconverter - ($f_2 > f_1$)
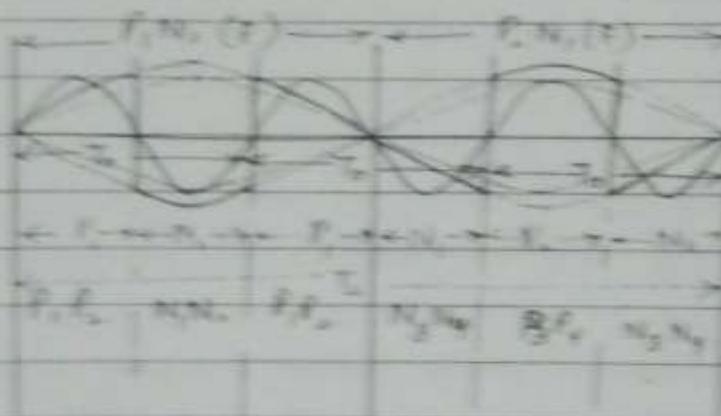
$$\text{Let } f_2 = 3f_1 \quad \therefore T_2 = \frac{1}{3} T_1 \quad \therefore T_0 = 3T_0$$



- Switch commutation is required in step up cycloconverters.
- Harmonic distortion is more in cycloconverters than may appear at low f_2 .


Applications -

(196)

It's used for high speed power, low speed and reversible AC drives.
eg. In SF J.M for controlling speed.

AC DRIVES -


1. Stator voltage control of I.M -

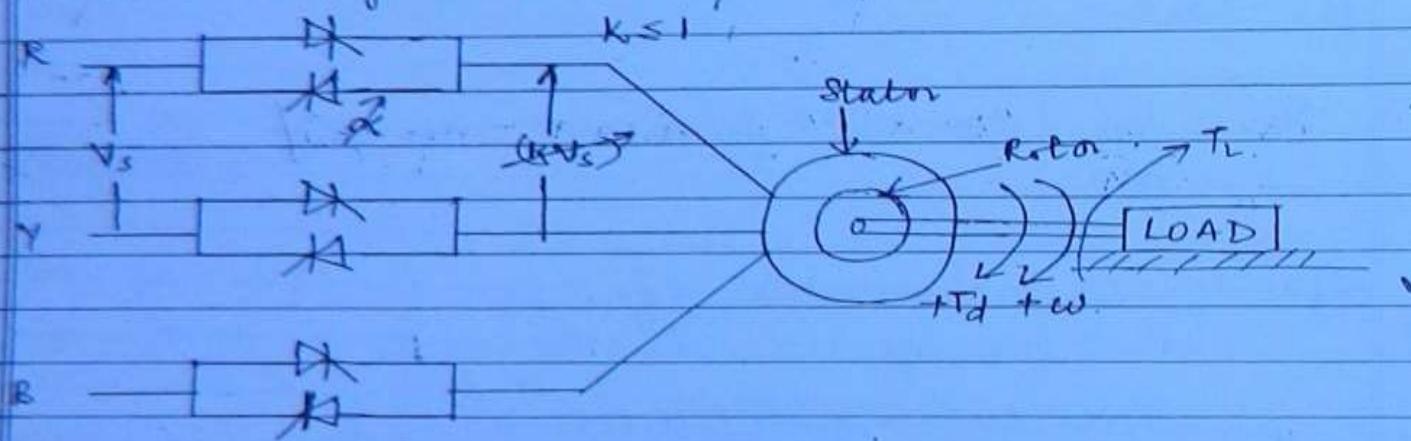

At starting $T_d > T_L$ $\omega \uparrow$

After reaching steady state speed $T_d = T_L$

$T_d < T_L$ $\omega \downarrow$

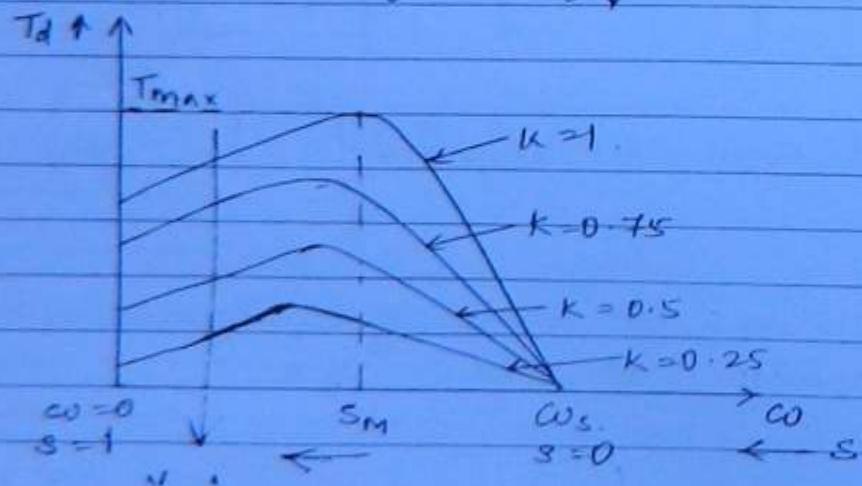

$$T_d = \frac{3}{w_s} \frac{(KV_s)^2 R_n' / s}{(R_s + R_n')^2 + (X_s + X_n')^2} \quad (197)$$

$$S = \frac{N_s - N}{N_s} = \frac{w_s - w}{w_s}$$

Mechanical Loads -

1. $T_L = \text{const}$
2. $T_L \propto \omega$
3. $T_L \propto \omega^2$
4. $T_L \propto \frac{1}{\omega_s}$

! \Rightarrow Check whether constant load torque is suitable or not suitable for the given electrical drive

Let us consider the m/c is running at rated speed

$$\therefore T_d = T_L$$

$$(KV_s) \downarrow, T_d \downarrow \quad (T_d < T_L)$$

$$\therefore \omega \downarrow S \uparrow I \uparrow \therefore T_d \uparrow$$

Here m/c will slow down if \uparrow the T_d until it balances the constant T_L .

Here the m/c draws more current from the supply mains in order to \uparrow the T_d for balancing the T_L . \therefore m/c gets overheating.

Hence this mech \rightarrow load is not suitable for the drive.

$$\Rightarrow T_i \propto \omega^2$$

$$(kN_s) \downarrow \quad T_d \downarrow \quad (T_d < T_L)$$

$$\omega \downarrow \quad T_L \downarrow$$

(198)

Now speed will slow down until the Φ & decreased T_i balances the T_d . Here the m/c will not draw more current from supply line.

Such type of mech load is suitable for given electrical drive.

Applications -

Used where $T_i \propto \omega^2$.

e.g. fan loads, reciprocating pumps, compressors etc.

2. Stator frequency control of I.M -

(a) V control ($\phi < \omega_s$)

To maintain const flux we go for V/f control.
 Φ is not maintained const overflusing occurs

- I_m ↑
- harmonic distortion ↑
- losses ↑
- f_f ↑

→ We can not realize V/f control by using cyclo converters but its used only for high power low speed. With cyclo converters the maximum speed is limited to 40% of rated speed.

- We can also realize the V/f control by using PWM inverters. With PWM inverters -
 - smooth rotation is possible and some lower order harmonics can be eliminated

(199)

(b) Constant V (for $\omega > \omega_n$)

At rated speed $V_s = V_{\text{rated}}$

$$V_c \propto f \propto \phi \propto \omega$$


$f \uparrow \quad \phi \downarrow$

Here as $f \uparrow \Rightarrow \phi \downarrow$ because we cannot exceed \uparrow
the stator vlg beyond rated value. So stator vlg
is fixed at 'rated value' in this method

We can realize this method by:

Square Wave Inverter

PWM Inverter

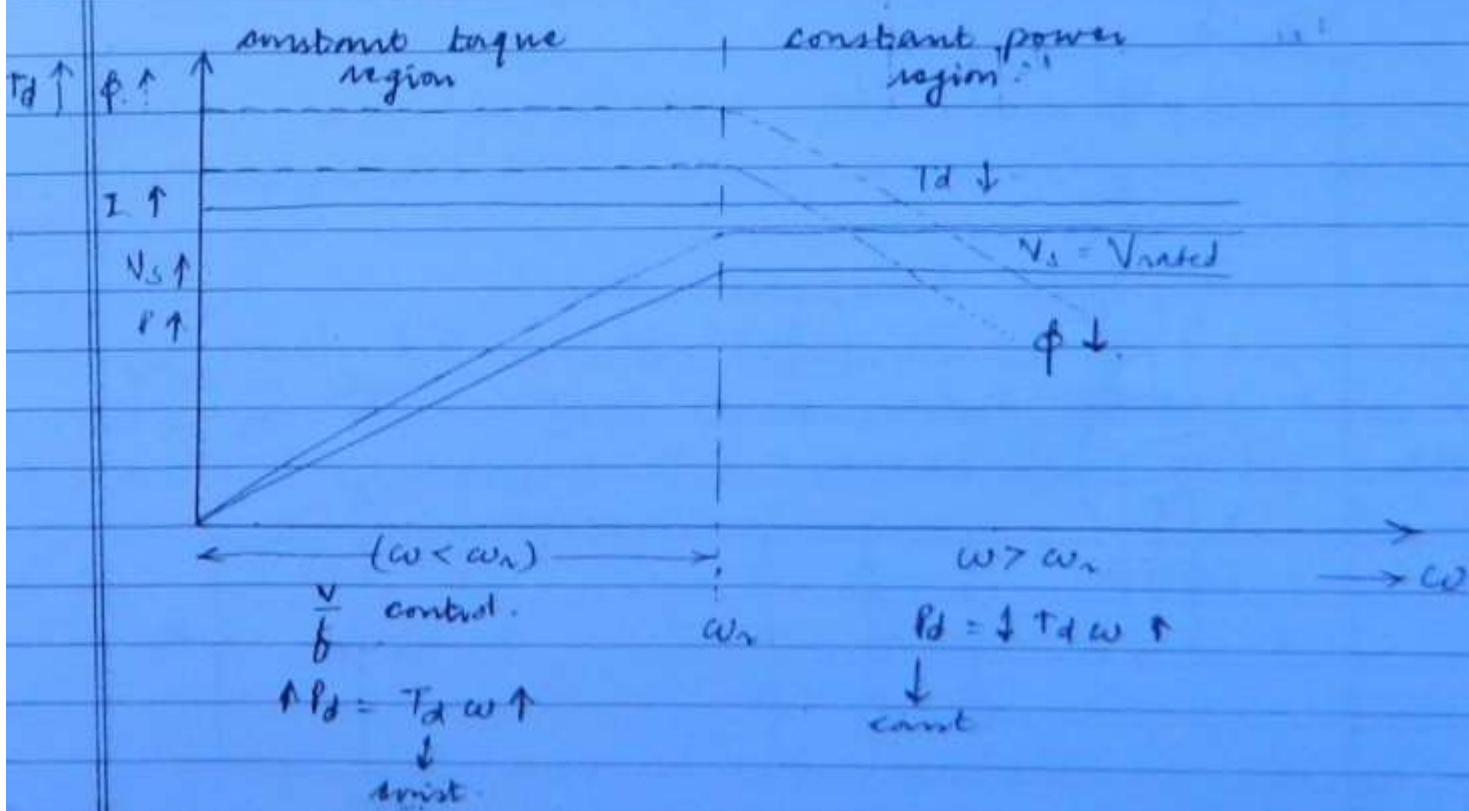


3 Rotor Resistance Control -

R Y B supply.

$$\text{Total Cu loss} = s P_g$$

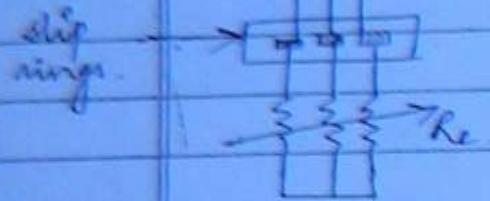
(20)

$$3 I_N^2 [R_n + \frac{1}{2} R_e] = P_s P_g$$




$s \uparrow \therefore \omega \downarrow$

Chopper Controlled Resistance -

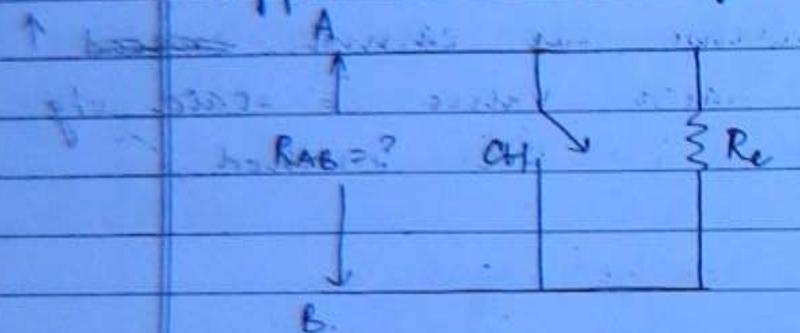

$$R_{AB} = R_e \left(\frac{T_{OFF}}{T} \right)$$
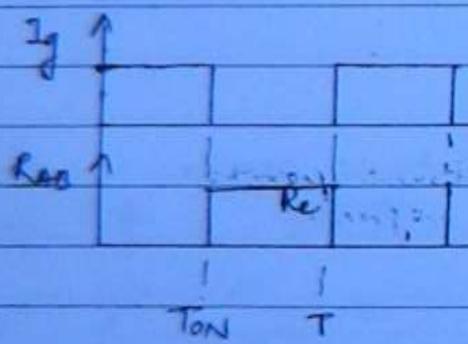
$$R_{AB} = R_e \left(1 - \alpha \right)$$



Stator Rotor Resistance Control -

R Y B.

$$f_0 = 6 \cdot s f_c$$


$s \downarrow f_0 \downarrow$

ripple in $I_d \uparrow$
 $\theta_{SR} \uparrow$

$(SR) \uparrow$

$M \uparrow$

$I_d \uparrow$
 R_e

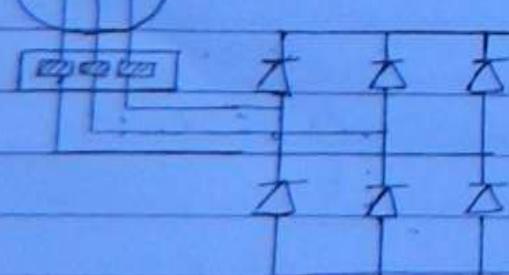

$f_0 = 6 \cdot s f_c$

Q) What's the effective resistance connected in series per phase with the rotor wdg's per phase for the above system?

(201)

$$\text{Total - Curr loss} = s P_g$$

$$3 I_n^2 R_n + I_d^2 R_d (1-\alpha) = s P_g$$

$$I_{n1} = I_0 \sqrt{\frac{2}{3}} \Rightarrow I_n = I_d \sqrt{\frac{2}{3}}$$

$$I_d = I_n \sqrt{\frac{3}{2}}$$

$$\Rightarrow 3 I_n^2 R_n + \frac{3}{2} I_n^2 R_d (1-\alpha) = s P_g$$

$$\Rightarrow 3 I_n^2 [R_n + 0.5 R_d (1-\alpha)] = s P_g$$


$$\alpha 1.5 I_n^2 [R_n + R_d]$$

eff resistance in series with
rotor wdg's per phase

This is not an efficient control cuz the slip power is dissipated in external resistance.

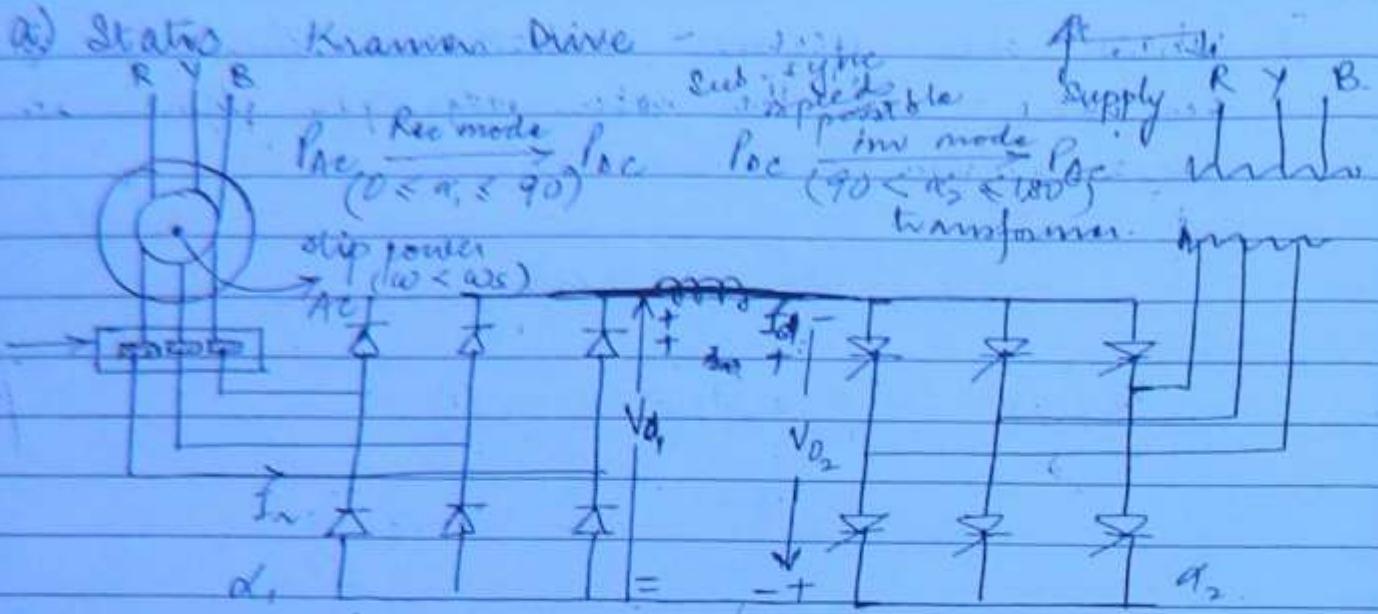4. Slip Power Recovery

This is an efficient speed control method because the slip power can be utilised or given back to supply line.



± 3 Ref polarities of converter

(DD)


± 3 Actual polarities of converter.

$$V_0 = 3 V_{ML} \cos \alpha$$


$$\alpha < 90^\circ \quad V_0 + \text{ (Rec mode)}$$

$$\alpha > 90^\circ \quad V_0 - \text{ (Inv mode)}$$

(b) Static Schenkin Line

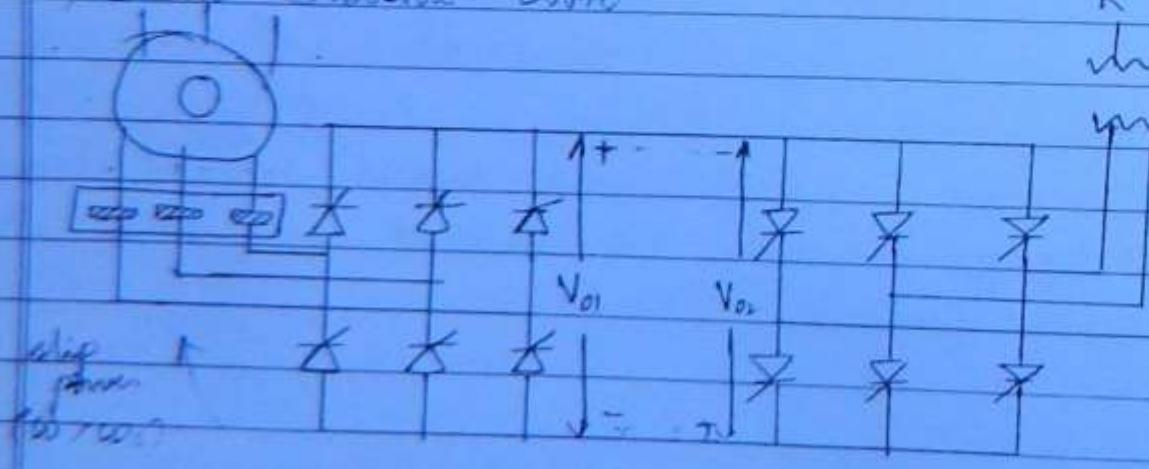

CWB chapter 5.

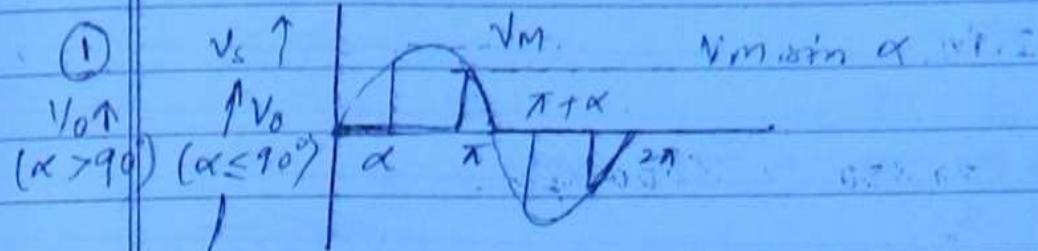

(253)

$$\rightarrow \text{peak power} = \frac{V_m^2}{R} = \frac{(280\sqrt{2})^2}{R} = \frac{(280\sqrt{2})^2}{10} = 10580 \text{ W (d)}$$

$$\text{peak power} \Rightarrow \frac{(V_m \sin \alpha)^2}{R}$$

② V_o is uncontrollable at $\alpha \leq \phi$

$$\phi = \tan^{-1} \frac{WL}{R} \Rightarrow \phi = \tan^{-1} \frac{50}{50} = 45^\circ$$

$$0 \leq \alpha \leq 45^\circ \quad (\text{a})$$

⑥ ~~and~~ Per unit power = $\frac{P_o}{P_{max}}$

$$= \frac{V_{os}^2 / R}{V_{sn}^2 / R}$$

$$= \left(\frac{V_{os}}{V_{sn}} \right)^2 = PF^2$$

$$PF = \sqrt{\text{per unit power}} \quad (\text{b})$$

Q&A chapter 6

y control of I.M -

$$N_A = \frac{100f}{s} = \frac{100 \times 50}{2} = 2500 \text{ rpm}$$

(204)

$$\theta = \frac{N_A - N_1}{N_1} = \frac{2500 - 2000}{2000}$$

$$S = 0.05$$


$$N = ? \text{ at } V_2 = 50 \quad f = 90 \text{ Hz}$$

$$N_2 = \frac{100 \times 40}{2} = 2000$$

$$0.005 = \frac{2000 - N_1}{2000}$$

$$N_1 = 1990 \text{ rpm (c)}$$

b. R_{al} in series with motor

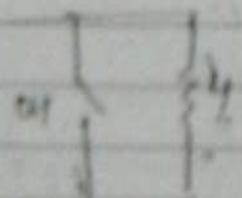

$$R_{eff} = \alpha^2 + 0.5 R_a / (1 - \alpha) \\ = \alpha^2 + 0.5 \times 4 \left(1 - \frac{T_{off}}{T} \right)$$

$$= \alpha^2 + 0.5 \times 4 \left(1 - 4 \times 10^{-3} \times 200 \right)$$

$$= 18 \text{ (c)}$$

(14) PF at $\frac{1}{2} N_A$?

$$PF = \frac{\alpha}{\pi} \cos \alpha$$

BB

$$\frac{N_S - N_A}{N_B}$$

$$N_D = 66 + 30kA^2$$

~~$$PF = \frac{V_0}{V_{max}} \sin \theta$$~~

$$V_0 = 3 V_{max} \cos \alpha = 66$$

$$At \frac{1}{2} N_A$$

$$\frac{3 V_{max} \cos \alpha}{\pi} = \frac{300 \times 440}{2}$$

$$\frac{3 \times 440 \sqrt{2} \cos \alpha}{\pi} = \frac{300 \times 440}{2}$$

$$\cos \alpha = \frac{\pi}{2\sqrt{2}} \times \frac{1}{3}$$

$$PF = \frac{\alpha}{\pi} \cos \alpha = \frac{1}{\sqrt{2}} = 0.354 \text{ (A)}$$

(15) As $\alpha \uparrow$ ripple & smoothness ↓.

At $\alpha \downarrow$ (smoothness of V_o waveform) ?

$\alpha \downarrow V_o \uparrow : \omega \uparrow$
high speed

(16) Regenerated power = $V_o I_o$

$$= V_o (1-\alpha) I_o$$

$$= 600(1-0.7)100$$


$$= 18 \text{ kW (c)}$$

TRENDS IN TRANSMISSION OF POWER


1. EHVAC

(206)

Features -

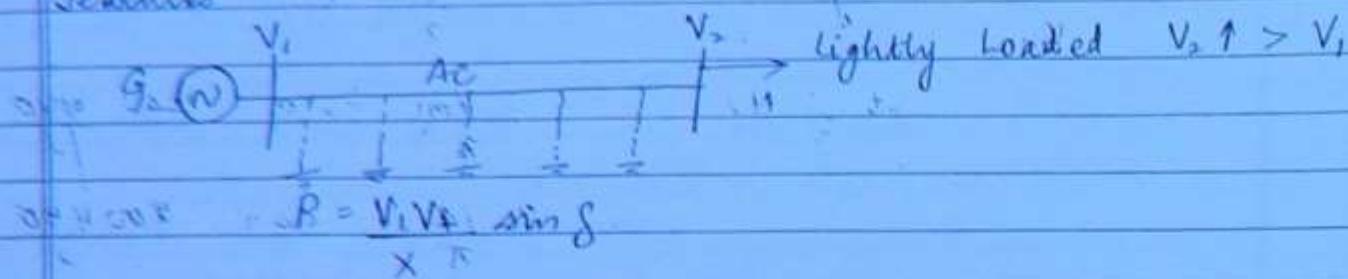

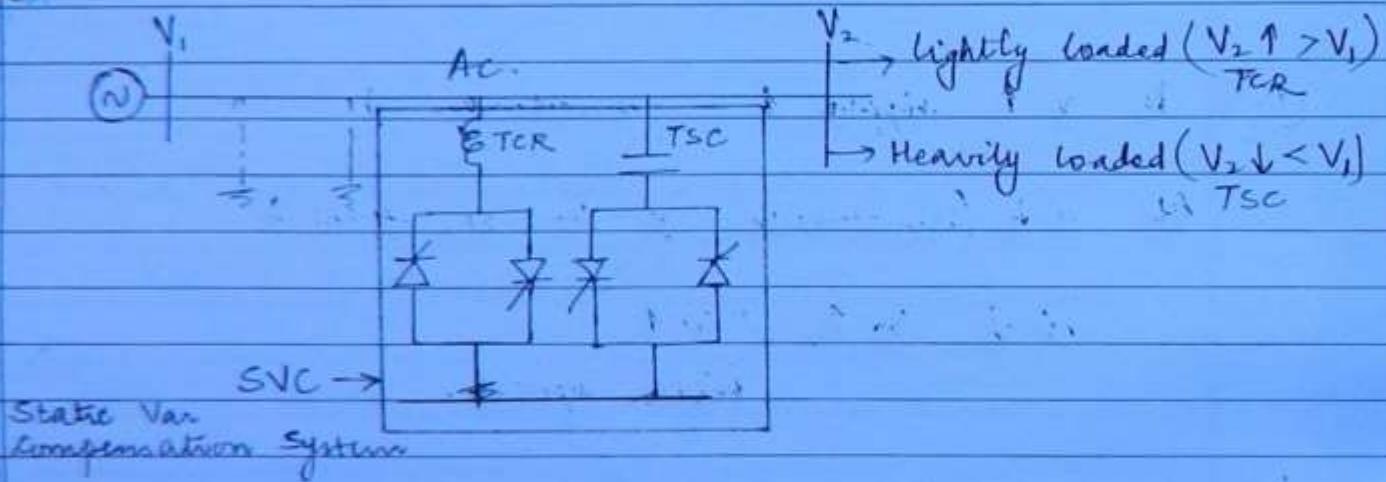- We cannot control the power flow mag & dir quickly & easily.



Thyristorised Controlled Reactor → TCR

Thyristorised 'Switched' Capacitance → TSC



- There is continuous variation of reactive power flow in the line & hence responsible for voltage fluctuations & additional power loss

- Intermediate substations are installed in the Ac line for every 200-300 km to compensate the

reactive power as per the requirement of reactive power in the line.

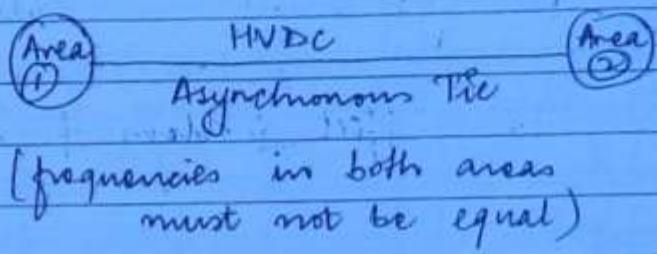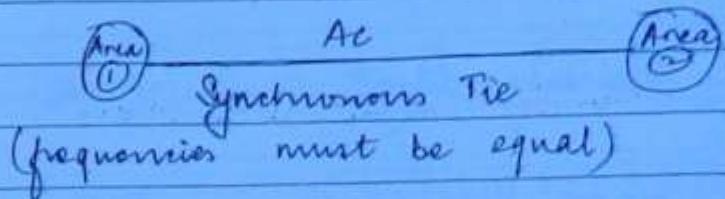(207)

- * → Other problems in the AC line is
 - Skin Effect
 - Corona loss.



- * → System disturbance in one of the area leads to power swings. If the power swings are unstable that may lead to cascaded tripping of alternators (if protection system fails)
- * → With AC interconnection frequency disturbance is carried forward to other areas.
- * → If multiple number of independent areas is interconnected by AC lines then the fault level of the system increases.

2. HVDC

- * HVDC is economical to transmit large amount of power over long distance.

(208)

* Advantages -


1. The power flow magnitude & direction can be quickly and easily controlled.
2. The transient stability limit is improved.
3. We can fast clear the fault in HVDC line.
4. There is no Skin Effect problem & corona loss is reduced.
5. HVDC can utilize Earth for its return path.
6. The phase to phase clearance, phase to ground clearance & tower height requirement is lesser in HVDC line.
7. Power handling capacity of a Bipolar HVDC line is almost twice that of 3^Ø single circuit AC line.
8. We can interconnect independent areas at different frequencies because it is an asynchronous tie.
9. Frequency disturbance is not transferred to other independent areas, with HVDC interconnection.
10. If multiple no. of independent areas is

- i interconnected by HVDC line the fault level of the system will not substantially increase.

(209)

- ii HVDC is used for underground or submarine cables even for short distance because there is no continuous charging of DC cables.

Types of HVDC

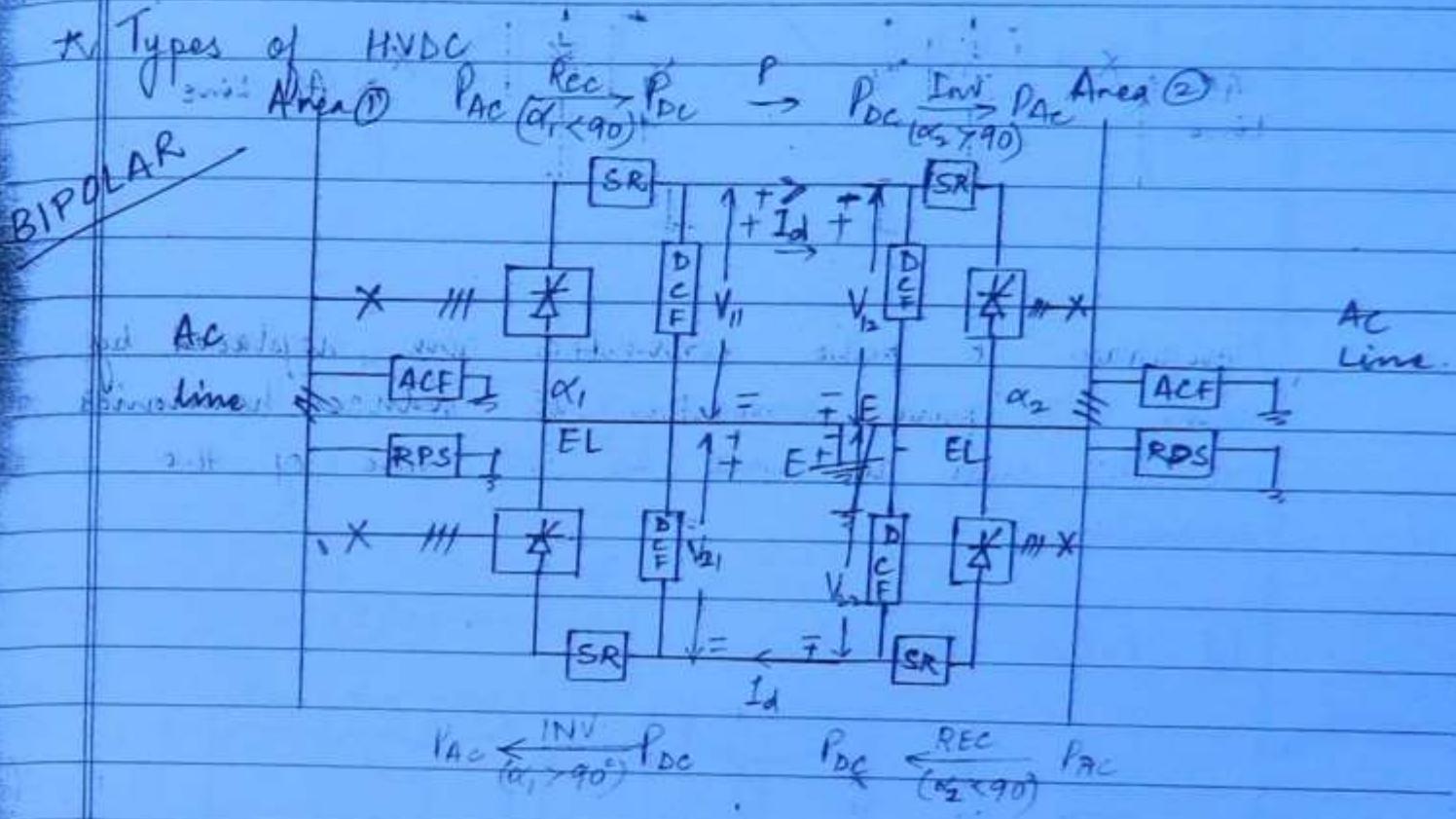

Smoothing Reactor (SR)

Used for smoothing

DC Filter (DCF)

Reduces harmonics on DC side of the converter (output side)

AC Filter (ACF)


Reduces harmonics on AC side of the converter

(21b)

Reactive Power Source (RPS)

To compensate the reactive power required for converter

MONOPOLAR Area ①

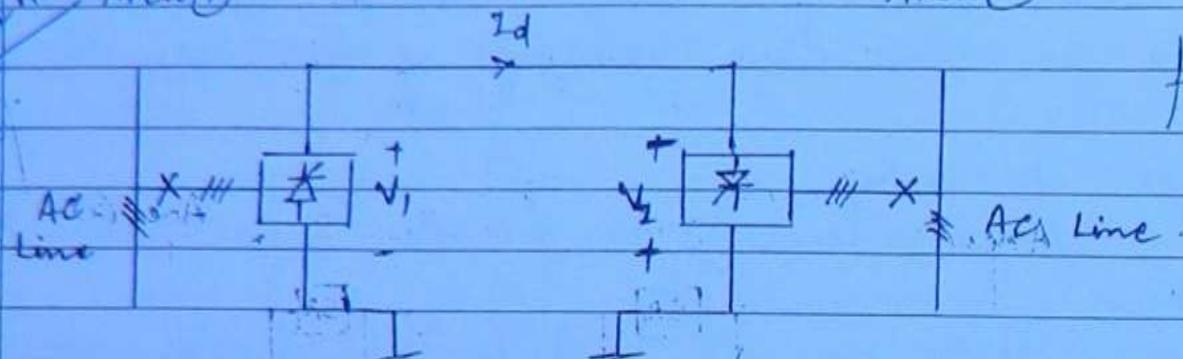


Area ②





filters are understood

Nowadays 6 pulse converters are replaced by using 12 pulse converters to reduce harmonics on AC side as well as DC side of the converter.

12 Pulse Converters -

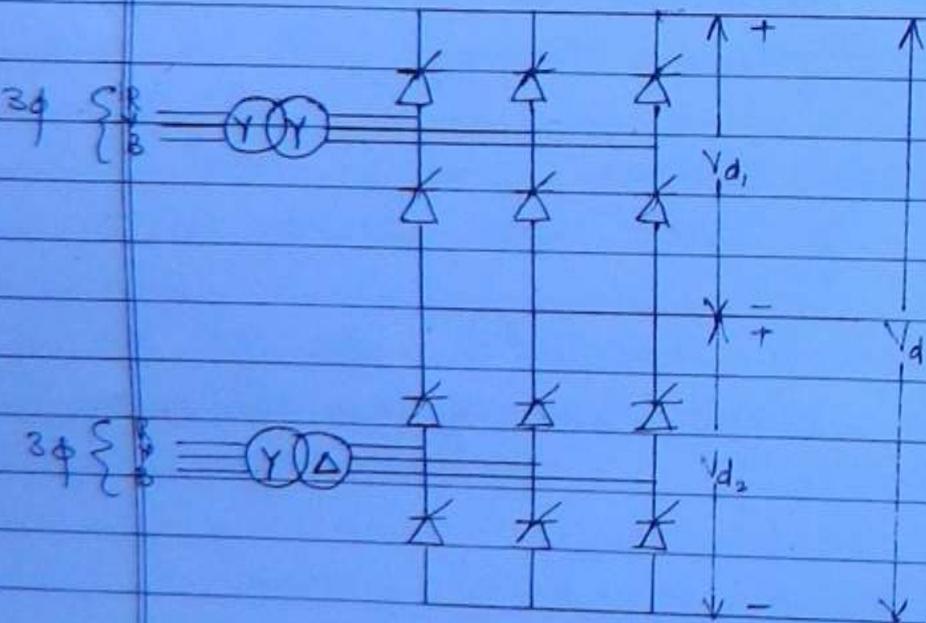

(21)

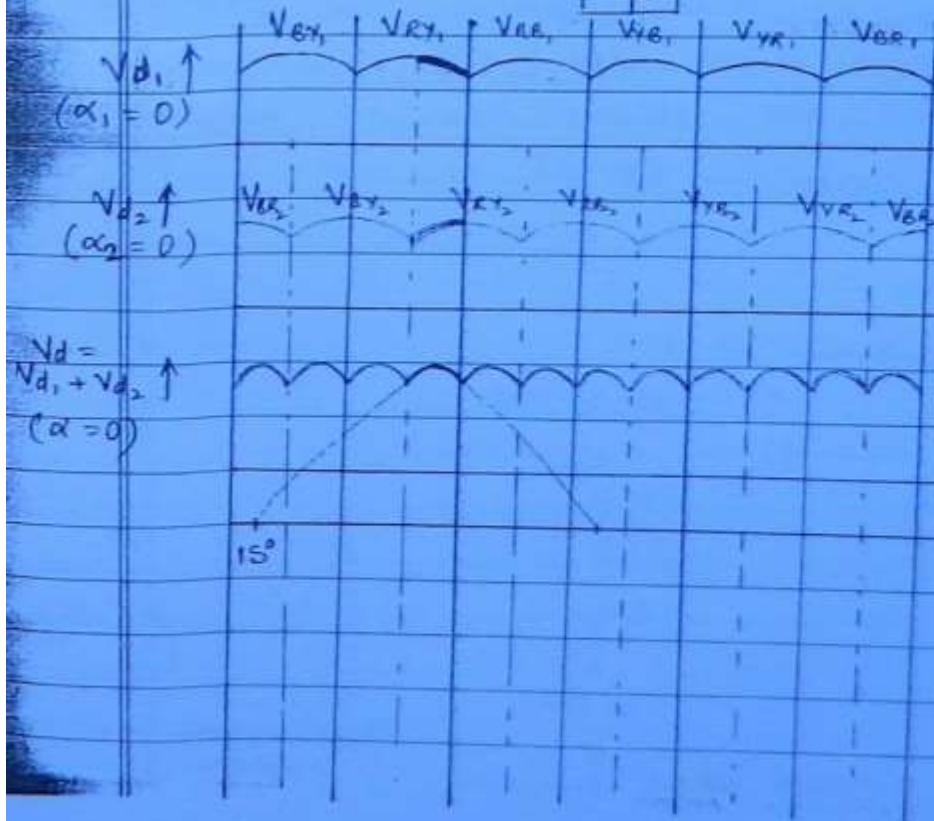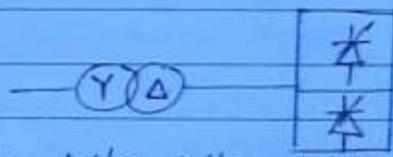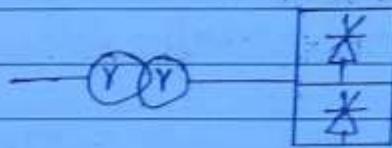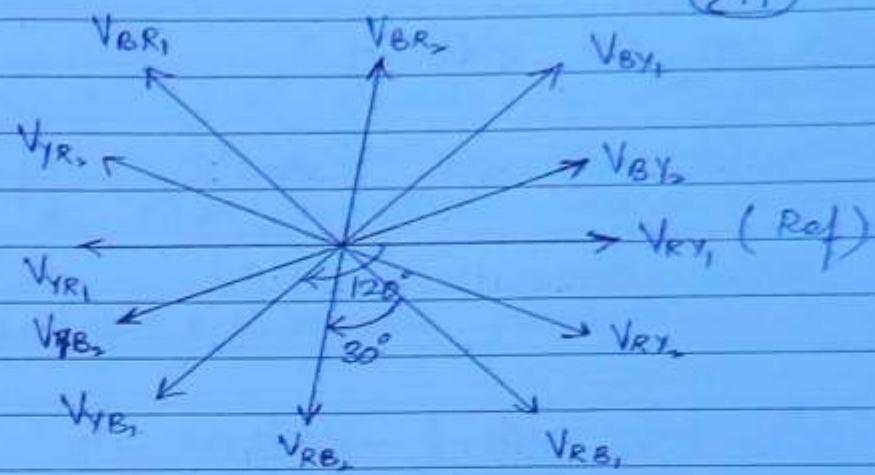

$$V_{RY_1} = V_{ML} \sin \alpha$$

$$V_{RY_2} = V_{ML} \sin(\alpha - 30^\circ)$$

$$V_{RY} = V_{RY_1} + V_{RY_2}$$

$$= V_{ML} [\sin \alpha + \sin(\alpha - 30^\circ)]$$

$$= V_{ML} [2 \sin \alpha \cos(-15^\circ)]$$

* Harmonics on AC side of δ

(212)

m pulse converter $\rightarrow m k \pm 1$

3 pulse converter $\rightarrow 2k \pm 1$

$$= 3, 5, 7, 9, 11, \dots$$

6 pulse converter $\rightarrow 6k \pm 1$

$$= 5, 7, 11, 13, 17, 19, \dots$$

12 pulse converter $\rightarrow 12k \pm 1$

$$= 11, 13, 23, 25, \dots$$

* Harmonics on DC side of δ

m pulse converter $\rightarrow mk$

3 pulse converter $\rightarrow 2k \pm 1$

$$= 2, 4, 6, 8, 10, 12, \dots$$

6 pulse converter $\rightarrow 6k$

$$= 6, 12, 18, \dots$$


12 pulse converter $\rightarrow 12k$

$$= 12, 24, 36, \dots$$


- * SMPS provides good quality of DC power supply required for some applications like ICs, digital circuits & other sensitive circuit boards.
- * SMPS operates on chopper principle.
- * At very high switching frequency, the ripple is almost reduced.
- * At such a high frequency we can reduce the size of the filter as well as transformer.
- * In SMPS the transistor operates in the switched mode (Cut-off region is used for OFF state & Saturation region for ON state).
- * SMPS is more efficient & compact in size compared to linear power supplies. In linear power supplies transistor operates in the active region & hence Power loss is higher.

Types of SMPS -

1. Flyback converter

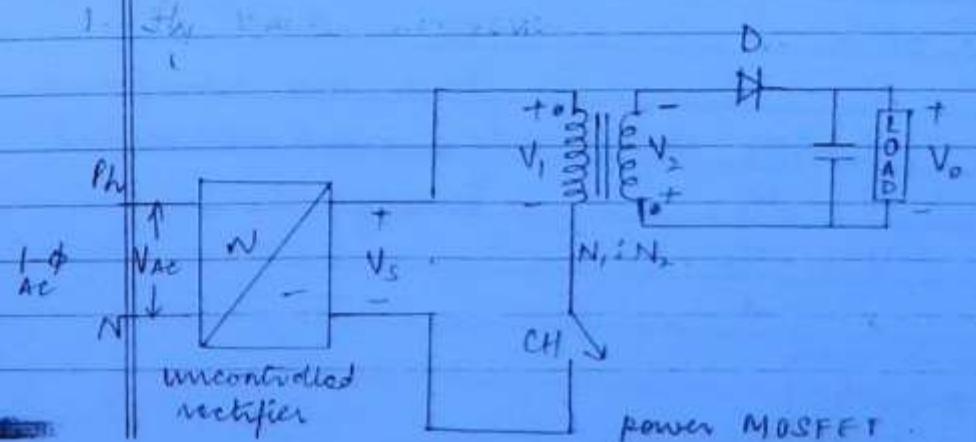

$$\therefore a = \frac{N_2}{N_1}$$

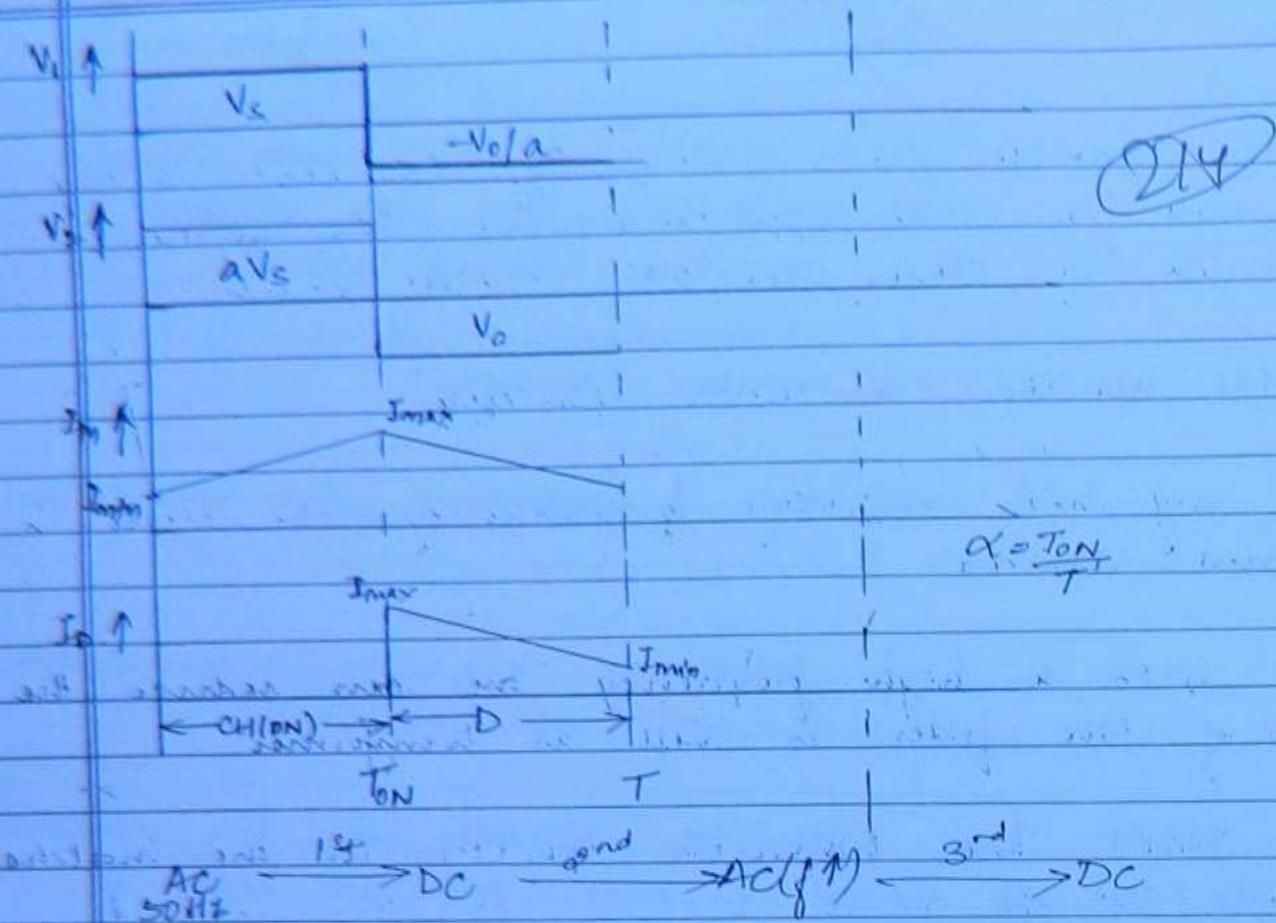

① $0 \leq t \leq T_{ON}$

$$CH \rightarrow ON \quad V_1 = V_s$$

$$D \rightarrow OFF \quad V_2 = N_2 \frac{V_1}{N_1}$$

$$V_2 = a V_1$$

transformer stores energy $\therefore I_m \uparrow$
 CH is in ON state

D is RD $\therefore I_D = 0$

② $T_{ON} \leq t \leq T$

$$CH \rightarrow OFF \quad V_2 = -V_0$$

$$D \rightarrow ON \quad V_1 = \frac{N_1}{N_2} V_2$$

$$V_1 = -\frac{V_0}{a}$$

Here the transformer releases the stored energy. $\therefore I_m \downarrow$

$$\text{Avg } \frac{V_0}{a} \Rightarrow V_0 = a \frac{\alpha V_s}{1-\alpha}$$

CWB chapter 7.

$$(4) \quad V_o = \alpha \cdot \frac{V_s}{1-\alpha}$$

(215)

$$= \alpha \cdot \frac{N_2}{N_1} \cdot \frac{T_{ON}}{T_{OFF}} \quad (c)$$

Peak Forward Blocking Voltage of chopper mito

$$= V_s + V_o$$

a.

$$(3) \quad PFB \text{ vfg} = \frac{V_s + V_o}{a}$$

$$= V_s + V_s \left(\frac{\alpha}{1-\alpha} \right)$$

$$= V_s \left[1 + \frac{\alpha}{1-\alpha} \right] = 115\sqrt{2} \left[1 + \frac{0.3}{1-0.3} \right]$$

$$= 932.34 \text{ V} \quad (a)$$

Output dc vfg of front end mito

\rightarrow with max coupling = V_m

\rightarrow peak Ac i/p vfg


\rightarrow with vfg coupling = αV_m

(1) mark the highest freq given

Q. Push-pull converter

Q10

3 Full Bridge Type -

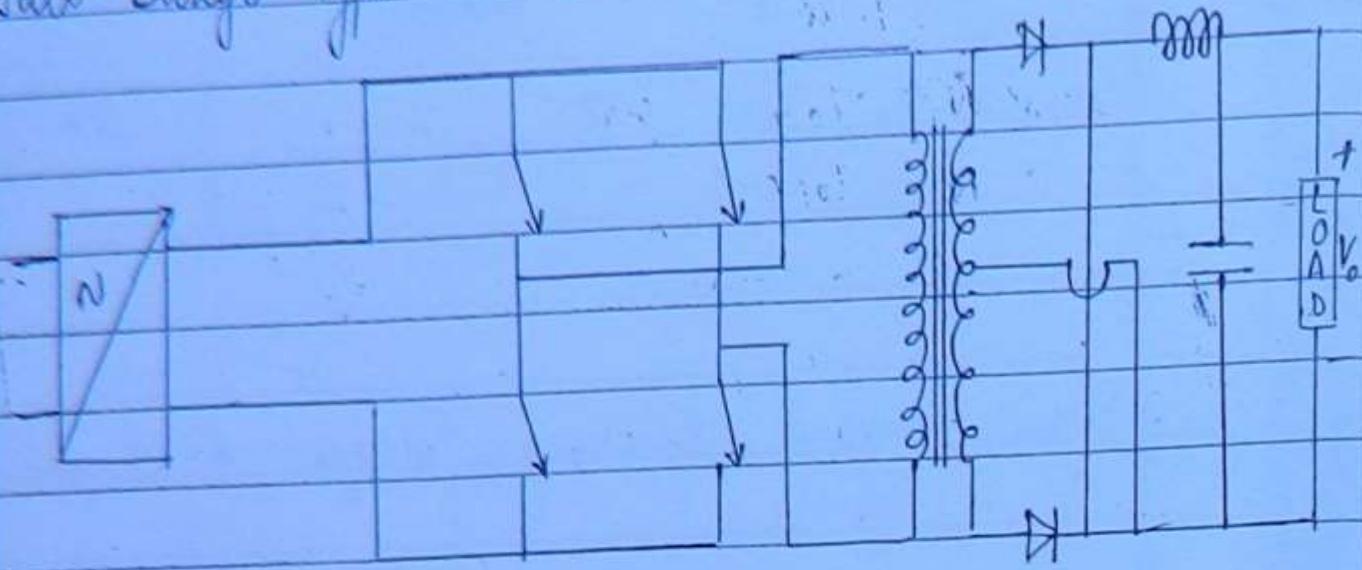

$$eV = \frac{1}{2} V_o \sin(4\pi f t)$$

Remembering Formulas -

(217)

R-load -

$$V_o = \frac{V_m}{d\pi} (1 + \cos \alpha) \rightarrow 1 \text{ pulse}$$

cont. $V_o \propto \cos \alpha$
discont. $V_o \propto (1 + \cos \alpha)$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha) \rightarrow d \text{ pulse}$$

$$V_o = \frac{V_{mph}}{d\pi/3} [1 + \cos(\alpha + 30^\circ)] \rightarrow (\alpha > 30^\circ)$$

3 pulse

In 3 pulse
 ↳ $\alpha < 30^\circ$ cont.
 ↳ $\alpha > 30^\circ$ discont.

$$V_o = \frac{V_{mph}}{2\pi/6} [1 + \cos(\alpha + 60^\circ)] \rightarrow (\alpha > 60^\circ)$$

In 6 pulse:
 ↳ $\alpha < 60^\circ$ cont
 ↳ $\alpha > 60^\circ$ discont.

$$V_o = \frac{V_{ML}}{\pi/6} [1 + \cos(\alpha + 60^\circ)] \rightarrow (\alpha > 60^\circ)$$